

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EPE EVERYDAY PRACTICAL ELECTRONICS

www.epemag.co.uk

www.epemag.com

ULTRASONIC EAVESDROPPER

Listen in to the echo-location 'chirps' of bats and other ultrasonic sounds



MAGNETIC CARTRIDGE PREAMPLIFIER

Resurrect your old LPs and 78s and dub them onto CDs or MP3 files

SUPER SPEEDO CORRECTOR

Get your electronic speedo reading correctly

Plus S-VIDEO TO COMPOSITE VIDEO CONVERTER

An easy-to-build adaptor

\$7.95 US \$9.95 CAN
SEPT 2008 PRINTED IN THE UK



0 74470 07806 7

08

Copyright © 2008, Wimborne Publishing Ltd
(Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU, UK)
and
TechBites Interactive Inc.,
(PO Box 857, Madison, Alabama 35758, USA)
All rights reserved.

WARNING!

The materials and works contained within *EPE Online* — which are made available by Wimborne Publishing Ltd and TechBites Interactive Inc — are copyrighted. You are permitted to make a backup copy of the downloaded file and one (1) hard copy of such materials and works for your personal use.

International copyright laws, however, prohibit any further copying or reproduction of such materials and works, or any republication of any kind. TechBites Interactive Inc and Wimborne Publishing Ltd have used their best efforts in preparing these materials and works. However, TechBites Interactive Inc and Wimborne Publishing Ltd make no warranties of any kind, expressed or implied, with regard to the documentation or data contained herein, and specifically disclaim, without limitation, any implied warranties of merchantability and fitness for a particular purpose.

Because of possible variances in the quality and condition of materials and workmanship used by readers, *EPE Online*, its publishers and agents disclaim any responsibility for the safe and proper functioning of reader-constructed projects based on or from information published in these materials and works.

In no event shall TechBites Interactive Inc or Wimborne Publishing Ltd be responsible or liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or any other damages in connection with or arising out of furnishing, performance, or use of these materials and works.

USB Connectivity for Embedded Designs

Microcontrollers

Digital Signal
Controllers

Analog

Serial
EEPROMs



If you need Full-Speed USB 2.0 device, embedded host, dual role and On-The-Go solutions, Microchip Technology has them available today. We offer 8-, 16- and 32-bit MCUs with USB connectivity, providing easy migration with a single development environment. This maximizes pin compatibility and seamless code migration from 20 to 100 pins, enabling you to scale your USB design with ease.

Download FREE USB software including source code:

- Host Stack
- OTG Stack
- Device Stack
- Class Drivers (HID, Mass Storage and CDC Drivers)
- Thumb Drive Support (Mass Storage Driver, SCSI Interface, 16-bit and 32-bit File Management, Application Software)

Core	Flash Program Memory	Pins	USB Type
8-bit	Up to 128 Kbytes	20 - 80	Device
16-bit	Up to 256 Kbytes	64 - 100	Device, Embedded Host, Dual Role, OTG
32-bit	Up to 512 Kbytes	64 - 100	Device, Embedded Host, Dual Role, OTG

GET STARTED IN 3 EASY STEPS

1. Purchase a USB Starter Kit
2. Download Free USB Software
3. Order Free Samples

www.microchip.com/usb

USB Starter Kits accelerate development of USB designs using 8-, 16- or 32-bit MCUs and are available at www.microchipDIRECT.com or from one of our authorised distributors



Intelligent Electronics start with Microchip

microchip
DIRECT
www.microchipdirect.com

www.microchip.com/usb

MICROCHIP

ISSN 0262 3617

• **PROJECTS** • **THEORY** •
• **NEWS** • **COMMENT** •
• **POPULAR FEATURES** •



VOL. 37. No.9 **September 2008**

EPE EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

www.epemag.co.uk

EPE Online: www.epemag.com

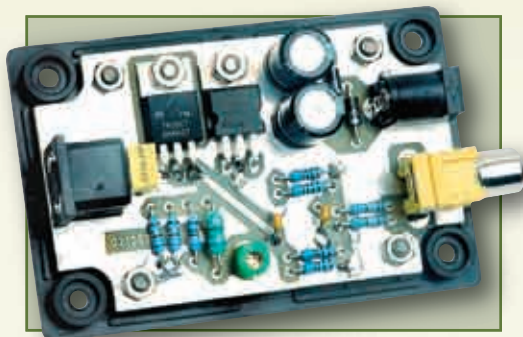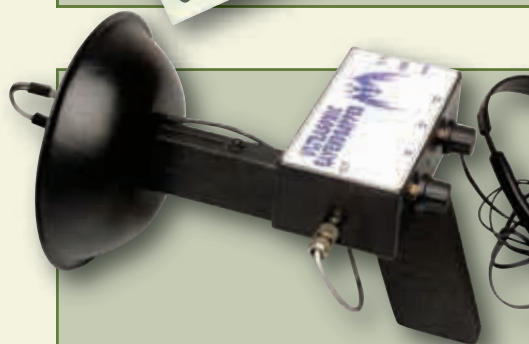

© Wimborne Publishing Ltd 2008. Copyright in all drawings, photographs and articles published in *EVERYDAY PRACTICAL ELECTRONICS* is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our October 2008 issue will be published on Thursday 11 September 2008, see page 72 for details.

Everyday Practical Electronics, September 2008

Projects and Circuits

- | | |
|--|-----------|
| SUPER SPEEDO CORRECTOR by John Clarke and Julian Edgar
Watch your speed! | 10 |
| ULTRASONIC EAVESDROPPER by Jim Rowe
A low-cost project that will let you listen to the 'unlistenable' | 18 |
| S-VIDEO TO COMPOSITE VIDEO CONVERTER by Jim Rowe
Boost your picture quality with this simple, easy-to-build adaptor | 32 |
| MAGNETIC CARTRIDGE PREAMPLIFIER by John Clarke
Dust off your old record player, resurrect your favourite old 78s, 45s and LPs and dub them onto CDs or MP3 files | 40 |
| INGENUITY UNLIMITED Sharing your ideas with others
Noise Generator | 55 |

Series and Features

- | | |
|--|-----------|
| TECHNO TALK by Mark Nelson
Colour conundrums | 16 |
| PRACTICALLY SPEAKING by Robert Penfold
Case study | 38 |
| TEACH-IN 2008 - USING PIC MICROCONTROLLERS - PART 11
by John Becker
Final article - Randomising values with PICs, plus a Fruit Machine! | 48 |
| PIC32 STARTER KIT REVIEW by Mike Hibbett
Microchip's newest processor | 52 |
| CIRCUIT SURGERY by Ian Bell
LED brightness and switching inductive loads | 56 |
| PIC N' MIX by Mike Hibbett
Interfacing PICs to the Internet | 58 |
| NET WORK by Alan Winstanley
Spare a thought; Chicken run | 66 |

Regulars and Services

- | | |
|--|-----------|
| EDITORIAL | 7 |
| NEWS - Barry Fox highlights technology's leading edge
Plus everyday news from the world of electronics | 8 |
| BACK ISSUES Did you miss these? | 30 |
| CD-ROMS FOR ELECTRONICS
A wide range of CD-ROMs for hobbyists, students and engineers | 60 |
| SUBSCRIBE TO EPE and save money | 63 |
| READOUT John Becker addresses general points arising | 64 |
| DIRECT BOOK SERVICE
A wide range of technical books available by mail order, plus more CD-ROMs | 67 |
| EPE PCB SERVICE | 70 |
| ADVERTISERS INDEX | 72 |

Readers' Services • Editorial and Advertisement Departments

7

PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £14.95
18Vdc Power supply (PSU010) £18.95
Leads: Parallel (LDC136) £3.95 / Serial (LDC441) £3.95 / USB (LDC644) £2.95

NEW! USB & Serial Port PIC Programmer



USB/Serial connection. Header cable for ICSP. Free Windows XP software. See website for PICs supported. ZIF Socket and USB lead extra. 18Vdc.

Kit Order Code: 3149KT - **£39.95**

Assembled Order Code: AS3149 - **£49.95**

NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows XP Software. ZIF Socket and USB lead not incl.



Assembled Order Code: AS3128 - **£44.95**

Assembled with ZIF socket Order Code: AS3128ZIF - **£59.95**

'PICALL' ISP PIC Programmer



Will program virtually all 8 to 40 pin serial-mode AND parallel-mode (PIC15C family) PIC microcontrollers. Free Windows software. Blank chip auto detect for super fast bulk programming. Optional ZIF socket.

Assembled Order Code: AS3117 - **£24.95**

Assembled with ZIF socket Order Code: AS3117ZIF - **£39.95**

ATMEL 89xxx Programmer



Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16Vdc.

Kit Order Code: 3123KT - **£24.95**

Assembled Order Code: AS3123 - **£34.95**

Introduction to PIC Programming

Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual, Programming Hardware (with LED test section), Win 3.11—XP Programming Software (Program, Read, Verify & Erase), and 1 rewritable PIC16F84A that you can use with different code (4 detailed examples provided for you to learn from). PC parallel port.



Kit Order Code: 3081KT - **£16.95**

Assembled Order Code: AS3081 - **£24.95**

PIC Programmer Board

Low cost PIC programmer board supporting a wide range of Microchip® PIC™ microcontrollers. Requires PC serial port. Windows interface supplied. Kit Order Code: VK8076KT - **£21.95**



PIC Programmer & Experimenter Board

The PIC Programmer & Experimenter Board with test buttons and LED indicators to carry out educational experiments, such as the supplied programming examples. Includes a 16F627 Flash Microcontroller that can be reprogrammed up to 1000 times for experimenting at will. Software to compile and program your source code is included. Kit Order Code: VK8048KT - **£22.95**
Assembled Order Code: VVM111 - **£39.95**



Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. 12Vdc PSU for all units: Order Code PSU445 £8.95

USB Experiment Interface Board

5 digital input channels and 8 digital output channels plus two analogue inputs and two analogue outputs with 8 bit resolution.



Kit Order Code: VK8055KT - **£20.95**

Assembled Order Code: VVM110 - **£39.95**

Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two & Ten Channel versions also available.



Kit Order Code: 3180KT - **£44.95**

Assembled Order Code: AS3180 - **£54.95**

Computer Temperature Data Logger

Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range or tree software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor.



Kit Order Code: 3145KT - **£17.95**

Assembled Order Code: AS3145 - **£24.95**

Additional DS1820 Sensors - **£3.95 each**

Most items are available in kit form (KT suffix) or pre-assembled and ready for use (AS prefix).

4-Ch DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc. Kit Order Code: 3140KT - **£54.95**
Assembled Order Code: AS3140 - **£69.95**



8-Ch Serial Port Isolated I/O Relay Module

Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA. Kit Order Code: 3108KT - **£54.95**
Assembled Order Code: AS3108 - **£64.95**



Infrared RC 12-Channel Relay Board



Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm. Supply: 12Vdc/0.5A

Kit Order Code: 3142KT - **£47.95**

Assembled Order Code: AS3142 - **£59.95**

Audio DTMF Decoder and Display



Detect DTMF tones from tape recorders, receivers, two-way radios, etc using the built-in mic or direct from the phone line. Characters are displayed on a

16 character display as they are received and up to 32 numbers can be displayed by scrolling the display. All data written to the LCD is also sent to a serial output for connection to a computer. Supply: 9-12V DC (Order Code PSU445). Main PCB: 55x95mm.

Kit Order Code: 3153KT - **£24.95**

Assembled Order Code: AS3153 - **£34.95**

Telephone Call Logger

Stores over 2,500 x 11 digit DTMF numbers with time and date. Records all buttons pressed during a call. No need for any connection to computer during operation but logged data can be downloaded into a PC via a serial port and saved to disk. Includes a plastic case 130x100x30mm. Supply: 9-12V DC (Order Code PSU445).



Kit Order Code: 3164KT - **£54.95**

Assembled Order Code: AS3164 - **£69.95**

Hot New Products!

Here are a few of the most recent products added to our range. See website or join our email Newsletter for all the latest news.

Bipolar Stepper Motor Chopper Driver

New bipolar chopper driver gives better performance from your stepper motors. It uses a dual full bridge motor driver based on SGS Thompson chips L297 & L298. Motor current for each phase is set using an on-board potentiometer. Can handle motor winding currents of up to 2 Amps per phase. Operates from a DC supply voltage of 9-36V. All basic motor controls provided including full or half stepping of bipolar steppers and direction control. Synchronisable when using multiple drivers. Perfect for desktop CNC applications.

Kit Order Code: 3187KT - **£29.95**

Assembled Order Code: AS3187 - **£39.95**



Shaking Dice

This electronic construction kit is great fun to build and play with. Simply shake and watch it slowly roll to stop on a random number.

Kit Order Code: VMK150KT - **£9.95**



Running MicroBug

This electronic construction kit is an attractive bright coloured bug-shaped miniature robot. The microbug is always hungry for light and travels toward it!

Kit Order Code: VMK127KT - **£9.95**



Video Signal Cleaner

Digitally cleans the video signal and removes unwanted distortion in video signal. In addition it stabilises picture quality and luminance fluctuations.

You will also benefit from improved picture quality on LCD monitors or projectors.

Kit Order Code: VK8036KT - **£19.95**

Assembled Order Code: VVM106 - **£26.95**



PC Interface Board

This interface card excels in its simplicity of use and installation. The card is connected in a very simple way to the printer port (there is no need to open up the computer). Likewise there is no need to install an extra printer port, even if a printer is to be used. This can be connected to the card in the usual manner. Connection to the computer is optically isolated, so that damage to the computer from the card is not possible.

Kit Order Code: VK8000KT - **£59.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Motor Speed Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

DC Motor Speed Controller (100V/7.5A)



Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque

at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H.

Kit Order Code: 3067KT - **£13.95**

Assembled Order Code: AS3067 - **£21.95**

PC / Standalone Unipolar Stepper Motor Driver

Drives any 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps max. Provides speed and direction control. Operates in stand-alone or PC-controlled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9Vdc. PCB: 80x50mm.

Kit Order Code: 3179KT - **£12.95**

Assembled Order Code: AS3179 - **£19.95**



Bi-Polar Stepper Motor Driver

Drive any bi-polar stepper motor using externally supplied 5V levels for stepping and direction control. These usually come from software running on a computer.

Supply: 8-30Vdc. PCB: 75x85mm.

Kit Order Code: 3158KT - **£17.95**

Assembled Order Code: AS3158 - **£27.95**



Bidirectional DC Motor Controller



Controls the speed of most common DC motors (rated up to 32Vdc/10A) in both the forward and reverse direction. The

range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections.

Kit Order Code: 3166v2KT - **£17.95**

Assembled Order Code: AS3166v2 - **£27.95**

AC Motor Speed Controller (700W)

Reliable and simple to install project that allows you to adjust the speed of an electric drill or single phase 230V AC motor rated up to 700 Watts.

Simply turn the potentiometer to adjust the motors RPM. PCB: 48x65mm. Not suitable for use with brushless AC motors.

Kit Order Code: 1074KT - **£12.95**

Assembled Order Code: AS1074 - **£18.95**

Box Order Code 2074BX - **£5.95**



QUASAR
electronics
Get Plugged In!

**Credit
Card
Sales
0871
717
7168**

Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

500-in-1 Electronic Project Lab

Top of the range. Complete self-contained electronics course. Takes you from beginner to 'A' Level standard and beyond! Contains all the hardware and manuals to assemble 500 projects. You get 3 comprehensive course books (total 368 pages) - *Hardware Entry Course*, *Hardware Advanced Course* and a microprocessor based *Software Programming Course*. Each book has individual circuit explanations, schematic and connection diagrams. Suitable for age 12+.

Order Code EPL500 - **£149.95**

Also available - 30-in-1 £16.95, 50-in-1 £21.95, 75-in-1 £32.95 £130-in-1 £39.95 & 300-in-1 £59.95 (details on website)



Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

Two-Channel USB Pc Oscilloscope

This digital storage oscilloscope uses the power of your PC to visualize electrical signals. Its high sensitive display resolution, down to 0.15mV, combined with a high bandwidth and a sampling frequency of up to 1GHz are giving this unit all the power you need.

Order Code: VPCSU1000 - **£289.95**



Personal Scope 10MS/s

The Personal Scope is not a graphical multimeter but a complete portable oscilloscope at the size and the cost of a good multimeter. Its high sensitivity - down to 0.1mV/div - and extended scope functions make this unit ideal for hobby, service, automotive and development purposes. Because of its exceptional value for money, the Personal Scope is well suited for educational use.

Order Code: VHPS10 - **£129.95 £119.95**

See website for more super deals!



www.QuasarElectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads

EVERYDAY PRACTICAL ELECTRONICS FEATURED KITS

September '08

Everyday Practical Electronics Magazine has been publishing a series of popular kits by the acclaimed Silicon Chip Magazine Australia. These projects are 'bullet proof' and already tested down under. All Jaycar kits are supplied with specified board components, quality fibreglass tinned PCBs and have clear English instructions. Watch this space for future featured kits.

Jaycar
Electronics


**NEW
FOR 08**

GALACTIC VOICE SIMULATOR KIT

KC-5431 £13.25 plus postage & packing

This galactic voice simulator kit has effect and depth controls to allow you to vary the effect to simulate everything from the metallically-challenged C-3PO, to the hysterical ranting of Daleks. The kit includes PCB with overlay, enclosure, speaker panel and all components.

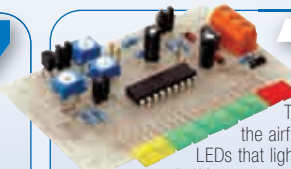- Requires 9V battery.
- As published in EPE Magazine August 2008



VOLTAGE MONITOR KIT

KC-5424 £6.00 plus postage & packing

This versatile kit will allow you to monitor the battery voltage, the airflow meter or oxygen sensor in your car. The kit features 10 LEDs that light in response to the measured voltage, preset 9-16V, 0-5V or 0-1V ranges, complete with a fast response time, high input impedance and auto dimming for night driving. Kit includes PCB with overlay, LEDs and all electronic components with clear English instructions.


- Requires 12VDC power
- Recommended box: UB5 HB-6015 £0.83
- As published in EPE Magazine November 2007.

STARSHIP DOOR SOUND EMULATOR

KC-5423 £11.75 plus postage & packing

This easy to build kit emulates the unique noise made when the cabin doors on the Starship Enterprise open & close. The 'shut' noise is also duplicated. The sound emulator can be triggered by switch contacts (normally open) which means you can use a reed magnet switch, IR beam or PIR detector to trigger the unit.

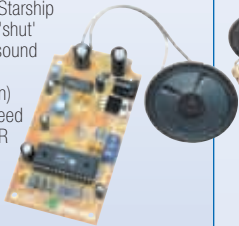- Requires 9-12VDC power
- Kit supplied with PCB & all electronic components
- As published in EPE Magazine June 2008




3V TO 9V DC TO DC CONVERTER KIT

KC-5391 £4.95 plus postage & packing

Allows you to use regular Ni-Cd or Ni-MH 1.2V cells, or alkaline 1.5V cells for 9V applications. Using low cost, high capacity

rechargeable cells, this kit will pay for itself in no time. You can use any 1.2-1.5V cells you desire. Imagine the extra capacity you would have using two 9000mAh D cells in replacement of a low capacity 9V cell.

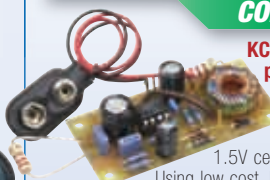- Kit supplied with PCB & all electronic components.
- As published in EPE Magazine June 2007



INTERCOOLER WATER SPRAY CONTROLLER

KC-5422 £3.00 plus postage & packing

Intercooler water sprays are a very effective and inexpensive way of upgrading intercooler performance. Using a 'dump' system to trigger the spray often results in the need for frequent water top-ups. Simply add these few components to the Smart Fuel Mixture Display Kit (KC-5374) and reduce water consumption by up to two-thirds with no loss in cooling efficiency.

- Kit supplied with PCB & all electronic components
- As published in EPE Magazine March 2008




THE FLEXITIMER KIT

KA-1732 £5.95 plus post & packing

This kit uses a handful of components to accurately time intervals from a few seconds to a whole day. It can switch a number of different output devices and can be powered by a battery or mains plugpack. The kit includes PCB and all components. Requires 12-15VDC wall adaptor.

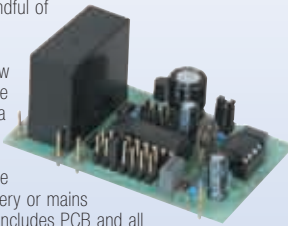- As published in EPE Magazine September 2007.



AUDIO VIDEO BOOSTER KIT

KC-5350 £31.95 plus post & packing

This kit will boost your video and audio signals preserving them for the highest quality transmission to your projector or large screen TV. It boosts composite, S-Video, and stereo audio signals. Kit includes case with silkscreened and punched panels, PCB and all electronic components.

- As published in EPE Magazine March 2006




STUDIO 350 HIGH POWER AMP KIT

KC-5372 £55.95 plus post & packing

It delivers a whopping 350WRMS into 4 ohms, or 200WRMS into 8 ohms. Using eight 250V 200W plastic power transistors, it is super quiet, with a signal to noise ratio of -125dB(A) at full 8 ohm power. Harmonic distortion is just 0.002%, & frequency response is almost flat (less than -1dB) between 15Hz and 60kHz.

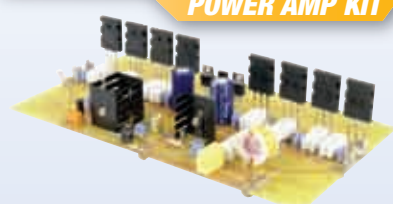- Kit supplied in short form with PCB and electronic components.
- Kit requires heatsink and +/- 70V power supply (a suitable supply is described in the instructions).
- As published in EPE Magazine October & November 2006



SMS CONTROLLER MODULE

KC-5400 £15.95 + postage & packing

Control appliances or receive alert notification from anywhere. By sending plain text messages this kit will allow you to control up to 8 devices. At the same time, it can also monitor four digital inputs. It works with old Nokia handsets such as the 5110, 6110, 3210, and 3310, which can be bought inexpensively if you do not already own one. Kit supplied with PCB, pre-programmed microcontroller and all electronics components with clear English instructions.

- Requires a Nokia data cable which can be readily found in mobile phone accessory stores.
- As published in EPE Magazine March 2007




RFID SECURITY MODULE RECEIVER KIT

KC-5393 £28.95 plus post & packing

Radio Frequency Identity (RFID) is a contact free method of controlling an event such as a door strike or alarm etc. An "RFID Tag" transmits a unique code when energised by the receiver's magnetic field. As long as a pre-programmed tag is recognised by the receiver, access is granted. This module provides normally open and normally closed relay contacts for flexibility. It works with all EM-4001 compliant RFID tags. Kit supplied with PCB, tag, and all electronic components.

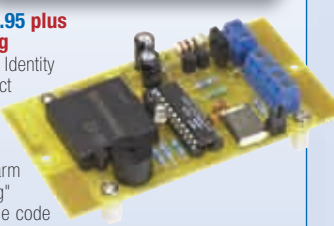- As published in EPE Magazine August 2007



- Secure on-line ordering
- ALL prices in Pounds Sterling
- Minimum order ONLY 10 PDS

**ORDER YOUR
FREE
CATALOGUE
TODAY!**



Jaycar
Electronics

0800 032 7241

jaycarelectronics.co.uk

IDEAL KITS FOR ELECTRONIC ENTHUSIASTS




ULTRA LOW DISTORTION AMPLIFIER MODULE

KC-5470 £26.25 plus postage & packing

This ultra low distortion amplifier module uses the new ThermalTrak power transistors and is largely based on the high-performance Class-A amplifier. This improved circuit has no need for a quiescent current adjustment or a Vbe multiplier transistor and has an exceptionally low distortion figure. Kit supplied with PCB and all electronic components. Heatsink and power supply not included.

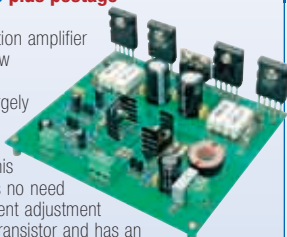- Output Power: 135WRMS into 8 ohms and 200WRMS into 4 ohms
- Freq Resp. at 1W: 4Hz to 50kHz
- Harmonic Distortion: <.008% from 20Hz to 20kHz




NEW FOR 08

BRIDGE MODE ADAPTOR

KC-5469 £7.75 plus postage & packing

IDEAL FOR STEREO AMPLIFIERS. Lets you run a stereo amplifier in 'Bridged Mode' to effectively double the power available to drive a single speaker. There are no mods required on the amplifier and the signal processing is done by the kit before the signals are fed to the stereo amp. Ideal for say, using a stereo amp as an occasional PA amp for social functions or using an old amplifier to drive a sub-woofer in a home theatre.

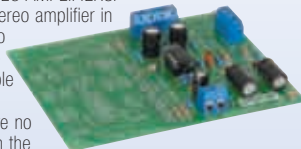- Kit supplied with silk screened PCB and all specified components.
- Requires balanced (+/-) power supply.



LOW COST DIGITAL MULTIMETER

QM-1500 £2.25 plus postage & packing

This full featured Digital Multimeter is perfect for the home handyman or young experimenter and will give years of reliable service. It features a huge 10A DC current range as well as diode and transistor testing functions. Also measures AC & DC volts and resistance. At this price you should buy two!



LED WATER LEVEL INDICATOR MKII KIT

KC-5449 £10.25 plus postage & packing

This simple circuit illuminates a string of LEDs to quickly indicate the water level in a rainwater tank. The more LEDs that illuminate, the higher the water level is inside the tank. The input signal is provided by ten sensors located in the water tank and connected to the indicator unit via light duty figure-8 cable. Kit supplied with PCB with overlay, machined case with screen printed lid and all electronic components.

- Requires 12-18V AC or DC 500mA plugpack.



PIC LOGIC PROBE KIT

KC-5457 £4.50 plus postage & packing

Most logic probes are designed to operate on 5V rails. This design operates on a wide voltage range down to 2.8V so it's suitable for use on the most modern circuits. It's also extremely compact with SMT devices on a PCB only 5mm wide, so it will fit inside a very slim case. It's capable of picking up a pulse only 50mS long and will also detect and hold infrequent pulses when in latch mode. Kit includes PCB and all specified electronic components including pre-programmed PIC. You'll need to add your own case and probe - a clear ballpoint pen case and a needle, works well.



STAINLESS STEEL TOOLS

5" Stainless Steel Long Nose Pliers

TH-1888 £4.95 plus postage & pkg

Made from polished stainless steel, have a leaf spring and have serrated jaws.

Stainless Steel Side Cutters - 115mm

TH-1890 £3.50 + postage & pkg

High quality small side cutters that have thick (2mm) blades and soft comfort plastic spring loaded handles.



THEREMIN SYNTHESIZER KIT

KC-5295 £17.50 plus postage & packing

The Therman is a strange musical instrument that was invented early last century but is still used today. The Beach Boys' classic hit "Good Vibrations" featured a Therman. By moving your hand between the antenna and the metal plate, you can create unusual sound effects.

Kit includes a machined, silkscreened, and pre drilled case, circuit board, all electronic components with clear English instructions.

- Required 9VDC wall adapter (Maplin #GS74R £7.99)



IR REMOTE EXTENDER MKII KIT

KC-5432 £7.25 plus postage & packing

Operate your DVD player or digital decoder using its remote control from another room. It picks up the signal from the remote control and sends it via a 2-wire cable to an infrared LED located close to the device. This improved model features fast data transfer, capable of transmitting pay TV digital remote control signals using the Pace 400 series decoder. Kit supplied with case, screen printed front panel, PCB with overlay and all electronic components.

- Requires 9 VDC power (Maplin #GS74R £7.99) and 2-wire cable



RESISTANCE WHEEL

RR-0700 £5.75 plus postage & packing

Great for experiments or selecting the best resistance for a circuit. Choose from 36 x 0.25W 5% resistors ranging from 5 ohms to 1M ohms. Comes complete with leads and insulated crocodile clips.



FREE CATALOGUE

Checkout Jaycar's extensive range

We have kits & electronic projects for use in:

- Audio & Video
- Car & Automotive
- Computer
- Power
- Lighting
- Test & Meters
- Learning & Educational
- General Electronics Projects
- Gifts, Gadgets & Just for fun!

For your FREE catalogue logon to www.jaycarelectronics.co.uk/catalogue or check out the range at www.jaycarelectronics.co.uk



POST & PACKING CHARGES

Order Value	Cost
£10 - £49.99	£5
£50 - £99.99	£10
£100 - £199.99	£20
£200 - £499.99	£30
£500+	£40

Max weight 12lb (5kg).
Heavier parcels POA.
Minimum order £10.

Note: Products are despatched from Australia, so local customs duty & taxes may apply. Prices valid till 30/09/08

HOW TO ORDER

- ORDER ON-LINE: www.jaycarelectronics.co.uk
- PHONE: 0800 032 7241*
- FAX: +61 2 8832 3118*
- EMAIL: techstore@jaycarelectronics.co.uk
- POST: P.O. Box 107, Rydalmere NSW 2116 Australia
- ALL PRICING IN POUNDS STERLING
- MINIMUM ORDER ONLY £10

*Australian Eastern Standard Time (Monday - Friday 09.00 to 17.30 GMT + 10 hours only)
Expect 10-14 days for air parcel delivery

0800 032 7241

jaycarelectronics.co.uk

Jaycar
Electronics

PCB Production - Development

0.1" Copper Stripboard

Size	Tracks/Holes	
25 x 64mm	9T / 25H	£0.24
64 x 95mm	24T / 27H	£0.87
95 x 127mm	36T / 50H	£1.41
95 x 432mm	36T / 170H	£4.39
100 x 100mm	39T / 38H	£1.40
100 x 500mm	39T / 199H	£7.50
119 x 455mm	46T / 179H	£5.40
Stripboard track cutter		£1.99

Solderless Breadboard

Tie Points & Size	Power Rails	
390 81 x 60mm	2	£2.75
840 175 x 67mm	2	£4.86
740 175 x 55mm	1	£3.32
640 175 x 42mm	0	£3.08

Many other sizes available,
also jump wires & matrix board.

PCB Production - Drafting Materials

A4 Artwork Film (per 10 sheets)

Clear Manual Film	£1.20
Clear Laser Film	£1.75
White HQ Laser Film	£4.62

Etch Resist Pens

"Dalo" Pen	£3.36
"Staedtler" Fine Pen	£1.20

Etch Resist Transfers

Seno mixed DIL pads	£2.24
Seno mixed Rnd pads	£2.24
Alfac mixed pads	£1.84
Transfer Spatular	£1.25

We carry the full range of Seno & Alfac PCB transfers, see our [web site](#) for full details.

Soldering Irons

We carry in stock a wide range of soldering iron and soldering accessories. Irons from 12 to 100 Watts.

25W 240V Ceramic	£6.00
30W 240V Basic	£4.68

Desolder Pumps

Basic 165 x 18mmØ	£2.85
Antistatic 195mm	£4.12
Antex Mini 198mm	£6.52
Antex Pro 210mm	£11.11

Soldering Station

A 48W adjustable temperature soldering station with a rotary dial, LED Temperature metering, on-off switch, iron holder and tip cleaning sponge. This station features accurate heat sensing for instant compensation & stable temperatures. Adjustable temperature range of 150 - 420°C, Low voltage iron with Silicone cable. Supply: 240V, Iron: 24V 48W

Model 167-540 £49.00

Soldering Station

A 48W adjustable temperature soldering station with a rotary dial, Digital Temperature Indication, on-off switch, iron holder and tip cleaning sponge. This station features accurate heat sensing for instant compensation & stable temperatures. Adjustable temperature range of 150 - 480°C, Low voltage iron with Silicone cable. Supply: 240V, Iron: 24V 48W

Model 167-570 £52.23

Digital Multimeter

Model: 121-120

Price: £11.47

A highly featured digital multimeter for professional use. Offers 30 ranges and 8 functions including temperature, capacitance, diode, continuity and hFE measurement. Large 3.5 digit LCD display with automatic polarity indicator. Supplied with shrouded test leads, K type temperature probe and shock proof rubber holster.

Technical Specifications

DC voltage 200mV - 1000V (±0.5%)	
AC volts 2V - 700V (±0.8%)	
DC current 2mA - 20A (±1.2%)	
AC current 200mA - 20A (±1.8%)	
Resistance 200 Ohms - 20M Ohms (±0.8%)	
Capacitance 2000pF - 20µF (±2.5%)	
Temperature 0°C - 1000°C (±1.5%)	
Frequency 20kHz (±1%)	
Max display 1999	
Power supply 9V (PP3 battery)	
Dimensions 88 x 173 x 40 mm	

PCB Production - Processing Equipment

We carry a large range of the photographic & chemical processing equipment for PCB production, a full list with full technical specifications is available in our catalogue or visit our web site.

UV Exposure units

2 x 8W Tubes, 6 min timer	
229 x 159mm working area	
Model 332-002	£95.00
4 x 15W Tubes, 7½ min timer	
330 x 260mm working area	
Model 332-004	£207.99

Chemical Processing

Low cost plastic tray	£2.90
Process tanks feature electrically operated pumps and/or heaters with thermostat control, suitable.	
ET20 Low cost Etching Tank with heater & pump.	£42.84
Universal Tank with heater	
Model 333-007	£160.00
Bubble etch tank with heater & bubble pump.	
Model 333-004	£196.00

Any of these items, carriage £5.50

PCB Production - Tools

Drill Bits

HSS parallel shank bits available in sizes from 0.3mm to 2.0mm	
0.3-0.95mm in 0.05mm steps	£0.60ea £4.00/10
1.0-2.0mm in 0.1mm steps	£0.40ea £3.60/10

HSS Reduced shank (2.35mm) bit available in sizes from 0.6mm to 1.7mm in 0.1mm steps £0.84ea £7.60/10

Reground Tungsten carbide reduced shank available in sizes from 0.6 to 1.6mm in 0.1mm steps £1.90

Drilling Machines

Expo Zircon 12V drill, 3.8mm capacity, 11900rpm £14.20

Minicraft MX1 230V, 8000 - 21000rpm with chuck & collet. Model EPE270-390 normal price £48.51

SPECIAL PRICE £31.02

Servisol Products

Aerosols

200ml Switch Cleaner	£2.30
200ml Freezer	£4.75
400ml Foam Cleaner	£2.50
400ml Cleaner / Lubricant	£2.99
75ml Vite Head Cleaner	£1.94
200ml Aero Klene	£3.33
200ml Aero Duster	£5.13
400ml Isopropyl alcohol	£3.42

Tubes

10g Heatsink Compound	£1.66
25g Heatsink Compound	£2.60
50g Silicone grease	£3.16

Bench Power Supplies

A range of single output regulated bench power supplies with variable voltage & current limiting. Features: Short circuit and "Foldback" overload protection, Metal case with on/off switch, outputs via Red, Black & Green (Earth) 4mm shrouded sockets.

Model 461-540	0-20V 2A	£19.95
Model 461-550	0-30V 0-3A	£59.95
Model 461-552	0-50V 0-3A	£69.50
Model 461-554	0-30V 0-10A	£105.90

Panel Meters

High quality analogue panel meters, class 2, zero point correction, mirror scale. Meter size 46 x 60mm, Cutout size: 38mmØ.

Range	Int Ω	All meters £5.89 each
0-50uA	6k5	
0-100uA	1k0	
0-1mA	200Ω	
0-10mA	20Ω	
0-50mA	1Ω	
0-100mA	0.065	
0-500mA	0.012	
0-1A	60mΩ	
0-3A	20mΩ	
0-5A	12mΩ	
0-15A	4mΩ	
0-10V	10k	
0-15V	15k	
0-30V	30k	
±50uA	1k9	

Magnifying Desk Lamp

A high quality scratch resistant magnifying glass fitted to a balanced swivel arm and desk mount. An integral fluorescent tube provides illumination. Magnification: 3x Lens: 120mmØ Tube: 22W Daylight simulation.

Model: 028-205 £28.80

PCB Production - Laminates

Copper clad - paper

Single sided low cost paper composite board

100 x 160mm Board	£0.58
100 x 220mm Board	£0.62
160 x 233mm Board	£1.34
220 x 233mm Board	£1.86
8" x 12" Board	£2.22

Copper clad - glass fibre

Single & Double 1.6mm 305g/m²

100 x 160mm Single	£1.06
100 x 220mm Single	£2.17
160 x 233mm Single	£2.29
220 x 233mm Single	£3.98
8" x 12" Single	£3.98
100 x 160mm Double	£1.09
100 x 220mm Double	£1.23
160 x 233mm Double	£2.30
220 x 233mm Double	£2.90
8" x 12" Double	£4.05

Photoresist Coated

1.6mm 35 micron Pre-coated with a high quality photoresist layer. Available in low cost paper composite or Glass fibre, Single & Double sided. Other sizes also available.

Size	Paper Single	Paper Double	Glass Fibre Single	Glass Fibre Double
4 x 6"	£1.47	£1.82	£1.89	£2.17
6 x 12"	£4.20	£5.04	£5.60	£6.23
9 x 12"	£6.30	£7.70	£8.40	£9.38
10 x 12"	£8.19	£10.01	£10.78	£11.83
12 x 12"	£8.26	£10.08	£10.99	£12.25
100 x 160mm			£2.35	£2.66
203 x 114mm			£3.01	£3.43
220 x 100mm			£3.08	£3.71
233 x 160mm			£4.83	£5.32
233 x 220mm			£6.86	£7.70

PCB Production - Chemicals

100ml Aerosol Photoresist spray, covers 2m²	£5.12
50g Powder developer, makes 1lt	£1.09
500g Powder developer, makes 10lt	£7.08
250g Ferric Chloride Pellets, makes 500ml	£1.68
500g Ferric Chloride Pellets, makes 1lt	£3.04
2.5kg Ferric Chloride Pellets, makes 5lt	£9.84
1.1kg Clear Fine etch crystals, makes 5lt	£17.58
90g Tin Plating Powder, makes 1lt	£11.58
200ml Aerosol Flux spray	£3.41
110ml Aerosol PCB Laquer spray	£3.54

Tools - Cutters & Strippers

We carry a wide range of specialist tools for the electronics industry including:

Side Cutters

130mm Low cost	£1.99
115mm Draper	£2.38
Wire Strippers	
130mm Low cost	£2.30
150mm Draper 5mmØ	£5.86

Tools - Ratchet Crimping Pliers

High quality ratchet crimping pliers for various terminals including Automotive, Data, Power and Data connections.

Red / Blue / Yellow	£15.80
BNC / TNC RF series	£15.62
RJ11/12 & 45 Series	£11.76
Non insulated crimps	£23.53
CK® Tools Crimp Pliers	
Green/Red/Blue	£30.62
Red/Blue/Yellow	£24.49
0.24-2.5mm² crimps	£30.62
0.5-6.0mm² crimps	£28.22
Non insulated crimps	£28.22

Cable - Ribbon

7/0.127mm Grey ribbon cable on a 0.05" 1.27mm pitch with a red identifying stripe. Supplied by 305mm (1ft) or on full 30.5m (100ft) reels.

Size	per 305mm	per Reel
10 Way	£0.10	£5.80
14 Way	£0.14	£7.50
16 Way	£0.16	£8.58
20 Way	£0.27	£14.34
26 Way	£0.26	£13.94
34 Way	£0.34	£18.22
40 Way	£0.40	£21.44
40 Way	£0.50	£26.80
60 Way	£0.64	£33.92
IDC Crimp tool		£10.60

CAT5e Networking

UTP Cable
Conforms to CAT5E
100MHz standard,
ETA verified TIA/EIA 568-B.2

305m Box	£63.56
100m Reel	£24.30

exc carriage.

RJ45 Outlet Kit

Backing Box
2 Gang Plate
RJ45 Module
Blank Module
Coloured id inserts,
£2.86ea £2.29 (10+)

Tools

Plastic punch down tool & cable stripper	£1.24
Professional punch down IDC & trim tool	£4.94

Outlets

CAT5e Outlet Module	£1.70
1 Gang Plate (2 Mods)	£0.50
2 Gang Plate (4 Mods)	£0.88
½ Module Blank	£0.25
1 Module Blank	£0.35
2 Module Blank	£0.45

Other keystone outlets, switches & accessories available. Patch & Cross-over leads from £0.50

Now available online
Our large range of Tools by



The Electronics Shop.co.uk
Sound & Lighting
equipment for the Entertainment Industry



Tel: 0191 2514363
Fax: 0191 2522296
sales@esr.co.uk

Station Road
Cullercoats
Tyne & Wear
NE30 4PQ



Prices Exclude Vat @17.5%.
UK Carriage £2.50 (less than 1kg)
£5.50 greater than 1kg or >£30
Cheques / Postal orders payable to
ESR Electronic Components Ltd.
PLEASE ADD CARRIAGE & VAT TO ALL ORDERS

Editorial Offices:
EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
Wimborne Publishing Ltd., Sequoia House, 398a Ringwood Road,
Ferndown, Dorset BH22 9AU
Phone: (01202) 873872. Fax: (01202) 874562.
Email: enquiries@epemag.wimborne.co.uk
Web Site: www.epemag.co.uk
EPE Online (downloadable version of EPE): www.epemag.com
EPE Online Shop: www.epemag.wimborne.co.uk/shopdoor.htm
See notes on **Readers' Technical Enquiries** below – we regret
technical enquiries cannot be answered over the telephone.
Advertisement Offices:
Everyday Practical Electronics Advertisements
Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU
Phone: 01202 873872 Fax: 01202 874562
Email: stewart.kearn@wimborne.co.uk

Breadboard Projects

This issue marks the end of the current Teach-In series; it has been a fascinating journey through the world of PICs, and John Becker is to be congratulated for providing such an illuminating and engaging tour – thank you John.

It's a tough act to follow, but I think we've come up with something that will prove just as useful and educational. Starting next month in the October issue, we're launching a 13-part series of breadboard-based projects written by Dr Malcolm Plant. This will be a true learning-for-beginners series, where the emphasis will be on design and making things work, rather than getting caught up in the intricacies of PCBs, soldering and more advanced construction techniques – hence the use of breadboards. The beauty of 'breadboarding' is that if you make a mistake then all you need to do is pull out a wire or component and reposition it – no solder suckers, lifted tracks or cooked ICs to worry about. It's a technique popular with advanced designers as well as new recruits, so you'll be in good company as you start out on your first circuits.

The real appeal of this series though is the quality of the circuits and projects – just because the articles are aimed at beginners does not mean that all you'll do is switch the odd LED on and off – quite the opposite. The projects lined up for the series include: a rain check device, a thermostat, an intercom, a frost alert, a motion detector and even an AM radio and sound meter, so plenty for all you budding circuit builders to get your teeth into.

In a practical hands-on environment such as electronics, 'doing' is far and away the best method of learning. We are sure this series of articles will not only be as popular as the recent Teach-In PIC one, but will also help you get to grips with the fundamentals of electronic design. And, as always, we look forward to your letters and emails describing triumphs and the occasional hiccup!

Malcolm Plant

AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see opposite) and from all UK newsagents (distributed by SEYMOUR). *EPE* can also be purchased from retail magazine outlets around the world. An Internet online version can be purchased and downloaded for just \$18.99US (approx £9.50) per year, available from www.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £19.95, 12 months £37.90, two years £70.50; Overseas: 6 months £23.00 standard air service or £32.00 express airmail, 12 months £44.00 standard air service or £62.00 express airmail, 24 months £83.00 standard air service or £119.00 express airmail.

Online subscriptions, for downloading the magazine via the Internet, \$18.99US (approx £9.50) for one year available from www.epemag.com.

Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to *EPE* Subs. Dept., Wimborne Publishing Ltd, Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Maestro or Visa. (For past issues see the Back Issues page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue PVC, printed with the magazine logo in gold on the spine. Price £7.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days, but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Maestro and MasterCard accepted. Send, fax or phone your card number, card expiry date, valid from date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK website. **Overseas customers** – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editor: MATT PULZER

Consulting Editors: DAVID BARRINGTON
JOHN BECKER

Subscriptions: MARILYN GOLDBERG

General Manager: FAY KEARN

Editorial/Admin: (01202) 873872

Advertising and Business Manager:

STEWART KEARN (01202) 873872

On-line Editor: ALAN WINSTANLEY

EPE Online (Internet version) Editors:

CLIVE (Max) MAXFIELD and ALVIN BROWN

Publisher: MIKE KENWARD

READERS' TECHNICAL ENQUIRIES

Email: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years' old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. We are not able to answer technical queries on the phone.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in *EPE* employ voltages that can be lethal. You should not build, test, modify or renovate any item of mains-powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of *EVERYDAY PRACTICAL ELECTRONICS* take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are bona fide, the magazine and its publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts. The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment, as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



NEWS

A roundup of the latest Everyday
News from the world of
electronics



New Sky Decoder

Barry Fox reports that the door is now opening for new devices which let a TV or PC receive encrypted satellite broadcasts from Sky

News broke recently when NDS – the company owned by Rupert Murdoch's News Corporation and developer of the VideoGuard encryption system used by Murdoch's Sky in the UK and DirecTV in the US – held briefings in London.

"There is a lot of work in our labs that may never see the light of day. But some projects are ready to become consumer products in the next two to five years," Nigel Smith NDS's Chief Marketing Officer and Jonathan Beavon, Director of Segment Marketing, revealed at recent briefings and demonstrations in London.

All existing Sky receivers have a dedicated slot for a VideoGuard smart card. But Sky and NDS have never licensed VideoGuard for use in PCs, TVs or third party set top boxes (STBs) which have a Common Interface slot for a Conditional Access Module. The CAM is like a PCMCIA card for a laptop that has its own smart card slot. The CAM has software onboard which works with the smart card to decrypt the TV signal and send it back into the TV or STB or PC. "We don't believe in the European Common Interface" says Smith. "The content can be taken when it comes out of the module. In the US, the PCMCIA solution used is more secure."

NDS has recently worked with SanDisk on SD memory cards that carry and play encrypted audio and video. Now,

NDS will launch its own solution; the VideoGuard PC Key is a USB stick which lets a PC receive encrypted TV broadcasts, for display on the PC screen or a TV, and transfer the programme to a personal media player for portable play. A conventional STB connects to a PC by USB ports, while a USB stick, with an in-built smart card system, works with DRM software on the PC to de-encrypt the programme.

Portable play

The signal can be reformatted for portable play and transmitted by WiFi or hard-wire, with encryption, to a phone or personal media player. Connection can be automatic, with the STB sending the PMP any programmes that have been recorded by the DVR but not yet watched. Programme transfers can be made as rental or electronic gifts. The USB key can also store the programme for physical transfer.

The encryption process must change each time it is used because PC architecture is open to hackers. "We are talking seriously to two operators in the US and two in Europe about a service launch at the beginning of next year. Sky has seen it", says Smith guardedly.

NDS thinks that with around one third of pay TV subscribers now using digital video recorders, the time is right to introduce targeted adverts. A broadcaster,

such as Sky or DirecTV, can 'push' a library of 30 second advertising slots into a subscribers' DVR so that the DVR can replace off-air adverts with sales pitches of more interest to the individual viewer. The same system can take adverts from the Internet and reformat them for TV display. "People will start liking adverts again" says Smith hopefully.

Time-out

Smith and Beavon acknowledge that DRM and encryption can be bypassed and defeated simply by copying the analogue output from a STB. "But the analogue hole is getting smaller," says Smith. "Like the ozone layer, it's disappearing. The use of HDMI and HDCP is making it harder to copy."

Time for analogue is running out, and analogue copying has to be done in real time. With a lot of material to copy it's just not viable for most people. Lack of bandwidth has been holding things back. But that's changing too."

NDS leaves no doubt it is gunning for Apple. "iTunes dominates the music market. But it is not the same for video, where there is so much material continually being originated. Apple does not yet have anything like the width of video content it has for music. There is an opportunity for the operators to use a different system for video – if they strike early enough. If they don't, the market goes to iTunes or the Internet."

CIRCUIT SPECIALISTS ARRIVE

Circuit Specialists was founded in the US in 1971 (www.circuitspecialists.com). Over the last 37 years the company has grown into one of the largest distributors of electronic equipment and supplies in the US, having built a reputation for quality and customer care along the way. Products are sourced for their reliability and value for money.

Products that have formed Circuit Specialists' core business over recent years are now available to customers in the EU. You can buy at the same competitive

prices without the shipping costs and the customs issues normally associated with importing from the US.

Based in Manchester, England, Circuit Specialists Europe (www.circuitspecialists.co.uk or www.circuitspecialists.eu), specialise in providing a quality range of products aimed at the hobbyist, the designer and the small commercial enterprise.

The company stock a select range of soldering and desoldering stations, and a wide range of associated accessories.

Own-brand bench power supplies are manufactured for the company, enabling them to be very competitively priced. A long-standing relationship with Chinese company Heng Fu ensures the supply of a range of enclosed switching power supplies, which are extremely reliable and offer excellent value for money.

Take a look at www.circuitspecialists.co.uk where, as we go to press, there is 10% off everything* in the Mid-season Sale. See their advert on page 71.

WIRE-FREE POWER

WildCharge Inc has announced the release to the general public of its adapters that WildCharge-enable Apple iPhone, iPod touch and Blackberry Pearl and 8800. The company's WildCharger wire-free charging pad, winner of this year's CES Best of Innovations Award, portable power category, is a sleek, flat charging pad that delivers up to 15 Watts of power, capable of simultaneously charging up to four small devices, such as cellular phones, portable music players, digital cameras, and other similar electronic devices.

"WildCharge's technology is more than a simple charging solution for mobile devices – it's a true revolution that will ultimately eliminate the array of tangled chargers, adapters and cords consumers currently deal with on a regular basis," claimed WildCharge CEO Dennis Grant, while displaying WildCharge's device adapter for Apple's iPhone.

For more information browse www.wildcharge.com.



FREE LINUX DRIVER

The new Linux driver from Pico Labs allows programmers to control the PicoScope 2000 Series and PicoScope 3000 Series scopes using their own software. Linux programmers can now have access to Pico's full range of entry-level and general-purpose oscilloscopes.

Anybody with a PC and a spare USB port can download and use the driver free of charge and with no licensing restrictions. The driver is supplied as an RPM package that has been tested with Fedora 8, Ubuntu 8.04 and openSUSE 10.4, and is accompanied by example programs in C and full instructions.

As Alan Tong, Managing Director of Pico Technology, explained, "Linux is widely used in the embedded computing, medical and scientific fields because it is stable, open-source and easy to modify, and can run a wide variety of applications. Now these users can choose any scope from our 2000 and 3000 Series scopes to integrate into their own applications."

The driver is available from the Pico website at www.picotech.com. For more information, Pico can be contacted at Pico Technology, James House, Colmworth Business Park, Eaton Socon, St. Neots, Cambridgeshire PE19 8YP. Tel: +44 (0) 1480 396 395 Fax: +44 (0) 1480 39629.

MERG Journal

The Model Electronic Railway Group (MERG) have sent us their Summer 2008 journal. As usual it has news of the Group's activities along with useful constructional articles.

MERG hold meetings in London five times a year. The venue is the Model Railway Club, Calshot Street N1 9DA, very near King's Cross Station. The next meeting is on 13 September, when one of their members will give a detailed illustrated talk on a relatively simple and cost effective bus for controlling model railways. Non-members are welcome.

For more information, contact MERG, Spread Eagles, Melbury Abbas, Dorset SP7 0DU, or browse www.merg.info.

PHONE THEFT PROTECTION

Modern phones store as much personal data as a PC, but are much more easily lost or stolen. Password protection does not help if the phone was 'open' when taken. IT and Internet security company Kaspersky has developed a low-cost application which sits on a phone and protects it against unauthorised use.

Kaspersky Mobile Security 7.0 costs £14 and works on smartphones running Windows Mobile 5.0 or 6.0 and Symbian Ver 9 operating systems. While the phone is with its rightful owner, the software routinely scans incoming files and accessed web sites, checking for viruses. If the phone goes missing the owner can send it a text which either temporarily blocks its use or permanently erases all data stored inside the phone.

If the thief tries to use the phone with a different SIM card, the phone sends a text message to a pre-arranged number, giving the number of the new SIM. So the rightful owner can send a text message to disable it.

Barry Fox

Electronworks Kits

Electronworks comment that they've taken some of life's insanity (and lots of their own) and put it into their electronic kits. The aim is to make learning electronics fun and to bring you a range of kits that are both practical and educational.

They have a whole ton of kits and ideas that they will be unleashing on you in the coming months, so if you are young or old, new to electronics or a seasoned veteran, you will find something to suit your needs. For example, they have an MP3 booster that amplifies the output of your MP3 player, so you can fill the room with music via your PC speakers. They have an electronic coffee mat that lights up a sequence of LEDs when you place a mug on it. They also have an in-car power supply, so you can power all your battery powered electronics from a 12V input and there's a simple desk thermometer that gives you the temperature of a room at the touch of a button.

Visit www.electronworks.co.uk and see their advert on page 65 to find out more.



Super Speedo Corrector

By **JOHN CLARKE** and **JULIAN EDGAR**

Get your electronic speedometer reading accurately

THESE DAYS, having an accurate car speedometer is vital if you're to avoid fines and collecting licence points. But how do you correct the speedometer if it is reading high or low? It's easy with the Super Speedo Corrector, which will work with any electronic speedometer – digital or analogue. It allows you to alter the reading in 1% increments, either up or down.

Before you can use the Speedo Corrector, you'll have to find and identify the speedometer sensor output wire or the speed signal output wire from the ECU. In some cars that's easier said than done, so make sure you have a car wiring diagram and that you can physically access the speedometer input wire, which is normally at the back of the instrument cluster. If you can't find

the right wire, you won't be able to install the Speedo Corrector.

This project includes an automatic set-up procedure, whereby the Super Speedo Corrector calibrates itself to suit the speed signal output characteristics; an on-board status LED flashes to show correct operation; and an AC output signal that will work with Nissan speedometers.

Circuit description

The circuit (Fig.1) is based on micro-controller IC1, which is programmed to alter an incoming frequency by a set amount. The exact amount is set using two BCD rotary switches (S1, S2), which alter the frequency in 1% steps.

The speedometer signal is applied to the input of the circuit that has the options of a 1k Ω pull-up resistor

Speedo Corrector: main uses

- Correct inaccurate speedometers in standard cars
- Correct inaccurate speedometer caused by changed differential or gearbox ratios.
- Correct inaccurate speedometer caused by changed tyre diameters.
- Correct tachometers




Fig.1: all the clever stuff in this circuit is done by PIC microcontroller IC1. It takes the speedometer signal and multiplies it by a factor set by two rotary BCD switches (S1 and S2). The speedometer signal frequency can be either increased or decreased in 1% increments – see text.

selected with transistor Q4 or a 1k Ω pull-down resistor selected with transistor Q2. By selecting either link LK1 or LK2, the pull-up resistor can be connected to either the +8.2V supply or the +5V supply.

The input signal is then fed via a 10k Ω resistor to Zener diode ZD2, which ensures that levels cannot go above +16V or below -0.6V. A parallel 10nF capacitor filters the signal, which then drives transistor Q1 via a voltage divider consisting of 10k Ω and 6.8k Ω resistors.

The 6.8k Ω resistor, at the base of Q1, can be either connected to ground via the RA4 output of IC1, or left floating when the RA4 output is set as a high-impedance input. When the resistor is connected to ground, the signal level required to switch Q1 is about 2.5V. Alternatively, when this

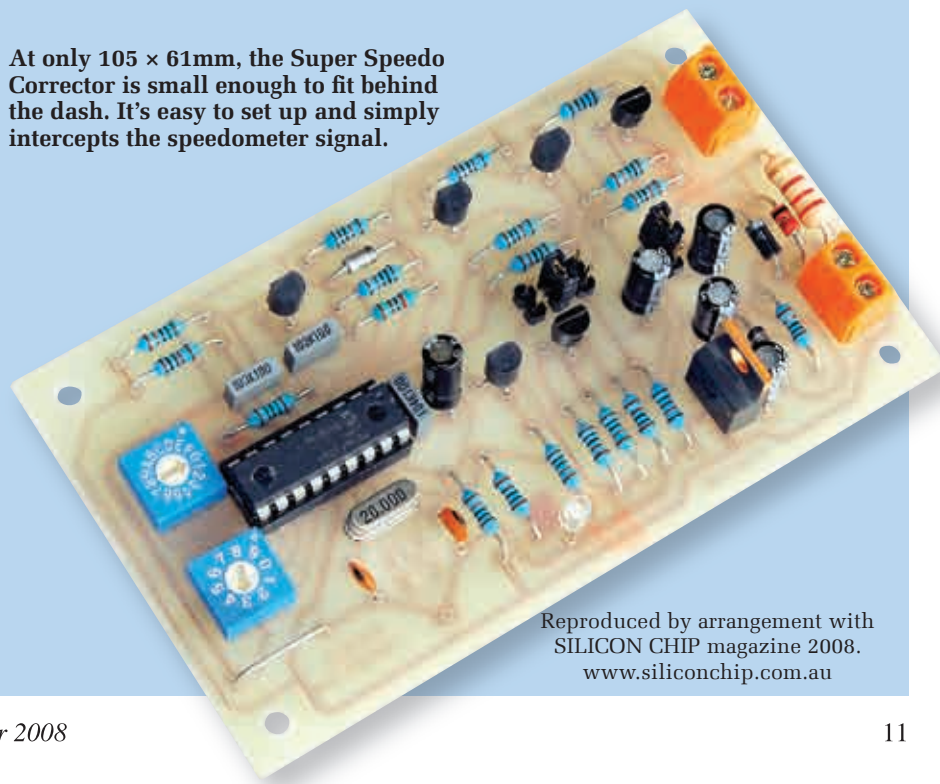At only 105 x 61mm, the Super Speedo Corrector is small enough to fit behind the dash. It's easy to set up and simply intercepts the speedometer signal.



Reproduced by arrangement with
SILICON CHIP magazine 2008.
www.siliconchip.com.au

Features and Specification

Main features

- Allows alteration of speedometer reading so it reads faster or slower
- Automatic or manual set-up of input signal detection
- Caters for three output signal types
- LED indication of valid speed sensor signal being received
- LED indication of output operation

Specification

- Output rate – adjustable in 1% steps from 0 to 99%
- Output – either faster or slower than the input rate
- Input and output types – pull-up or pull-down resistance, or AC
- Output swing – 0 to 8.2V or 0 to 5V or 8.2V peak-to-peak AC or 5V peak-to-peak AC
- Minimum operating frequency – adjustable from 1Hz to 16Hz
- Maximum input frequency to maintain 1% change resolution: 1.2kHz
- Maximum input voltage: 50V RMS
- Minimum input sensitivity: 0.7V peak (on high sensitivity setting)
- Minimum input sensitivity: 2.5V peak (on low sensitivity setting)
- Power: 9V to 15V at 25mA

Mechanical speedo?

The Super Speedo Corrector will work only on electronic speedometers – ie, those that don't have a mechanical rotating cable driving them. If you have an older car with a mechanical speedometer, then you won't be able to correct it – at least not using this circuit.

the pull-up, pull-down and AC outputs, respectively.

An internal power-on reset for IC1 is provided using the MCLR input (pin 4) which is connected to the 5V supply via a 1k Ω resistor. This keeps the IC reset until the power supply voltage is correct.

IC1 operates at 20MHz using crystal X1. This frequency was chosen so that the software program runs sufficiently fast to operate with speedometer signals up to 1.2kHz. Note that the Super Speedo Corrector will operate with speedometer signals above these frequencies, however the accuracy of speedometer correction will be reduced.

Power supply

Power for the circuit is applied via diode D1, which provides reverse polarity protection. Zener diode ZD1 and the 10 Ω resistor provide transient protection to protect the input of REG1. The 100 μ F capacitor at REG1's input provides a further degree of transient voltage suppression. A 10 μ F filter capacitor is provided directly at REG1's output and the 100 μ F and 100nF capacitors decouple the supply to IC1.

An 8.2V supply is derived from the supply at REG1's input via a 220 Ω resistor and Zener diode ZD3. This supply is for the pull-up resistors if required.

Software

The software files are available for free download via the *EPE* Downloads site, access via www.epemag.co.uk. Pre-programmed PICs are available from **Magenta Electronics** – see their advert in this issue for contact details.

Construction

The Super Speedo Corrector circuit fits onto a small PC board measuring 106 × 60mm. This board is available

resistor is effectively out of circuit, the sensitivity is lowered to around 0.7V peak.

The RA2 output of IC1 is used to select the pull-up resistor. When RA2's output is at 5V, it switches on transistor Q3 and this in turn switches on transistor Q4. Q4 then connects the 1k Ω pull-up resistor from the input to Q4's collector, which then connects the pull-up resistor to the +8.2V or +5V supply rail. If RA2 is at 0V, transistors Q3 and Q4 are off and there is no pull-up resistor in circuit.

The RA3 output selects the pull-down resistor when its output is at 5V. This output drives transistor Q2 to connect the 1k Ω resistor at its collector to ground. When RA3 is at 0V, the pull-down resistor is out of circuit.

Transistor Q1's collector inverts the signal and drives pin 6 (RB0) of IC1 via a 10k Ω pull-up resistor and a 150 Ω series resistor. A 1nF capacitor filters out any high-frequency voltage variations. Pin 6 includes an internal Schmitt trigger to ensure a clean signal for measurement.

The rotary BCD switches (S1 and S2) are monitored via the RB1 to RB7 inputs and the RA1 input. The RB inputs are normally held high via internal pull-up resistors within IC1, while the RA1 input uses a 10k Ω resistor to ensure that its input is held high, unless pulled low via switch S2.

The switches provide a unique BCD (binary coded decimal) value on these inputs for each setting.

Output signal

The output signal is at RA0 (pin 17). This drives the indicating LED (LED1) via a 1k Ω resistor and the base of transistor Q5. Q5's collector is held high via a 1k Ω resistor, which connects to either the +8.2V or +5V supply (via link LK1 or LK2).

Transistor Q5's collector provides the pull-up output signal and also drives Q6, which has a pull-down resistor at its collector to provide the pull-down output. Coupling the pull-down output via a 100 μ F capacitor provides an AC output. The 10k Ω resistor provides the discharge path, while links LK3, LK4 and LK5 select

Tacho as well?

The Super Speedo Corrector will also work with electronic tachos that take their feed from the ECU (ie, all cars with engine management).

The configuration procedure is the same as for use of the device as a speed interceptor, except that the 'speed sensor' becomes the 'tacho output signal' from the ECU. This application is particularly suited to engine and gearbox swaps.

24V operation

The Super Speedo Corrector can be used on 24V vehicles if the following changes are made: change ZD1 to 33V 1W; change the 220Ω 0.5W resistor that feeds ZD3 to 1kΩ 1W; change the 100μF 16V capacitor at the input to REG1 to 100μF 35V.

Non-linearity?

The Super Speedo Corrector will not compensate for non-linear errors. In other words, if the speed reads 10% high at 25km/h and 4% high at 100km/h, you won't be able to use the Super Speedo Corrector to get the speedometer accurate at all speeds. However, most speedometer errors are proportional and so can be dialled out with the Speedo Corrector.


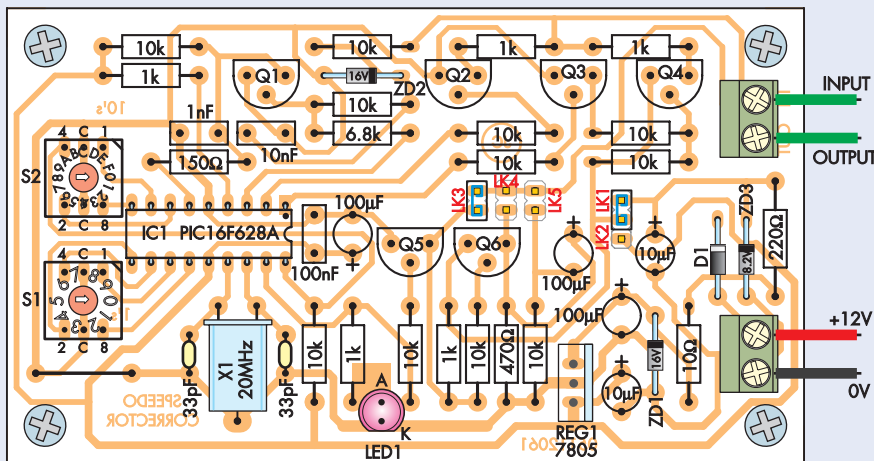


Fig.2: when assembling the PC board, take care with the orientation of the BCD switches, the PIC and the other polarised components. Use this diagram and the photos of the completed project (below) to help you in your assembly.

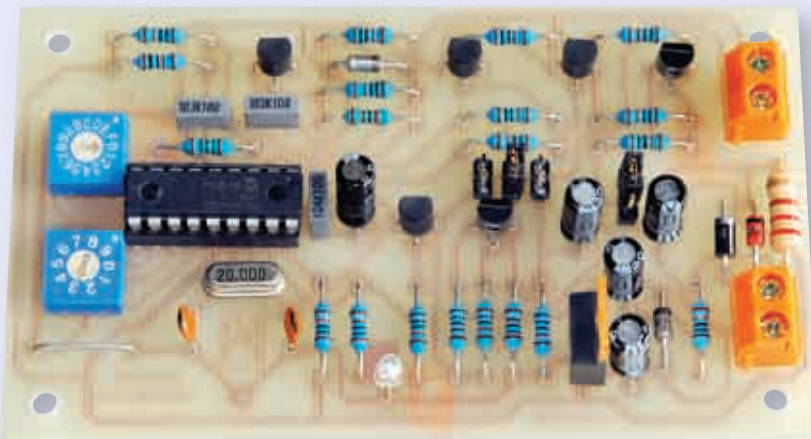

Corrections are easy to dial-up – just set the two rotary switches to give the up or down percentage correction that's needed. Here, the Super Speedo Corrector is configured to reduce the speedometer reading by 3%.

from the *EPE PCB Service*, code 682. The board topside component layout is shown in Fig.2.

Construction is straightforward, but be sure to correctly install the polarised components, such as the PIC microcontroller, electrolytic capacitors and the diodes. Note that transistors Q4 and Q6 are not the same type as Q1, Q2, Q3 and Q5, even though they look the same.

The BCD switches must be mounted with their dots positioned as shown on the overlay diagram (Fig.2). The BCD switch with 0-9 capabilities is S1 and the BCD switch with 0-F on it is S2.

Making adjustments

The speed reading can be altered in 1% increments. This is most easily explained if you use a test speed of

100km/h. If the speedometer is wrong by 5km/h at 100km/h, the adjustment needed is about 5%.

Switch S1 (the one nearest the bottom, when the PC board is orientated with the connections at the right) corrects the speedometer reading in single units and S2 changes the output in tens. So when you want a correction of 5%, simply set S1 to '5' and S2 to '0'. If the required correction is 16%, set S1 to '6' and S2 to '1'.


Using the two BCD switches in combination allows the speedometer reading to be altered by as much as 99%, in increments of just 1%.

The default output reduces the reading of the speedometer. This default was picked because most speedometers read fast (often by about 5%). Alternatively, if you wish

to increase the speedometer reading, set S2 to its F position and wait for a two-flash acknowledgement from the LED. This needs to be done with the unit connected and powered up.

You will need an accurate reference to set the speedometer. This can be provided by a handheld GPS, another car with a known accurate speedometer or even, if you ask nicely, a police car. *Just make sure that you have an assistant to do the adjusting as you drive!*

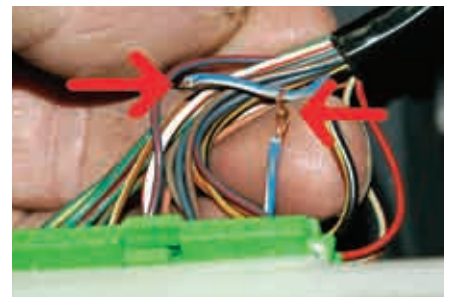You can also use the 'speedo check' distances that are marked on some roads – although strictly speaking, this is intended for checking the accuracy of the odometer rather than the speedometer.



Once located, the speed sensor wire must be cut. The wire that goes to the speed sensor connects to the Super Speedo Corrector's 'IN' terminal and the wire going to the speedometer connects to the 'OUT' terminal.

corrector will mostly work out for itself what configuration is required. These are the steps to follow:

- 1) Connect power (use an ignition-switched source), ground, speedometer 'in' and speedometer 'out' (to the Speedo). Position the corrector so that a passenger can observe the on-board LED.
- 2) Set S1 to 2.
- 3) Set S2 to A.
- 4) Install link LK2.
- 5) Drive the car for a minute (the Speedo will not work).
- 6) Observe that the LED flashes at 1Hz when the car is moving. This shows that the Speedo Corrector has set itself for the type of speedometer signal that is present and is receiving a valid signal from it.
- If the LED doesn't flash, install link LK1 (instead of LK2) and try again.
- 7) Set S2 to 0
- 8) Set S1 to 0

Finding the speed input wire to the speedometer can involve a dash disassembly job. In this Honda, the steering column had to be dropped, the dash fascia removed and the speedometer cluster unbolted and pulled forward. Make sure you're aware of the safety precautions that need to be taken if the car is equipped with airbags.

Installation

Now for the installation – but first, a word of warning: if you need to pull the dash out to locate the speed input wire to the speedometer, make sure you're aware of the safety precautions that need to

be taken if the car is equipped with airbags.

Of course, you must also check that you are not invalidating any manufacturers warranties that may still be running.

In the vast majority of cars, little setting-up will be needed – the

Table 1: Functions of S2 settings

Switch setting	Function	IC1 pin status
A	Autoset (automatically finds a suitable input setting)	Pins 1, 2 and 3 change. Pin 17 goes from 0V to 5V to 0V at a one-second rate to flash LED when automatic sensing is complete
B	Pull-up resistor (low sensitivity @ 2.5V peak)	Pin 1 @ 5V, Pin 2 @ 0V, Pin 3 @ 0V
C	AC input (high sensitivity @ 0.7V peak)	Pin 1 @ 0V, Pin 2 @ 0V, Pin 3 open circuit
D	Pull-down resistor (low sensitivity @ 2.5V peak)	Pin 1 @ 0V, Pin 2 @ 5V, Pin 3 @ 0V
E (initial setting)	No pull-up resistor or pull-down resistor (low sensitivity @ 2.5V peak)	Pin 1 @ 0V, Pin 2 @ 0V, Pin 3 @ 0V
F (default is slow)	Fast or slow option (LED acknowledgement: 1 flash = slow, 2 flashes = fast)	
Note 1: in most applications, only the 'A' (automatic) setting will need to be used during set-up. Note 2: switch setting must be selected for a minimum of four seconds to initiate new function.		

Digital speedometer lag

If the Speedo Corrector is fitted to a car with a digital speedometer, some lag may occur in the action of the speedometer. Typically, this is noticeable when abruptly coming to a stop from a slow speed (eg, 10km/h), where the speedometer may keep displaying a number greater than zero for up to a second, even when the car is stationary.

Lag may also make itself evident when moving away from a standstill, where the speedometer initially shows 0km/h before then jumping to 15km/h or 16km/h.

This problem can be overcome by the use of the special 'digital speedometer function' built into the Corrector. This function is enabled during set-up by setting switch S1 to a position other than 2 before selecting A on S2. Positions 1 to 9 on S1 vary the number of pulses for which the Speedo Corrector calculates the output frequency of the speedometer sensor (odd switch numbers calculate over one pulse and even numbers calculate over two pulses) and the time delay before the corrector stops sending a signal to the speedometer after the input signal ceases.

The delays are: positions 0,1 (1 sec); positions 2,3 (500ms); positions 4,5 (250ms); positions 6,7 (125ms); positions 8 and 9 (62.5ms).

If the speedometer reading noticeably lags behind actual vehicle speed, try different positions of S1 before each time setting S2 to A and proceeding with the self set-up process described in the main text. The optimal setting is that which gives the shortest lag while still reliably operating the speedometer.

9) Try the link options LK3, LK4 or LK5 until Speedo works (the speedometer should read as it did with the car standard).

10) Set S1 and S2 to give the required correction (S1 is for single units, S2 for tens).

11) If the speedometer reading needs to be corrected upwards rather than the default downwards, set S2 to F and then wait for the LED to flash twice. Then set S2 back to its required correction value. To return to downwards speed correction, again set S2 back to 'F' and wait for a single flash acknowledgement.

If the required settings are already known (eg, in the case of auto electricians fitting large numbers of the design to just one type of car), Table 1 shows how S2 can be used to manually set the input configuration, while Table

2 shows the output configurations achievable by the different link positions. Any changes to the switches will not be registered by the circuit until after about four seconds, so make sure you don't switch off power during this time! This delay

allows you to rotate the switches to the required position without any unwanted changes occurring.

Conclusion

Once the Corrector is working properly, it can be mounted in a UB3-type plastic box and tucked up behind the dash out of sight. But don't assume that your speedometer is always going to be dead accurate – accuracy depends on tyre diameter, which changes with wear and when new tyres are fitted.

Of course, with the Super Speedo Corrector, it's easy enough to then make the required speedometer calibration change!

EPE

Parts List

- 1 PC board, code 682, available from the *EPE PCB Service*, size 105 × 61mm
- 1 UB3-type plastic box, size 130 × 68 × 44mm
- 2 2-way PC-mount screw terminal blocks
- 1 18-pin DIL socket
- 3 2-way 2.5mm jumper headers
- 1 3-way 2.5mm jumper header
- 2 jumper shunts
- 1 0-9 BCD rotary switch (S1)
- 1 0-F BCD rotary switch (S2)

Semiconductors

- 1 PIC16F628A-I/P microcontroller, programmed with speedcor.hex (IC1)
- 4 BC337 NPN transistors (Q1,Q2,Q3,Q5)
- 2 BC327 PNP transistors (Q4,Q6)
- 1 7805 +5V voltage regulator (REG1)
- 1 1N4004 1A diode (D1)
- 2 16V 1W Zener diodes (ZD1,ZD2)
- 1 8.2V 1W Zener diode (ZD3)
- 1 3mm high-intensity red LED (LED1)
- 1 20MHz crystal (X1)

Capacitors

- 3 100µF 16V PC electrolytic
- 2 10µF 16V PC electrolytic
- 1 100nF MKT polyester
- 1 10nF MKT polyester
- 1 1nF MKT polyester
- 2 33pF ceramic

Resistors (0.25W 1%)

- 11 10kΩ
- 1 220Ω 0.5W
- 1 6.8kΩ
- 1 150Ω
- 5 1kΩ
- 1 10Ω
- 1 470Ω

Table 2: Link functions

Link	Function
LK1	8.2V max. output
LK2	5V max. output
LK3	Pull-up output
LK4	Pull-down output
LK5	AC output



Laser

Why tolerate when you can automate?



X10 Home Automation



KAT5 AV transmission and IR control system



Barix Ethernet based MP3, communications and control systems



C-Bus Shop
C-Bus and C-Bus Wireless

www.laser.com

www.cbushop.com

Laser Business Systems Ltd
Tel: +44 (0) 20 8441 9788
Fax: +44 (0) 20 8449 0430
Email: info@laser.com
16 Garthland Drive, EN5 3BB

Integrators, Installers, Trade and Retail customers welcome

How do you put the colour into the cheeks of people appearing in black and white films and photos? State-of-the-art techniques exist for colourising old images, and even recovering colour information once considered lost, as Mark Nelson explains.

Fifty years ago, the Hollywood movie mogul Samuel Goldwyn was not convinced of the claims made for colour television. Famously, he declared, "I won't believe it until I see it in black and white." Whether the irony was intended is not recorded. Personally, I find black and white images much more relaxing, but I know I'm in a minority on that score.

Heresy in the 21st century

In fact, many viewers find black and white television and films a total turn-off, which is why there is so little monochrome material in today's television schedules, despite the obvious merit of much archive programming.

The major studios have tackled this aversion to monochrome by colourising some classic films that were made in black and white, and quite recently the same heresy has been carried out for television on footage of the First World War. Personally, I found the results rather unconvincing but your mileage may vary.

A different situation applies where the dyes in old colour film have faded and here computer processing can often restore the richness of the original hues. Eastmancolor is one of the most vulnerable of colour film processes and prints can fade in as little as five years if you are unlucky. Technicolor, on the other hand, is considered the most fade-resistant colour process.

A colour challenge of an entirely different kind is one that the BBC is addressing right now, namely recovering the colour information locked invisibly in black and white film recordings of 'lost' colour programmes. In the early days of colour television in Britain (we're talking about the late 1960s) videotape was simply too expensive to use as an archiving medium. At that time, each reel of tape cost about the same as a small car.

Selected programmes – particularly those that had an export potential – were, however, recorded on black and white film, effectively by pointing a cine camera at a television screen. The film stock used for these 'telerecordings' was monochrome, because it was cheaper and few Commonwealth countries (the prime export market for BBC Enterprises) transmitted in colour anyway.

Good news

As it happens, the BBC has a large number of black and white telerecordings of colour programmes for which no tape exists. Even better, some 98 per cent of

these programmes were recorded without the colour chroma filtered off. Now why is this technical trivia such good news?

In fact, trivial it is not. Back in the 1960s, the then-new PAL colour television process was designed to be compatible with the large number of black and white sets already in use at that time. It achieved this objective by concealing the colour information within a 4.43MHz subcarrier signal superimposed on the monochrome picture signal.

This additional colour signal was outside the display capability of most TV receivers, but can be detected as a slight fuzziness on a very good quality monochrome monitor screen. For an optimum black and white telerecording the BBC engineers should have filtered out electronically this interference signal (known as chroma information) but often this extra task was overlooked.

Applied electronics

What this means is that the colour in these 40 year-old programmes may not be lost after all. Using the latest technology, BBC research staff have been experimenting with a process to scan film recordings at high-definition (HD) standard and then pick out the PAL chroma signal. The process looks very promising, making a large number of programmes from 1968 to 1974 capable of being brought back to full colour.

Candidates for recovery include science fiction such as *The Year of the Sex Olympics* and *Doctor Who*, the *Morecambe and Wise Show* and music programmes like *Top of The Pops* and *The Old Grey Whistle Test*, all of which will become far more palatable with the colour restored. How soon we shall see these on our screens at home is still to be determined, but BBC Worldwide (the new name for BBC Enterprises) has a clear commercial interest in releasing archive content.

It's important to stress that the process used here is not a colourisation process as such; it does not apply new colour to old programmes, but instead recreates the original colour from the film. Decoding the colour from a forty year old monochrome film print is a far greater technical triumph than anything carried out previously. The BBC did some work of this kind in the early 1990s, but the results were quite feeble in comparison.

Clever guys

The person leading this ground-breaking research is James Insell, founder of the Colour Recovery Working Group (<http://colour-recovery.wikispaces.com/>).

Although James works for BBC Research, this website is entirely independent and is a discussion area for people producing software and systems that can be used by any broadcaster to recover colour information from archive film.

He says that the notion of recovering chroma captured in monochrome film came to him first in 1994 when viewing a film recording of the *Doctor Who* series called *Ambassadors of Death*? Six years later he put forward a theory for recolourising recordings to Steve Roberts of the BBC's *Doctor Who* restoration team. It took several years to secure funding and support for a research project, but now James has the supreme satisfaction of seeing his theory proved with amazing results.

Also involved in the project is Richard Russell, whose name you may recognise as the creator of the BBC BASIC for Windows computer language, and the author of the Z80 and MS-DOS versions of BBC BASIC. He designed several electronic colour test cards for the BBC, as well as versions for hobbyists. Richard's own website is at www.rtrussell.co.uk/.




Want to try this at home?

Unfortunately, as much as you might like to, you cannot try this at home! But you can at least read about the techniques on the websites mentioned. On the other hand, you can try your hand at computer colourisation, adding colour to old photos, picture postcards and suchlike. This work can be extremely absorbing, with remarkably impressive results that get even better as you build up your skills. The program to use is called *Recolored* and you can download a free 21-day trial version from their website at www.recolored.com/.

A palette of colours allows you to pick the most realistic tints for flesh tones, grass, sky and all other objects in the photograph. Unlike many graphics programs, there is no need to struggle with layers or complicated settings. Everything is accomplished with a few brush strokes, with the software performing the otherwise difficult and time consuming task of colouring the image and creating smooth transitions between different coloured objects.

The Gallery section of the website shows some stunning examples of work with this program, and it's important to stress that the results look like colour photos rather than tints applied crudely on top of a black and white image. The software is not expensive (around £15) and the only shortcoming is the lack of a health warning saying how addictive this program can be!

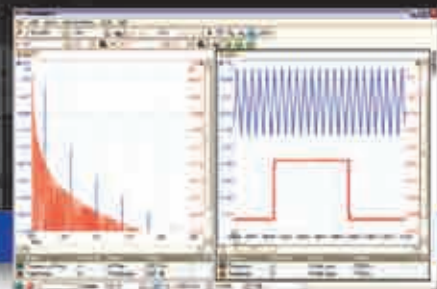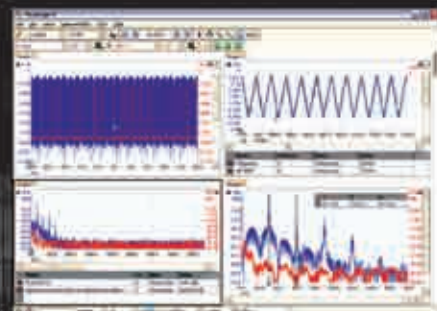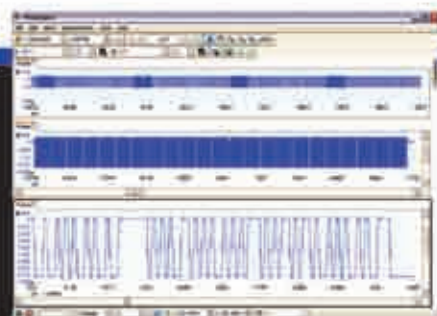USB Connected High Speed PC Oscilloscopes



250 MHz bandwidth
1 GS/s real-time sample rate
128 megasample record length

PicoScope 5000 Series The No Compromise PC Oscilloscopes

With class-leading bandwidth, sampling rate, memory depth and an array of advanced high-end features, the PicoScope 5000 PC Oscilloscopes give you the features and performance you need without any compromise.

Advanced Triggers

In addition to the standard triggers the PicoScope 5000 series comes as standard with pulse width, window, dropout, delay, and logic level triggering.

250 MHz Spectrum Analyser High-speed USB 2.0 Connection

Automatic Measurements

Arbitrary Waveform Generator

Define your own waveforms or select from 8 predefined signals with the 12 bit, 125 MS/s arbitrary waveform generator.

Waveform Playback Tool

PicoScope software now allows you to go back, review, and analyse up to 1000 captures within its waveform playback tool.

5000 SERIES

3000 SERIES

2000 SERIES

The PicoScope 3000 Series of oscilloscopes from Pico Technology includes general purpose and high resolution models: With 12 bit resolution and 1% accuracy, the 10MHz PicoScope 3424 is able to detect changes as small as 0.024% (244ppm) – making it the ideal 4-channel oscilloscope for analog design and analysis. The higher speed 8 bit models in the PicoScope 3000 series feature sampling rates up to 200MS/s and up to 1 MS/s record lengths for general purpose and portable applications.



The PicoScope 2000 series oscilloscopes offer single and dual channel units that offer highly portable/low cost solutions to general purpose testing. The award winning 25MHz handheld PicoScope 2105 fits comfortably into the palm of your hand yet still includes the powerful features found in larger oscilloscopes.



pico
Technology

www.picotech.com/scope484

to check out our full line of PC-based instruments or call **01480 396 395** for information and a product catalogue

Ever wanted to be able to listen to the 'unlistenable' – sounds that are way beyond the range of normal human hearing? Like the supersonic whine of a gas leak, or the echo-location 'chirps' of bats? Here's a low-cost project that will let you do just that. It's a down-converter, which shifts ultrasonic sound signals down into the frequency range where they can be heard (or recorded).

by
Jim Rowe

ULTRASONIC EAVESDROPPER

A FEW WEEKS AGO, I found myself watching a wildlife documentary on TV in which naturalists were studying the behaviour of bats. They were using infrared lighting to photograph them and a down-converter so that they could hear and record the ultrasonic 'chirps' that the bats use for navigation in the dark – and often for tracking down their insect prey/food.

My curiosity was aroused and I decided to 'have a go' at coming up with a low-cost down-converter of my own. This project is the end result, presented so that readers can also indulge their curiosity.

I won't claim that the project has all kinds of uses, because it's mainly going to be useful for listening to the ultrasonic sounds emitted by bats and one or two other nocturnal insect-eating creatures.

But you should also be able to use it to track down the exact location of high-pressure gas leaks – which apparently also produce an ultrasonic whistle or whine. You could even use it to make sure an ultrasonic dog whistle is working. If Fido seems to be ignoring it perhaps his hearing has deteriorated like mine!

How it works

Most of the sounds emitted by bats are in the frequency range from about 15kHz to 50kHz, with a few extending


up to about 150kHz and a small number extending down below 10kHz. So most of them are above the range of human hearing, and some well above. (Young people can often hear up to about 18-20kHz, but this upper limit generally falls as we grow older.)

The idea of the eavesdropper is to shift the ultrasonic sounds down in frequency, so they fall within our comfortable hearing range.

This is done by using the heterodyne principle, in much the same way as it's used in many radio receivers. Or more accurately, in exactly the same way as it's used in 'direct conversion' receivers: we mix the incoming ultrasonic signals with a continuous ultrasonic signal from a 'local oscillator'.

In the mixer, the two signals heterodyne or 'beat' together, generating signals which correspond to the sum and difference of the two frequencies. The 'sum' signal will be very high in the ultrasonic range – and thus even more inaudible – but the 'difference' signal is easily arranged to be much lower in frequency and therefore in the audible (to humans!) range.

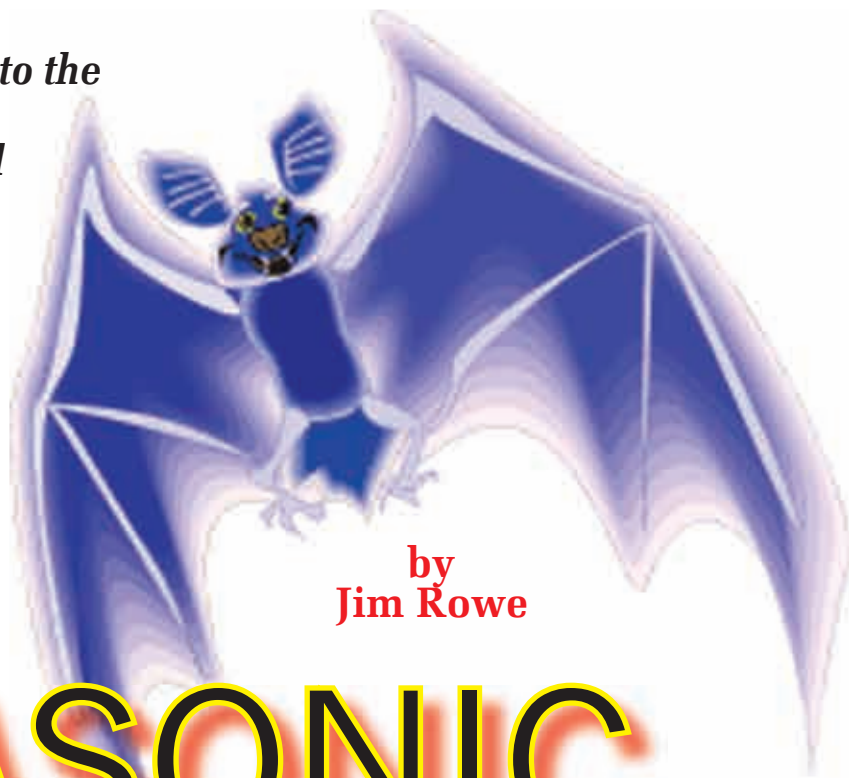You can see how this down-conversion system works from the block diagram in Fig.1. The ultrasonic sounds are picked up by a small electret microphone, which turns them into small ultrasonic electrical signals. This type of microphone has a frequency





response which extends well up into the ultrasonic region.

The signals are then passed through a preamplifier to boost them to a more useful amplitude (or level), where they can be passed into one input of a balanced mixer. The other input to the mixer is fed with a continuous ultrasonic signal produced by a tuneable 'local oscillator', so it can be varied in frequency from about 15kHz to 50kHz.


As a result, the output of the balanced mixer contains three main frequency components: the difference signals ($F_{IN} - F_{OSC}$) and ($F_{OSC} - F_{IN}$), and the sum signal ($F_{IN} + F_{OSC}$). The sum signal is obviously even higher in the ultrasonic range than F_{IN} and F_{OSC} , so it's of no interest to us. We filter it out, anyway. But by adjusting the tuning of the local oscillator the difference signals can be placed down in the audible range, so all we have to do is feed them through an audio amplifier (via a volume control),

so that they can be either heard through a pair of headphones or sent to a tape or other recorder (even recorded on a computer hard disk or memory card for later analysis).

What's with the dish?

Used by itself, the electret microphone insert works – but not very well. To make it more effective, we concentrate the ultrasonic sound waves with a small, 'somewhat' parabolic dish.

As you may recall from previous projects, a parabolic dish reflects all the waves which strike it to its focal point. With the microphone insert mounted

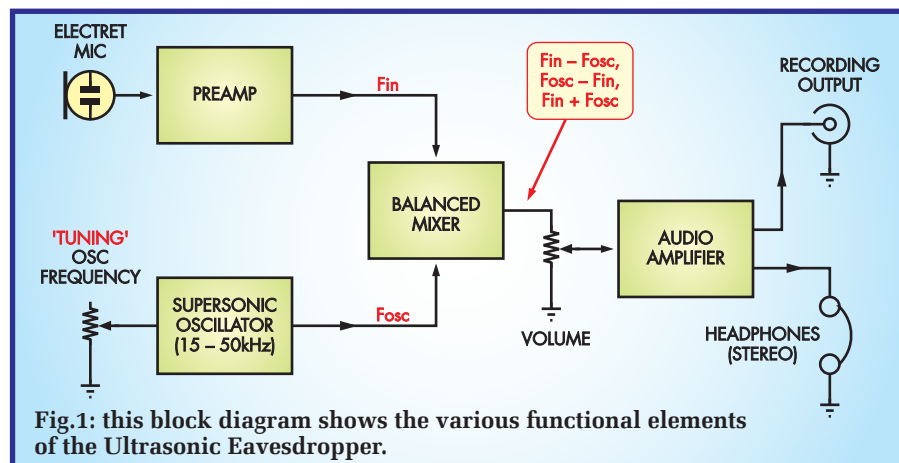

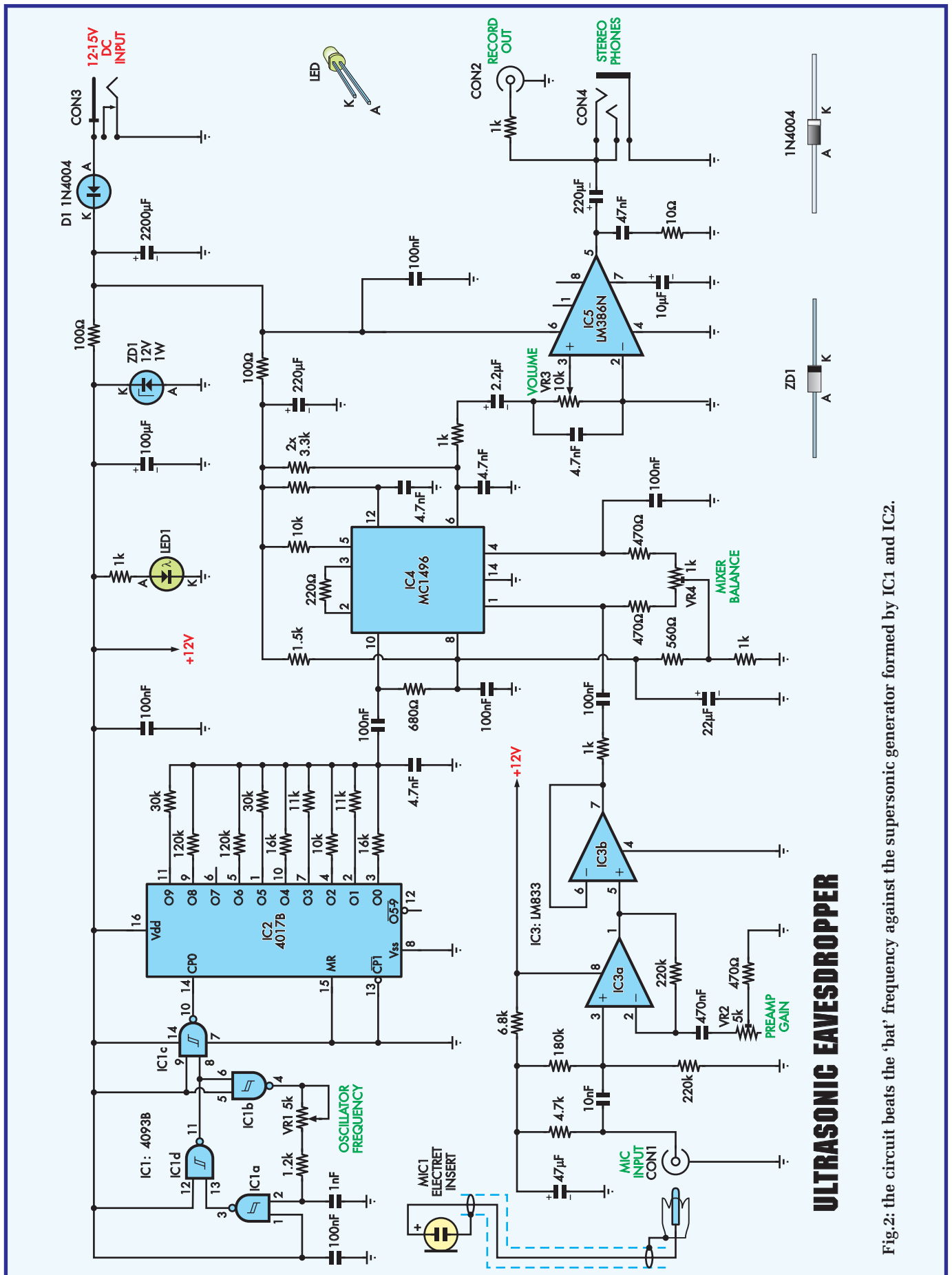


Fig.2: the circuit beats the 'bat' frequency against the supersonic generator formed by IC1 and IC2.

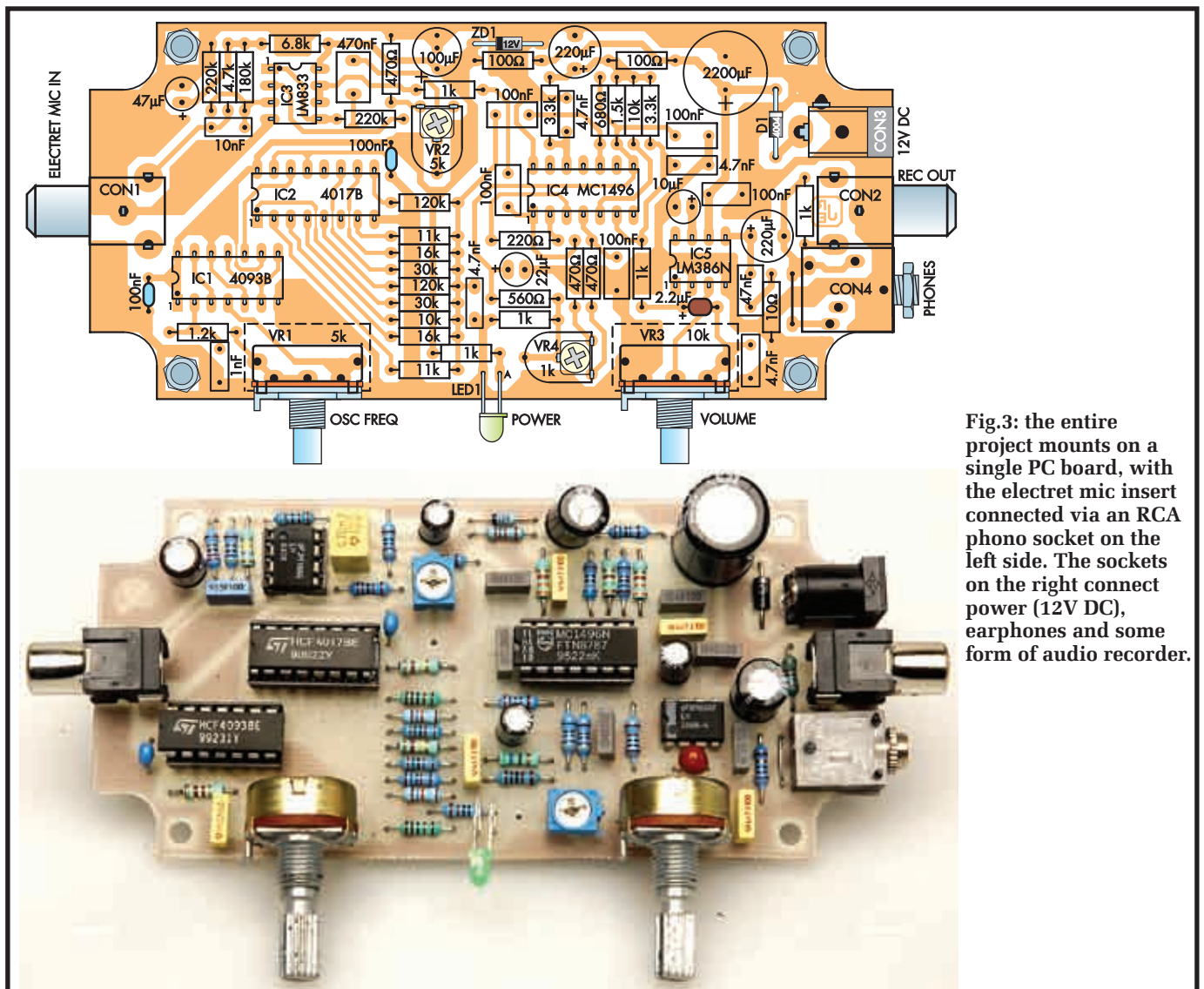


Fig.3: the entire project mounts on a single PC board, with the electret mic insert connected via an RCA phono socket on the left side. The sockets on the right connect power (12V DC), earphones and some form of audio recorder.

at the focal point (or as close as we can guess!), pick-up becomes much more efficient and effective.

This dish can be made from just about any material which will reflect sound waves – we used a laminated wood cereal or salad bowl, bought from a ‘bargain store’ for just a couple of pounds. It is about 155mm in diameter and about 39mm deep, but this is not at all critical – a larger dish should be even better, but would start to become unwieldy.

A similar (hard) plastic or even stainless steel salad bowl could also be used.

We said a moment ago that it was ‘somewhat’ parabolic in shape – it has a flat bottom. This might not be technically ideal but it is good enough for our purposes – and certainly makes it a lot simpler to attach things to!

You can work out the focal point of a parabola by formula (but it is complicated by the flat bottom), or you could line the bowl with aluminium foil and aim the bowl at the sun to enable you to get it spot on.

Another way of finding the focal point would be to connect the mic insert to an audio amplifier and aim the dish at a single point sound source (such as a speaker connected to an oscillator). Moving the microphone back and forward

along the centre axis would reveal one point where the maximum signal was found.

Having said all that, we found near enough (an educated guess) was good enough – but feel free to experiment with distances! We’ll look at mounting the dish and microphone a little later.

The circuit


Now let’s look at the circuit diagram (Fig.2) for a more detailed understanding of how it works. The ultrasonic sounds are picked up by the electret microphone insert, MIC1.

The fairly small signals from MIC1 are fed in via CON1 and first amplified by IC3a, half of an LM833 dual low-noise op amp. It’s used here as a preamp with its gain variable between about 40 and 400, using trimpot VR2.

This allows the project to be set up for either short or long range bat monitoring, and with bats having either loud or soft ‘chirping’ (they do vary between species).

After amplification, the signals are passed through IC3b, the ‘other half’ of the LM833, connected as a unity-gain buffer to provide a low impedance source feeding the mixer IC4, via a 1kΩ series resistor.

Constructional Project

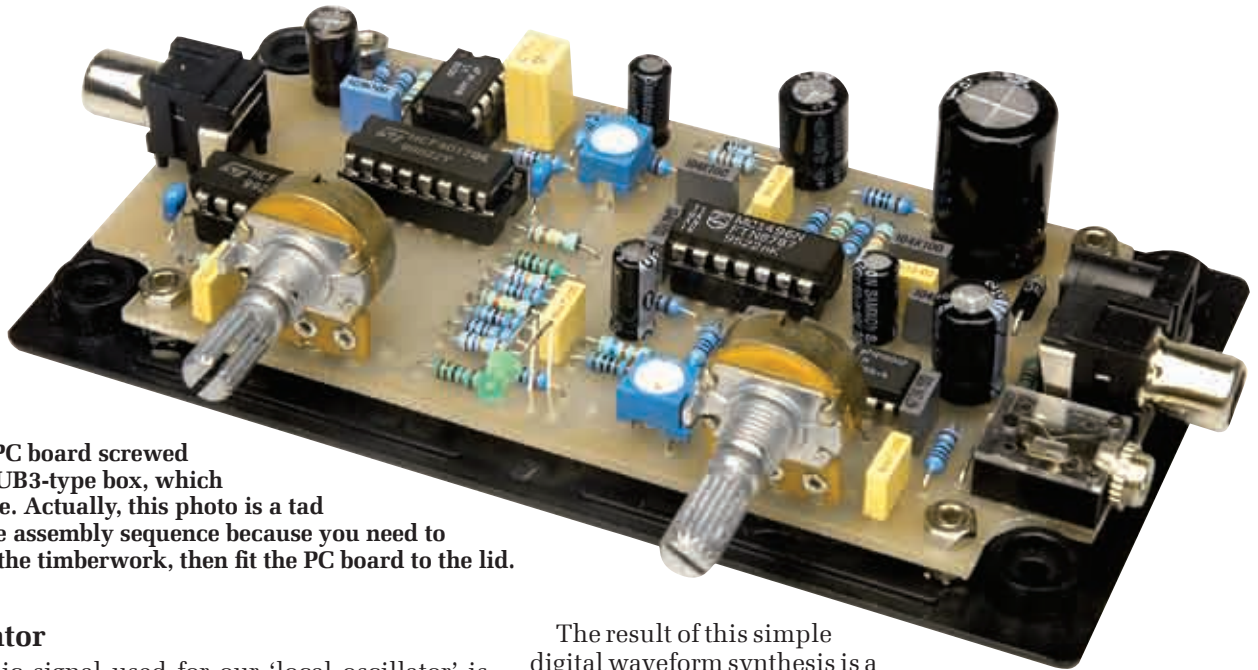

The completed PC board screwed to the lid of the UB3-type box, which becomes the base. Actually, this photo is a tad premature in the assembly sequence because you need to screw the lid to the timberwork, then fit the PC board to the lid.

Local oscillator

The ultrasonic signal used for our 'local oscillator' is generated using IC1 and IC2. This signal (a) needs to be tuneable over a fairly wide frequency range; (b) should be reasonably low in harmonic content and (c) should also be fairly constant in amplitude. However, this combination of qualities is not easy to produce using conventional audio oscillator circuits.

So we generate it in a slightly unusual fashion. Gates IC1a, IC1b and IC1d are used as a relaxation-type oscillator, producing a square wave clock signal which is variable between 150kHz and 500kHz using potentiometer VR1. This clock signal is buffered by gate IC1c and fed into the clock input of IC2, a 4017B Johnson-type decade counter.

This IC therefore counts the clock signals so that its 10 outputs, O0 to O9, switch high in turn, on a continuous cyclic basis. These outputs are used to drive a simple digital-to-analogue converter (DAC) using a set of resistors. While it may appear that output O7 is not used, it is – its 'infinite value' resistor (ie, open circuit) actually sets the zero point.

The values of the resistors are carefully chosen so that as the outputs of IC2 go high in turn, a 10-sample approximation of a sinewave is developed across the output (ie, the 680Ω resistor between pins 10 and 8 of IC4). The 4.7nF capacitor which is also across the output provides a measure of low-pass filtering and further 'smoothing' of the sinewave.

The result of this simple digital waveform synthesis is a fairly smooth sinewave signal of reasonably constant amplitude, with a frequency exactly one tenth that of the clock signal from IC1. So as the clock signal is varied between 150 and 500kHz via VR1, the 'local oscillator' sinewave signal at the pin 10 input of IC4 is varied between 15kHz and 50kHz.

Balanced mixer

IC4 is an MC1496 double-balanced mixer, expressly designed for this kind of use. When we feed our amplified ultrasonic sound input signal into pin 1 and our local oscillator signal into pin 10, it performs an analogue multiplication between them and provides the corresponding sum and difference frequency signals at its outputs (pins 6 and 12, which are simply dual polarity outputs).

By the way, the mixer strictly only produces just the sum and difference signals at its outputs when it is carefully balanced using trimpot VR4. If it is not truly balanced, both of the input signals can also be present in the outputs – although this is not a major problem here because both of these input signals are inaudible.

All the same, it's a good idea to have the mixer reasonably close to balance, to reduce distortion



Here you can see how the plastic case needs to be drilled and slotted...



...so that the PC board is an easy fit. Again, the lid is screwed to the handle before the board is placed inside the box.

in the audio amplifier. We'll explain how to do this later.

As you can see, in this project we take the mixer output signal from pin 6 of IC4 and then pass it through a simple low-pass filter using the 1k Ω series resistor and 4.7nF capacitor (across volume control VR3). This filtering attenuates the 'sum' frequency components quite significantly, leaving mainly just the audible 'difference' components that represent the downshifted version of our ultrasonic sound signals. We then pass these through audio amplifier IC5, after adjusting their volume level via potentiometer VR3.

The amplified output of IC5 is used to drive a standard pair of stereo headphones via CON4 and/or an audio recorder via line-level output CON2.

The complete circuit is designed to operate from almost any source of 12V to 15V DC, which is fed in via CON3 and can come from either a small AC plugpack supply or a nominal 12V battery, such as that in a car or motorcycle.


The total current drain is less than 35mA, so you could also run it from a pair of 6V lantern batteries connected in series, or even a pack of eight C-cells. Zener diode ZD1 limits the voltage which can be fed to ICs 1 to 3, while LED1 indicates that power is applied.

Construction

All of the Eavesdropper circuitry is mounted on a single PC board, measuring only 122 x 57mm. This board is available from the *EPE PCB Service*, code 683. The component layout is shown in Fig.3. As you can see, the board has rounded cutouts at each corner so that it can be mounted snugly inside a standard plastic box measuring 130 x 68 x 44mm.

Microphone input socket CON1 is mounted on the left-hand end of the board, while the DC input, headphone output and recording output connectors are all mounted on the right-hand end. The local oscillator 'tuning' pot VR1, power LED1 and volume control pot VR3 are all mounted along the front side for easy access.

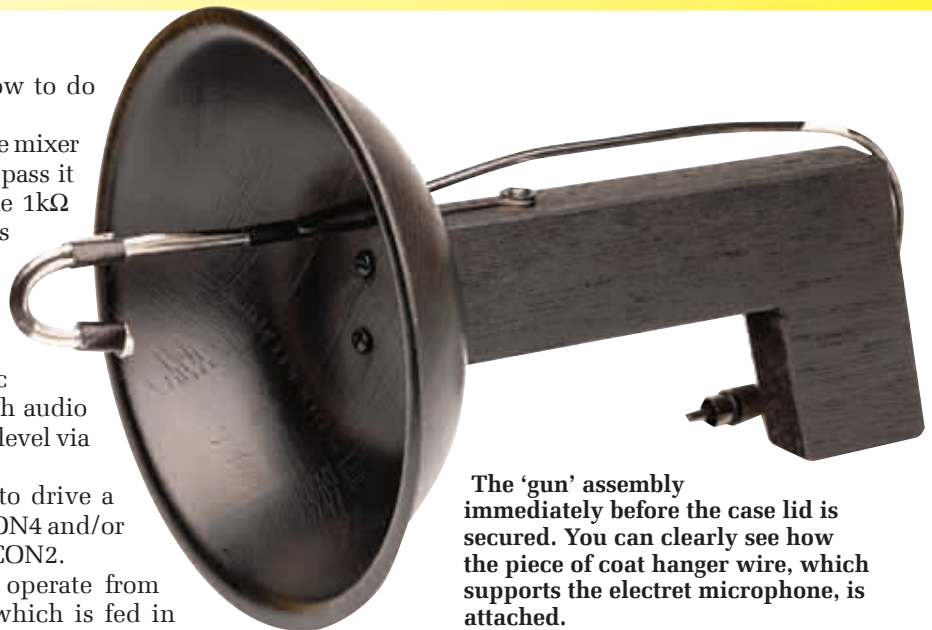Begin construction by checking the PC board for any etching problems or undrilled holes and fixing these before



The 'gun' assembly immediately before the case lid is secured. You can clearly see how the piece of coat hanger wire, which supports the electret microphone, is attached.

you proceed. Then it's a good idea to fit the various connectors (CON1 to CON4), as these sometimes require a small amount of fiddling and board hole enlargement.

There is only one wire link to be fitted to the board, so it's suggested you fit this next to make sure it isn't forgotten. It's located just behind CON4 at lower right, as viewed in the PC board overlay diagram.

Next, fit the various fixed resistors, taking care to fit each one in its correct position. These can be followed by trimpots VR2 and VR4, making sure you don't swap them around. The 5k Ω trimpot is VR2, while the 1k Ω trimpot is VR4. Don't fit the two large rotary pots at this stage – they're best fitted later.

Now you can fit the capacitors, starting with the two 100nF multilayer monolithics (near IC1 and IC2) and then progressing through the small MKT caps, the 2.2 μ F tag tantalum electrolytic (just to the front of IC5) and then the other electrolytics. Remember that all the electrolytics are polarised, so make sure you orient them correctly (as shown in Fig.3, the PC board overlay diagram).

After these you can fit the semiconductors, starting with diode D1 and Zener diode ZD1 – again, make sure you don't

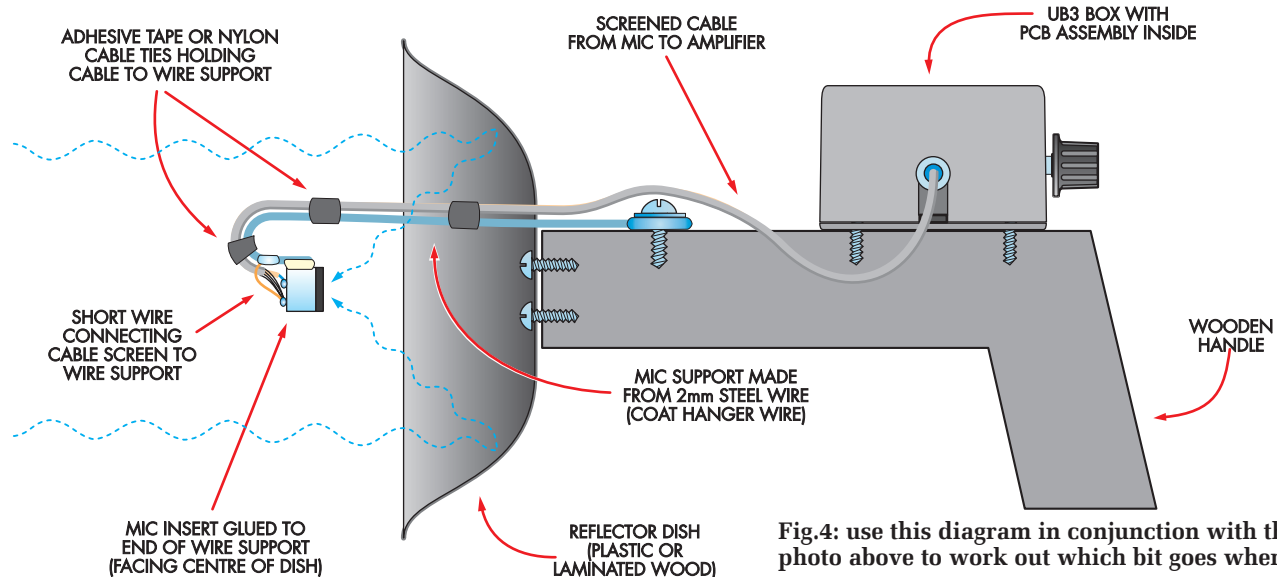


Fig.4: use this diagram in conjunction with the photo above to work out which bit goes where!


Constructional Project

swap these accidentally and that they are both fitted with the correct orientation, as shown in the overlay diagram and photos. Then fit the ICs, preferably in reverse numbered order (ie, IC5 first, then IC4, working your way back to IC2 and IC1). Although there is no need to fit any of the ICs in sockets, we suggest that you do. All five ICs must be oriented as shown.

If you are soldering IC2 and IC1 directly into the board, take extra care to protect them from the possibility of electrostatic damage. Use an earthed soldering iron, earth yourself if possible (or at least discharge yourself before handling the ICs) and solder the supply pins of the ICs first (pins 7 and 14 on IC1, pins 8 and 16 on IC2) to enable their internal protection circuitry as early as possible.

After the ICs are in position, it's time to fit power LED1. This is fitted to the board vertically to begin with, with its longer anode (A) lead to the right and both leads soldered to their pads underneath with the LED's body about 18mm above the board. Then, using a pair of needle-nose pliers or similar, bend both leads forward by 90°, 12mm above the board. This will position the LED facing forward and ready to protrude through the matching hole in the box, after final assembly.

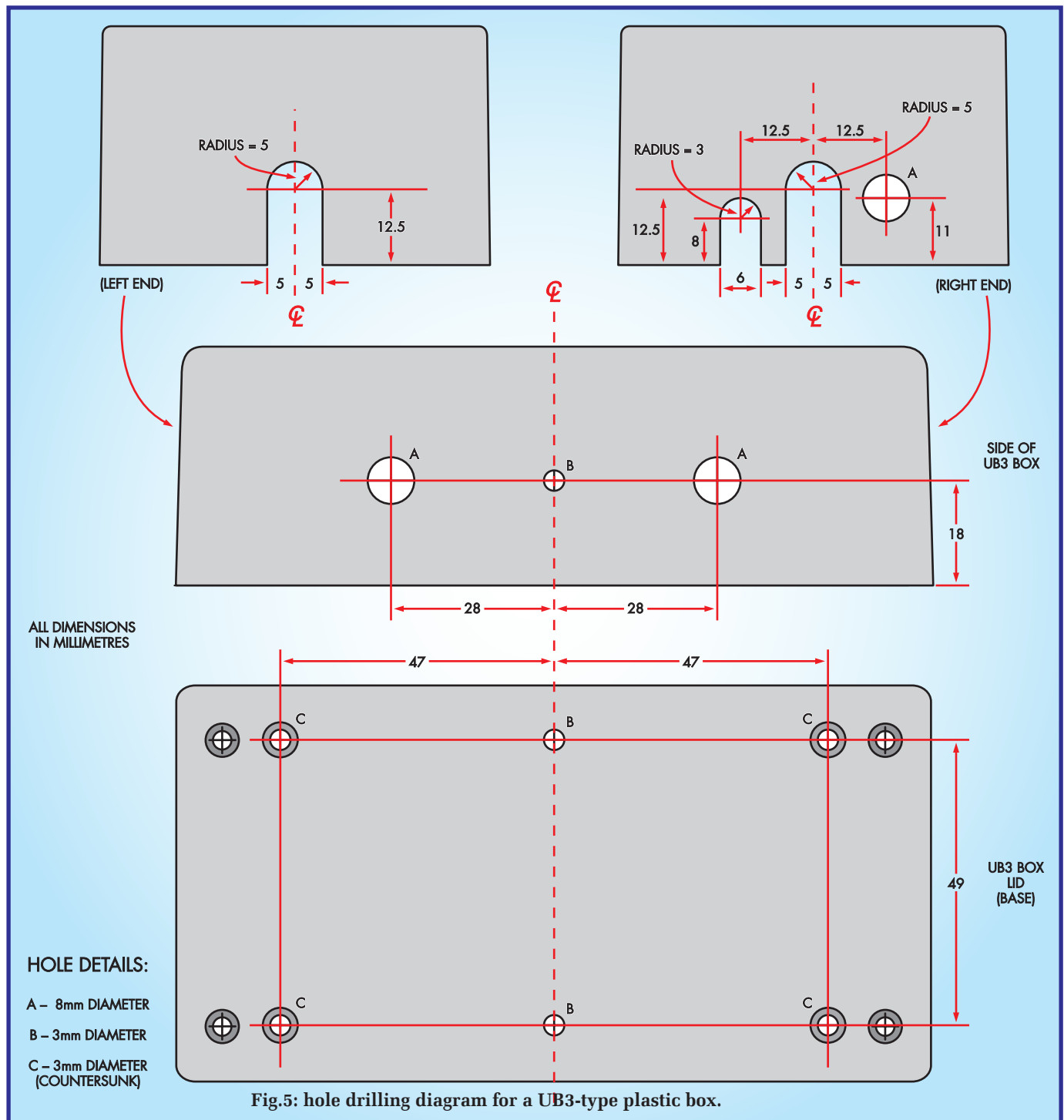The last two components to mount on the board are control pots VR1 and VR3, which are both fitted along the front of the board on either side of LED1. You may need to cut the pot spindles to about 10-12mm long before they're



fitted, if they're not already this length. Make sure you fit the 5k Ω linear pot as VR1, and the 10k Ω log pot as VR3, as shown in the overlay diagram.

Your Eavesdropper board should now be complete and ready to be fitted to the lid of the UB3-type plastic box, which is used here as the base. But before doing this, you may need to prepare both the lid and the box itself, by drilling and cutting the various holes that are needed for mounting, assembly and access to the various connectors and controls. The location and dimensions of all of these holes are shown in the drilling diagram (Fig.5), so you shouldn't have any problems if you use this as a guide.

The hardware

It would also be a good idea at this stage to make the Eavesdropper's wooden 'handle' and attach it to the front small reflector dish we mentioned earlier.

The dish is simply attached to the front of the wooden handle using a couple of 15mm-long self-tapping screws, passing through 3mm holes drilled in the centre of the 'bowl'. Two further 3mm holes were drilled just above these mounting holes to allow the mic support 'bracket' and its shielded lead to pass through – see Fig.4.

The mic support bracket was bent up from a 200mm length of 2.2mm diameter steel wire, salvaged from a coat-hanger. After straightening and cutting to length, the wire was bent into a small loop at one end (around the shank of a 4mm twist drill). Then the straight section of wire was passed through the matching hole in the back of the dish, and the loop end attached to the top of the wooden handle, about 45mm behind the bowl, using a 15mm-long wood-screw, with a small flat washer under the screw head.

The front end of the bracket was then bent around and downwards in an open J-shape, about 20mm in diameter, so the end was aligned very closely with the centre axis of the bowl and about 65mm in front of the bowl's inside centre – corresponding to an approximation of this bowl's likely 'focus' as an ultrasonic reflector.

Then the mini electret mic insert was cemented to the side of the wire's end using epoxy cement, with its 'front' facing inwards towards the centre of the bowl (ie, it looks backwards, not forwards).

After the epoxy cement has cured, solder the wires at one end of a 300mm length of light duty, screened microphone cable to the mic insert connection pads, with the cable screen wires connected to the insert's earthy/case pad and the inner wire to the other '+' pad. This is a slightly tricky job, as the pads are very small and closely spaced. So take your time, and in particular take care not to overheat the mic insert.

If you're new to soldering, it might surprise you to find that a hot, well-tinned iron poses much less danger than a cooler iron. The solder job is completed much more quickly – before the insert has had a chance to realise it's getting hot!

It's also a good idea to connect the cable screen to the wire support bracket just near the mic using a short length of fine tinned copper wire, to minimise hum pickup. The free end of the mic cable is then passed back through the remaining hole in the centre of the bowl and fitted with a metal-shelled RCA phono plug at the other end, ready to plug into the Eavesdropper. To prevent the cable from flapping around, it can be fastened to the mic supporting

Parts List – Ultrasonic Eavesdropper

- 1 PC board, code 683, available from the *EPE PCB Service*, size 122 × 57mm
- 1 plastic UB3-type box, size 130 × 68 × 44mm
- 2 RCA phono sockets, PC-mount (CON1, CON2)
- 1 2.5mm DC power socket, PC-mount (CON3)
- 1 3.5mm stereo jack socket, PC-mount (CON4)
- 1 Electret mic insert, miniature type (MIC1)
- 1 300mm length of screened mic cable
- 1 RCA phono plug, metal screened type
- 4 10mm long M3 machine screws, countersink head
- 4 M3 star lockwashers
- 8 M3 nuts
- 2 Small control knobs (for VR1 and VR3)

Semiconductors

- 1 4093B quad Schmitt NAND gate (IC1)
- 1 4017B decade counter (IC2)
- 1 LM833 dual low-noise op amp (IC3)
- 1 MC1496 double-balanced mixer (IC4)
- 1 LM386N audio amplifier (IC5)
- 1 12V 1W Zener diode (ZD1)
- 1 3mm green LED (LED1)
- 1 1N4004 1A diode (D1)

Capacitors

- 1 2200 μ F 16V RB electrolytic
- 2 220 μ F 16V RB electrolytic
- 1 100 μ F 16V RB electrolytic
- 1 47 μ F 16V RB electrolytic
- 1 22 μ F 16V RB electrolytic
- 1 10 μ F 16V RB electrolytic
- 1 2.2 μ F 35V TAG tantalum
- 1 470nF MKT metallised polyester
- 5 100nF MKT metallised polyester
- 2 100nF multilayer monolithic
- 1 47nF MKT metallised polyester
- 1 10nF MKT metallised polyester
- 4 4.7nF MKT metallised polyester
- 1 1nF MKT metallised polyester

Resistors (0.25W 1%)

- | | | | |
|---|-----------------|-----------------|-----------------|
| 2 220k Ω | 1 180k Ω | 2 120k Ω | 2 30k Ω |
| 2 16k Ω | 2 11k Ω | 2 10k Ω | 1 6.8k Ω |
| 1 4.7k Ω | 2 3.3k Ω | 1 1.5k Ω | 1 1.2k Ω |
| 5 1k Ω | 1 680 Ω | 1 560 Ω | 3 470 Ω |
| 1 220 Ω | 2 100 Ω | 1 10 Ω | |
| 1 5k Ω linear pot, 16mm or 24mm PC-mount (VR1) | | | |
| 1 5k Ω mini trimpot, horizontal PC-mount (VR2) | | | |
| 1 10k Ω log pot, 16mm or 24mm PC-mount (VR3) | | | |
| 1 1k Ω mini trimpot, horizontal PC-mount (VR4) | | | |

wire using three short lengths of 'gaffer' tape (visible in the photos) wrapped around them both.

At this stage, we gave the whole assembly a couple of coats of matt black spray paint. It looks 100% better than leaving it 'au naturel', which simply looks like a wooden salad bowl screwed to a piece of timber. If you do this, don't forget to completely cover the electret mic insert in adhesive tape to stop it getting painted. Masking tape is preferable because ordinary adhesive tape can be a real pest to remove.

Constructional Project

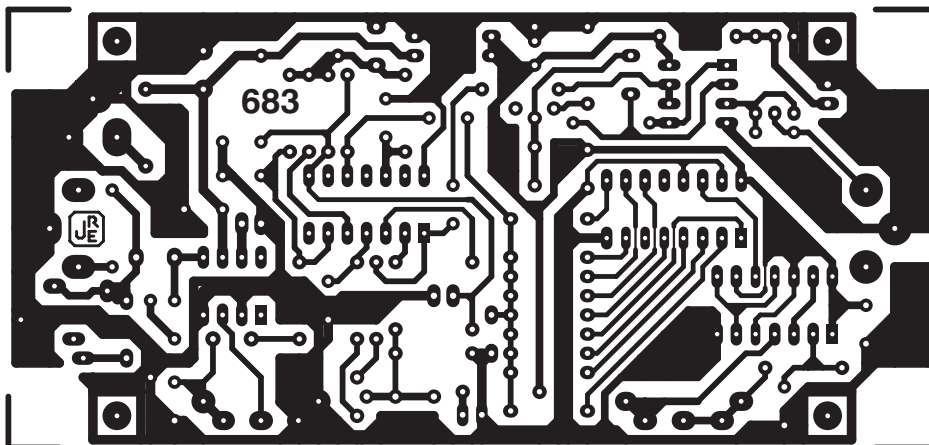


Fig.6 (above): the same-size PC board pattern, while below (Fig 7) is a same-size front panel artwork. We simply laminated and glued the paper label to the box, leaving a 2mm border around the edge.



Once the handle-dish-mic assembly is complete, you can attach the Eavesdropper's lid/base plate to the top rear of the wooden handle using a couple of 15mm-long woodscrews through the two 3mm holes in the centre. As you can see, the lid is orientated at right angles to the handle axis, and centred over it.

With the box lid attached to the handle, you can fit the Eavesdropper's finished PC board assembly on to the lid.

It's attached using four 10mm-long M3 machine screws with countersink heads, passed up from below, and each then fitted with a star lockwasher and M3 nut. These nuts act as spacers, so the screws and nuts should be firmly tightened before the board assembly is fitted. Then, when it is in position, four further nuts are used to hold it in place.

Checkout and adjustment

When the PC board assembly is fixed in place, it's time to fire up the Eavesdropper and give it a quick functional checkout.

Set both of the main control pots to roughly their midrange positions, and also set both trimpots to their midrange positions using a small screwdriver or alignment tool. Plug the mic cable into CON1, a pair of standard stereo

Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	2	220kΩ	red red yellow brown	red red black orange brown
□	1	180kΩ	brown grey yellow brown	brown grey black orange brown
□	2	120kΩ	brown red yellow brown	brown red black orange brown
□	2	30kΩ	orange black orange brown	orange black black red brown
□	2	16kΩ	brown blue orange brown	brown blue black red brown
□	2	11kΩ	brown brown orange brown	brown brown black red brown
□	2	10kΩ	brown black orange brown	brown black black red brown
□	1	6.8kΩ	blue grey red brown	blue grey black brown brown
□	1	4.7kΩ	yellow purple red brown	yellow purple black brown brown
□	1	3.3kΩ	orange orange red brown	orange orange black brown brown
□	1	1.5kΩ	brown green red brown	brown green black brown brown
□	1	1.2kΩ	brown red red brown	brown red black brown brown
□	5	1kΩ	brown black red brown	brown black black brown brown
□	1	680Ω	blue grey brown brown	blue grey black black brown
□	1	560Ω	green blue brown brown	green blue black black brown
□	3	470Ω	yellow purple brown brown	yellow purple black black brown
□	1	220Ω	red red brown brown	red red black black brown
□	2	100Ω	brown black brown brown	brown black black black brown
□	1	10Ω	brown black black gold	brown black black gold brown



Two views looking for'ard and aft. If you paint the whole shebang black, like we did, make sure you wrap a piece of masking tape around the microphone insert first. They don't like being covered in paint!



headphones into CON4 (but don't put them on yet, just in case something is wrong!) and the cable from your 12V battery or plugpack into CON3.

Power LED1 should immediately light up, to show that the circuit is operating. If the LED doesn't light, this will probably be because one of three components is fitted to the board with reversed polarity: LED1 itself, D1 or ZD1. Either that or the plug on your DC input cable is wired with reversed polarity.

With a multimeter, check the voltage between the anode of diode D1 and the board's ground – it should be the same

as the incoming DC. Similarly, the voltage at the cathode of D1 should be only 0.6V lower, while that at the cathode end of Zener diode ZD1 should be a little lower again.

You should also be able to measure the same voltage at pin 14 of IC1, pin 16 of IC2 and pin 8 of IC3. Likewise, at pin 6 of IC5 you should find the same voltage as you measured at the cathode of diode D1.

Listen to the headphones without actually putting them on. If they are not shrieking, place the headphones on your ears and you should hear a small amount of noise and/or hum. If you turn up volume control VR3, this noise should increase a little, showing that the audio section of the circuit is working correctly.

Now try returning VR3 to its mid-range position and adjusting 'tuning' control VR1 up or down. You may hear a faint heterodyne 'whistle' as you tune through one position in the tuning range. This is probably due to the mic preamp picking up a small amount of RF from a local AM radio

station, which then heterodynes with the Eavesdropper's local oscillator or one of its harmonics. This is not likely to interfere with the Eavesdropper's normal operation, but if nothing else it shows that the Eavesdropper's local oscillator, ultrasonic preamp and mixer sections are all working.

If all seems well at this stage, your Eavesdropper is probably working correctly and all that remains to be done before final box assembly is to set the mixer 'balance' trimpot VR4 to the correct position.

Got a 'scope?

Mixer balance adjustment is easiest with an oscilloscope, but if you don't have access to one, you don't really have to concern yourself about it; simply leave VR4 set to its midrange position, which is very likely to be 'near enough' for most purposes.


If you do have access to a scope and you want to set the mixer for the best possible performance, the adjustment is quite easy.

Capacitor Codes

Value	μF Code	EIA Code	IEC Code
470nF	0.47 μF	474	470n
100nF	0.1 μF	104	100n
47nF	.047 μF	473	47n
10nF	.01 μF	103	10n
4.7nF	.0047 μF	472	4n7
1nF	.001 μF	102	1n0

Constructional Project

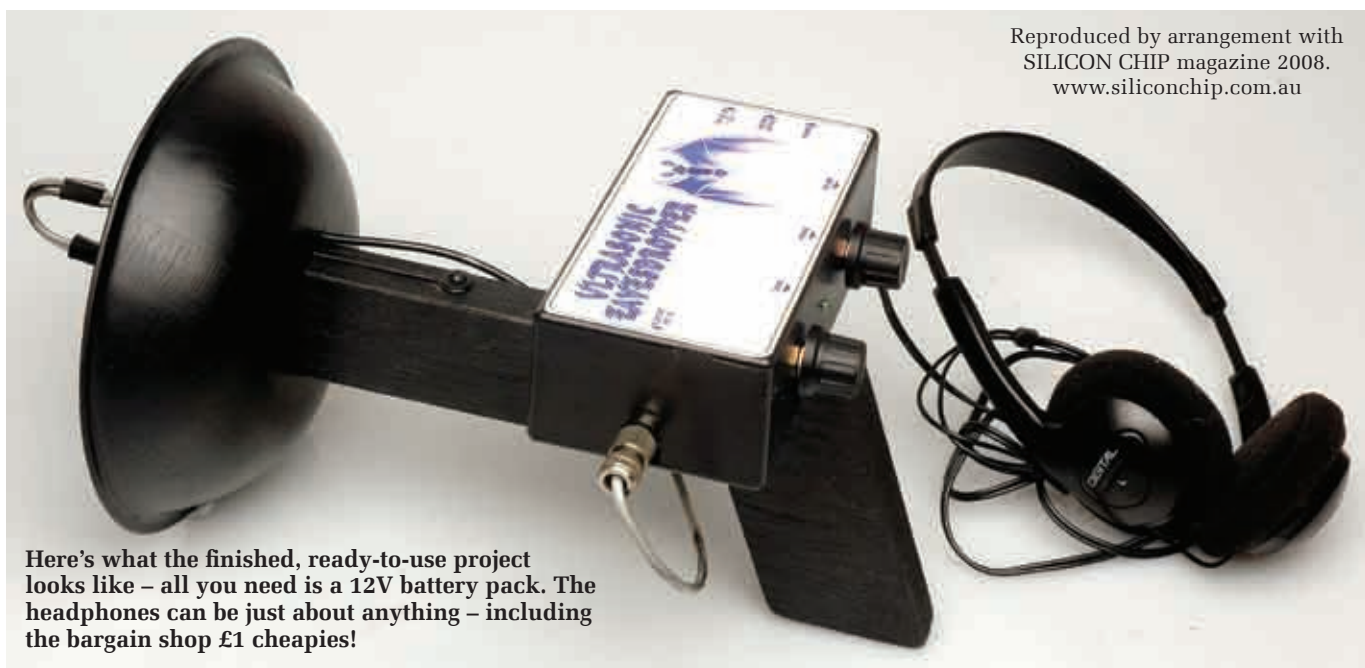Reproduced by arrangement with
SILICON CHIP magazine 2008.
www.siliconchip.com.au



Here's what the finished, ready-to-use project looks like – all you need is a 12V battery pack. The headphones can be just about anything – including the bargain shop £1 cheapies!

All you need to do is monitor the level of the Eavesdropper's 'local oscillator' signal appearing at pin 6 of IC4 with your 'scope, while adjusting VR4 with a small screwdriver, or plastic trimming tool. At either end of the trimpot's range the signal will increase in level, while it will pass through a minimum or 'null' somewhere near the middle of the range.

The correct setting for VR4 is right at the *centre* of this null – this corresponds to the mixer being balanced.

Final assembly

The final assembly step is to fit the box itself down over the PC board assembly, as a protective cover.

This is done by inverting the box and tilting it an angle of about 45° so that it can be offered up to the PC board with the control pot spindles and LED1 entering their matching holes on the box 'front side' from the inside.

Then the box is moved towards the mic and reflector bowl, gradually

tilting it down so that the undrilled long side swings down outside the 220 μ F electrolytic and the other components along the rear of the board.

The slots at each end of the box will allow the ends to clear the protruding sleeves of RCA phono connectors CON1 and CON2.

When the box has been juggled into position, it can be attached to the lid/base using the four small self-tapping screws supplied with it. Then the control pots can be fitted with their nuts, which can also be lightly tightened to help support the pots when the Eavesdropper is being used.

After this, you can fit the knobs, and your Eavesdropper should be ready for use.

Using it!


Operating the Ultrasonic Eavesdropper is very straightforward. You use 'tuning' pot VR1 to search for ultrasonic sounds over the Eavesdropper's range and then, when you find one, the same control is used to shift the sounds down to a convenient frequency for listening or recording. Volume control VR3 is used simply to adjust the output audio to a convenient level.

You'll probably find the Eavesdropper sensitive enough to pick up bat chirps with the preamp gain trimpot VR2 left in its suggested midrange position.

However, if you want to have the highest possible sensitivity, preset VR2 can be turned up to its fully clockwise position.

Happy bat tracking!

EPE

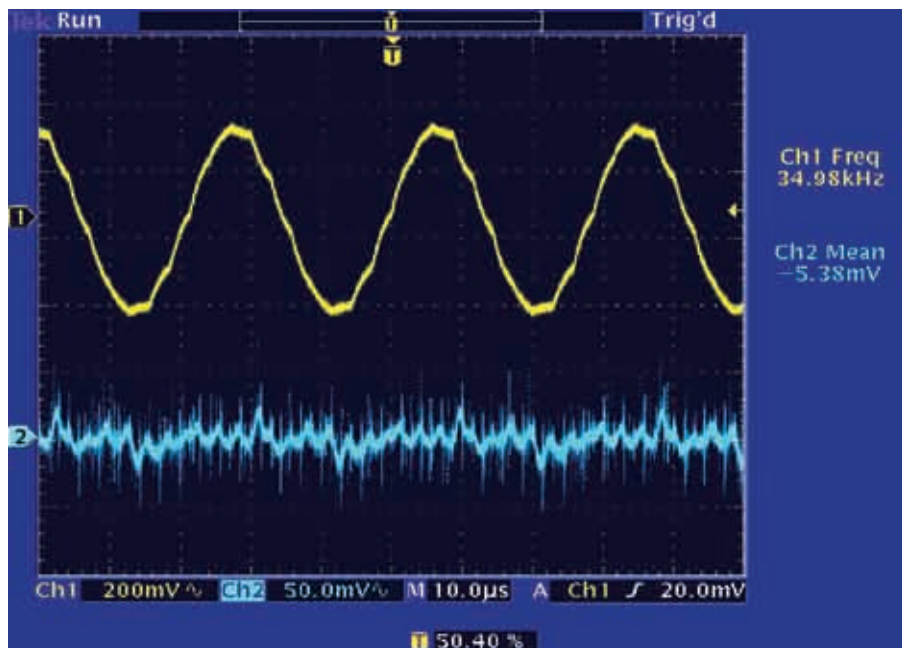

The top trace of this 'scope shot shows the synthesised sinewave coming from the ladder network of IC2. The lower (blue) trace shows the output at pin 6 of IC4. The very low mean voltage measurement of 5.38mV shows that the modulator is balanced.



Summer Offer! Free premium carry case!*

Padded carry case holds up to 2 units plus accessories

Atlas ESR - Model ESR60
ESR and Capacitance Meter
Measures capacitance, ESR (in-circuit too!).
Automatic controlled capacitor discharge!

Atlas DCA - Model DCA55
Semiconductor Analyser
Identifies type and pinout! Connect any way
round. Measures gain, junction
characteristics and more.

Atlas SCR - Model SCR100
Triac and Thyristor Analyser
Auto lead identification. Auto gate test
current from 100uA to 100mA.

Atlas LCR - Model LCR40
Automatic LCR Analyser
Automatic part identification, automatic
frequency selection and auto ranging!

*Free carry case for UK orders for 1 or more
instruments ordered before 31st Aug 2008.

Peak Electronic Design Ltd
West Road House, West Road,
Buxton, Derbyshire, SK17 6HF.
tel. 01298 70012 fax. 01298 70046

www.peakelec.co.uk sales@peakelec.co.uk

Atlas ESR

£85



New Low Price!

Atlas DCA

£55



Atlas SCR

£99



New Low Price!

Atlas LCR

£79



Please add £1.00 p&p per order. Prices include UK VAT. See website for overseas prices.

Electronics Engineers - Join A Winning Team! UK, Europe and Middle East

The Lektronix Group of Companies are the worlds leading provider of Industrial Automation repairs with an enviable reputation for the best in technical excellence and customer service.

Due to the huge demand for our services, and our future expansion plans, we need to employ additional engineers at all our workshops to keep pace with the additional work we are receiving.

We are looking for English speaking Electronic Repair Engineers, Electronic Repair Technicians and Electronic Component Level Repair Engineers in all the following locations:

- Walsall, UK
- Newry, Northern Ireland
- Brno, Czech Republic
- Bridgend, UK
- Katowice, Poland
- Dubai, UAE

Do you have an interest in electronics?
Have you any experience in the field of practical electronics?
Have you experience in Radio/Television/Home Electronics?
Does your hobby/interest include electronics?
Are you willing to learn new tricks – electronic engineering?
Do you want work in an exciting and challenging environment?
Do you have any experience with Machine Tool Systems - PLC's - Servo Drives
- Servo Motors - Monitors-VDU's - AC Drives - DC Drives - Temperature
Control - Digital Electronics – Analogue Electronics?

We offer a competitive salary and all the other benefits normal with a go ahead company.


Lektronix



Please Contact:
Mr Brian Stewart - Group Technical Director
Lektronix International Ltd, Unit C1, Lockside,
Anchor Brook Ind Park, Aldridge, West Midlands,
WS9 8EQ, United Kingdom.

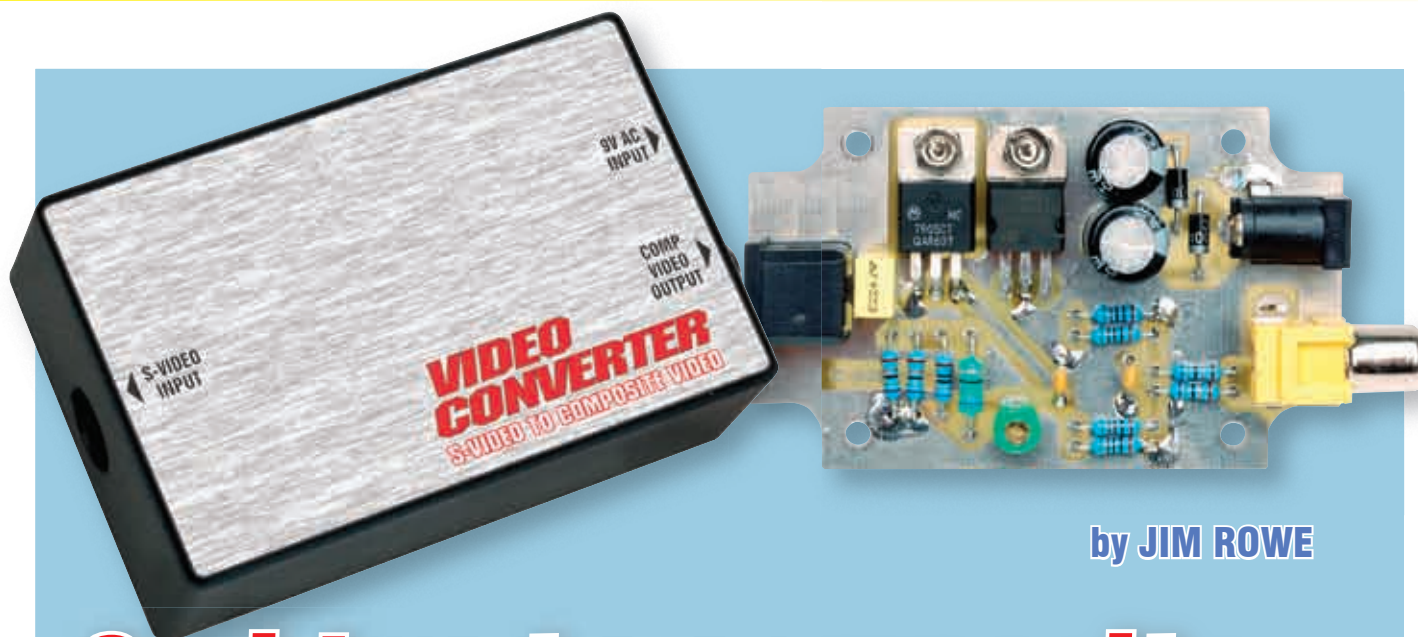For an application form please either:
Telephone +44 (0)1922 455555, or apply online
at www.lektronix.net/about/careers





by JIM ROWE

S-video to composite video converter

Some digital TV set-top boxes provide only S-video and component video outputs, which can pose a problem if your TV set only has a composite video input – or you've used up the S-video and component video inputs. The same can happen with video tuner cards for PCs. Here's an easy-to-build adaptor to get you out of trouble.

YOU CAN BUY CHEAP S-video to composite video adaptors in bargain stores, but the unit described here will do a much better job.

Although those really cheap bargain-store adaptors do work, if you examine the pictures critically, you'll find that their quality leaves quite a bit to be desired. In particular, you'll find that wherever the image has large areas of fine detail – like a shirt with a fine striped or check pattern, or an exterior panning shot


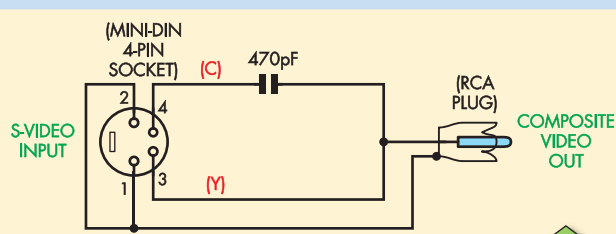


Fig.1: adding a low-value capacitor in series with the chrominance signal at the S-video input can reduce cross-colour interference, but also softens the picture.

Fig.2 (right): the unit described here uses an LC circuit to notch out a narrow band of frequencies centred on the 4.433MHz colour subcarrier frequency. This reduces cross-colour interference while leaving a sharp picture.

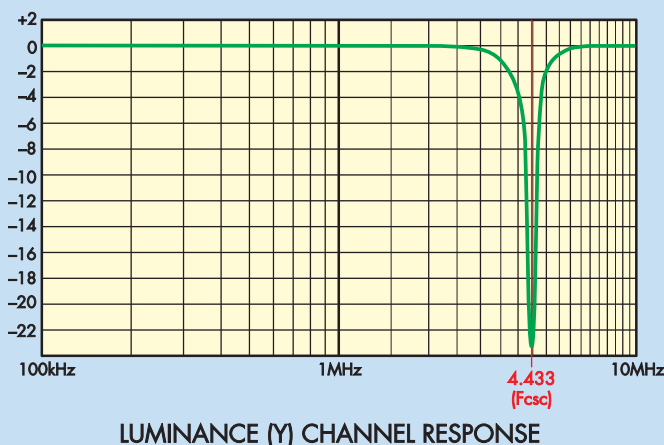



Low-cost 'bargain-store' adaptors commonly produce pictures that suffer from cross-colour interference, as shown in the photograph on the left. By contrast, the S-Video Converter dramatically reduces cross-colour interference – see photo on the right.

of a multi-storey building – then you'll see a very obvious coloured *Moiré* interference pattern, usually in shades of yellow and purple.


This effect is called 'cross-colour interference' and it's caused by heterodyne beats between the higher frequencies in the luminance (Y) signal and the chrominance (C) subcarrier in the receiver's decoder. In effect, the higher luminance frequencies tend to behave as if they were part of the chrominance signal, and as a result, produce fake colour patterns.

This happens when the two signals are simply mixed together in the video adaptor – which is what commonly happens in the bargain store units. This interference pattern can't happen when the Y and C signals are kept separate, which is why S-video produces much better image quality.

Reducing the interference

Some of the better low-cost adaptors try to reduce this cross-colour interference by adding a small capacitor in series with the chrominance input signal, as shown in Fig.1. The capacitor's value is chosen so that it passes most of the chrominance (C) information (it's in a band about 2.5MHz wide, centred on 4.43361875MHz), while at the same time attenuating the higher frequency luminance signals – ie, by shunting the luminance output into the chrominance output of the S-video signal source.

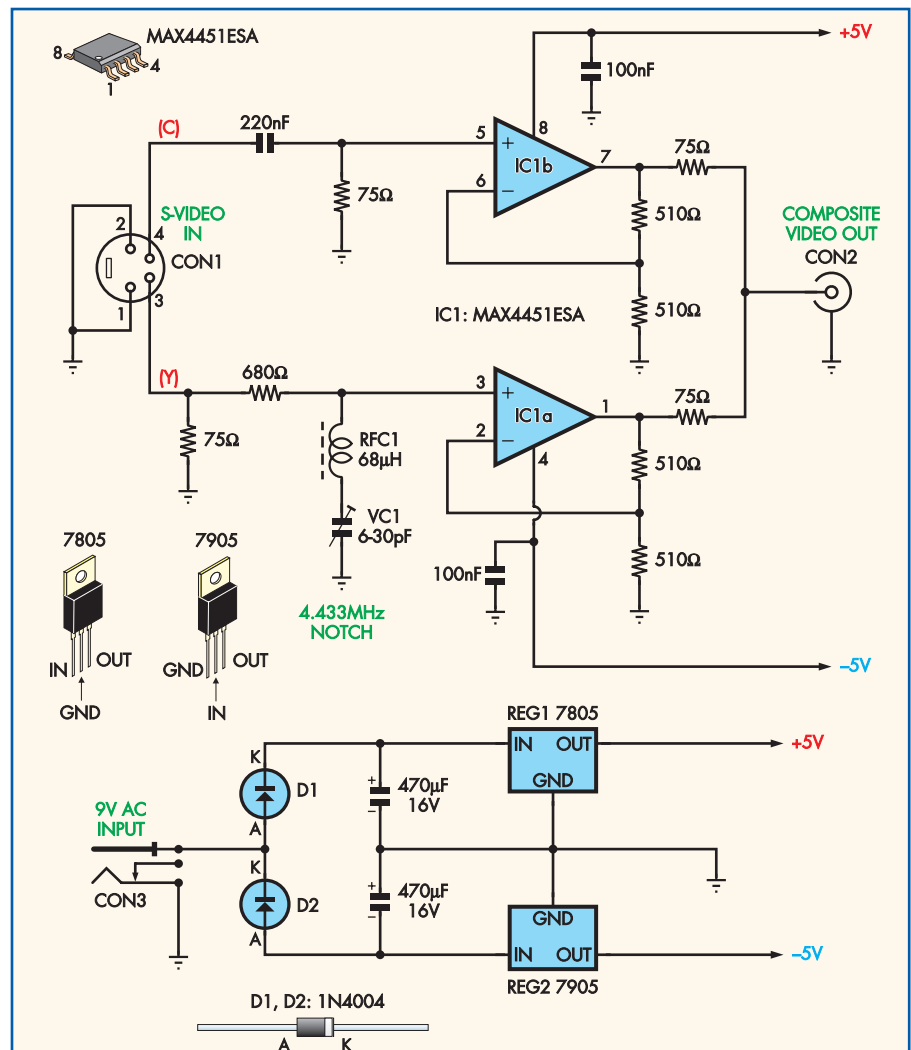This reduces the cross-colour interference, although it also removes some of the fine detail from the images, so



S-VIDEO TO COMPOSITE VIDEO CONVERTER


Fig.3: the circuit is based on a MAX4451 dual-wideband video amplifier IC, with each stage wired as a non-inverting amplifier with a gain of 2.0. Components RFC1 and VC1 provide the 4.43361875MHz notch in the luminance signal.



This screen shot shows the Snell and Wilcox moving plate test pattern fed through a 'cheapo' S-video to composite video converter. Note the obvious colour *Moiré* patterns on the moving plate section and in other areas where there are fine lines.



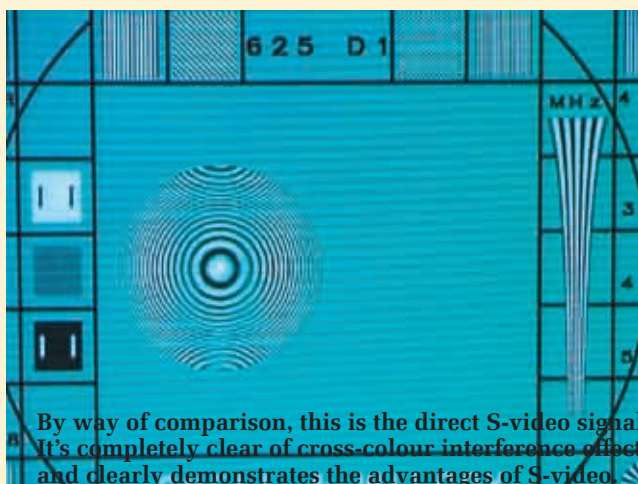This is the same test pattern as above, but this time fed through the S-Video converter. As can be seen, the cross-colour interference effects have been dramatically reduced.



By way of comparison, this is the direct S-video signal. It's completely clear of cross-colour interference effects and clearly demonstrates the advantages of S-video.

Parts List – S-Video Converter

- 1 double-sided PC board, code 684, available from the *EPE PCB Service*, size 76 × 46mm
- 1 UB5-type plastic box, size 83 × 53 × 31mm
- 1 68μH RF choke (RFC1)
- 1 mini 4-pin DIN socket, PC mounting (CON1)
- 1 RCA phono socket, yellow, PC mounting (CON2)
- 1 2.5mm concentric power connector, PC mounting (CON3)
- 4 M3 × 10mm machine screws, countersink head
- 4 M3 star lockwashers
- 10 M3 nuts
- 2 M3 × 6mm machine screws, round/pan head

Semiconductors

- 1 MAX4451ESA dual video op amp (IC1)
- 1 7805 +5V voltage regulator (REG1)
- 1 7905 -5V voltage regulator (REG2)
- 2 1N4004 400V 1A rectifier diodes (D1,D2)

Capacitors

- 2 470μF 16V RB electrolytic
- 1 220nF MKT metallised polyester
- 2 100nF multilayer monolithic
- 1 6-30pF trimmer, green (VC1)

Resistors (0.25W 1%)

- 1 680Ω
- 4 510Ω
- 4 75Ω

they become softer – ie, the chrominance output is also shunted to some extent.

In contrast, the unit described here does a better job of reducing cross-colour interference without sacrificing the higher frequencies in the Y signal nearly as much. As a result, the images stay reasonably sharp. It's admittedly a bit more complex than the 'cheapo' adaptors, but it's still low in cost and very easy to build and get going.

How it works

The approach taken here to reduce cross-colour interference is to use a simple *LC* trap circuit to notch out a fairly narrow range of frequencies in the incoming luminance (Y) signal, centred on the 4.43361875MHz colour subcarrier frequency. This removes most of the higher luminance frequencies that cause obvious cross-colour patterning, while leaving the luminance frequencies below about 3.5MHz and above 5.4MHz untouched. You can see the resulting luminance response in Fig.2.

By contrast, the incoming chrominance signal passes through its channel largely untouched, so there's no degradation of colour detail. As a result, the image quality of the composite video output signal is quite good. Of course, it's not as good as watching S-video directly, but it's noticeably better than what you get with a 'cheapo' adaptor.

Circuit details

Now let's take a look at the circuit diagram for the video converter – see Fig.3. As shown, the incoming S-video (Y/C) signals come in via CON1, a standard 4-pin mini-DIN socket. The C signal is fed through a 220nF coupling capacitor and is terminated by a 75Ω resistor to prevent ringing due to cable reflections.

From there, the signal is fed to pin 5 of IC1b, one half of a MAX4451 dual-wideband video amplifier IC, wired here as a non-inverting amplifier with a gain of 2.0. This gain is necessary to allow for mixing and output cable back-termination losses.

The incoming Y signal is treated a little more harshly. After being terminated by the correct 75Ω impedance, it's then passed through the 'notch' circuit. This consists of a series 680Ω resistor and a series LC-tuned circuit, formed by a 68μH RHF choke (RFC1) and a 6-30pF trimmer capacitor (VC1).

When VC1 is adjusted to resonate with RFC1 at 4.43361875MHz, this LC circuit forms a low-impedance path to earth at that frequency. This acts together with the 680Ω series resistor to produce the desired notch in the response, as shown in Fig.2.

From there, the rest of the Y signal is passed through IC1a, the other half of the MAX4451 device, which is also wired as a non-inverting amplifier with a gain of 2.0. The outputs of both IC1b and IC1a are then mixed using the two 75Ω output back-terminating resistors, to produce the final composite video output signal at output connector CON2.

Power supply

The MAX4451 IC needs a DC supply of ±5V and this is provided using the simple power supply circuit shown at the bottom of Fig.3.

Power comes from a 9V AC plug-pack supply and this feeds two half-wave rectifiers based on diodes D1 and D2. Their outputs are filtered using two 470μF capacitors and fed to positive and negative 3-terminal

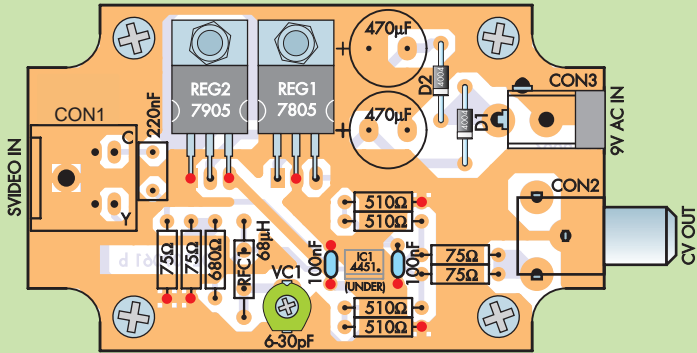


Fig.4: install the parts on the PC board as shown here, making sure that all polarised parts are correctly orientated. The leads designated with a red dot must be soldered to both sides of the board.


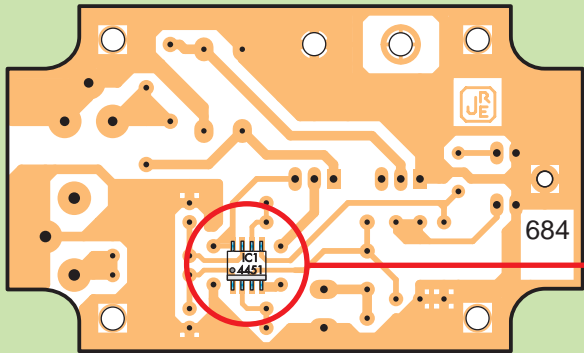



Fig.5: the MAX4451 comes in an SOIC-8 package and is mounted on the underside of the PC board as shown above and in the photo below right. Be sure to mount it with its chamfer side towards the bottom and use a soldering iron with a very fine chisel-tip to solder its leads.

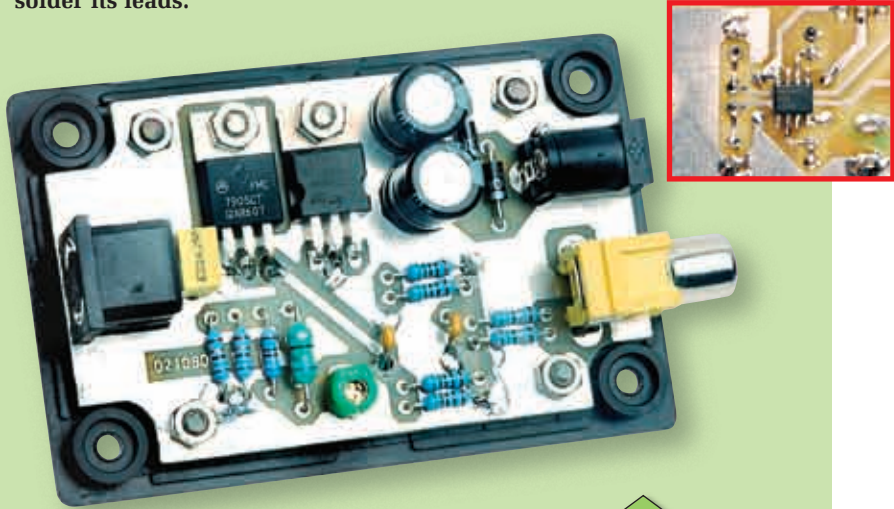

This is the fully-assembled PC board, mounted on the lid of the case. Power comes from an external 9V AC plugpack.

Table 2: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	1	680Ω	blue grey brown brown	blue grey black black brown
□	4	510Ω	green brown brown brown	green brown black black brown
□	4	75Ω	violet green black brown	violet green black gold brown

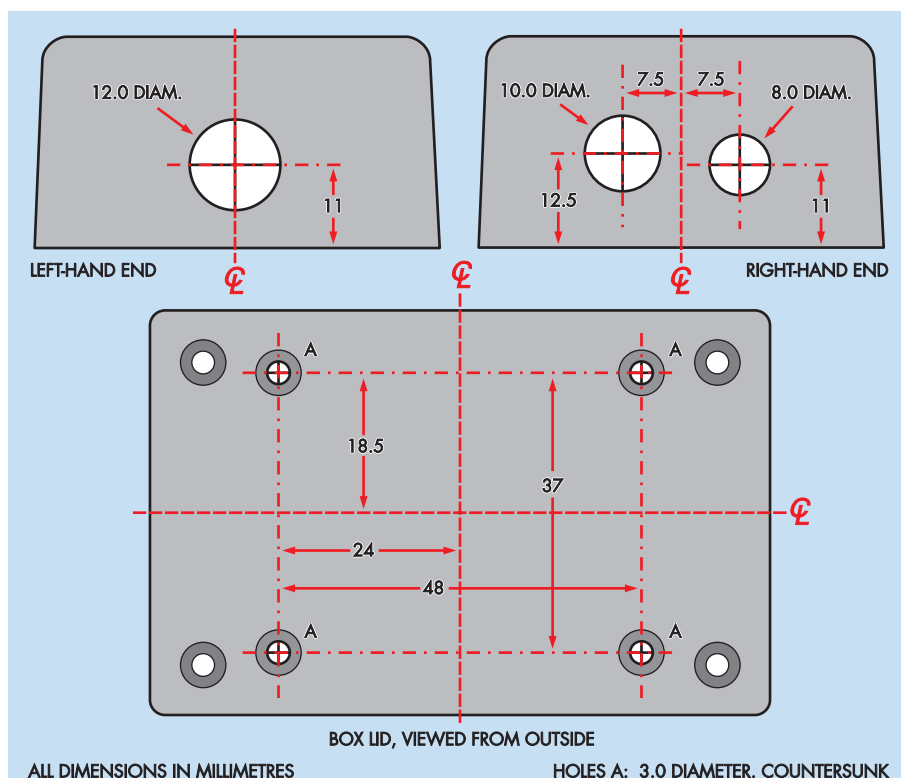

ALL DIMENSIONS IN MILLIMETRES

HOLES A: 3.0 DIAMETER. COUNTERSUNK

Fig.6: follow this diagram to mark out the holes to be drilled in the ends of the box and the box lid. Alternatively, you can scan this diagram, print it out and use it as a drilling template. The larger holes are best made by drilling a small hole first and then enlarging them using a tapered reamer.

voltage regulators REG1 and REG2. Regulator REG1 then provides the +5V rail, while REG2 provides the -5V rail.

Construction

All of the parts for the converter fit on a small double-sided PC board measuring 76 × 46mm. This board is available from the *EPE PCB Service*, code 684. Note, the board is not a 'plated through the hole' type. The topside component layout and the underside view, showing the MAX4451 IC positioning, is illustrated in Fig.4 and Fig.5.

The board has rounded cutouts in each corner, so it will fit snugly in

to one of the small plastic UB5 type boxes. The S-video input socket CON1 is at one end of the board and box, while the composite video output and power sockets (CON2 and CON3) are at the other end.

Begin construction by checking the hole sizes for the three connectors and enlarge these if necessary. That done, start the assembly by installing the resistors and the capacitors. Note that the two 470μF electrolytic capacitors are polarised and must be fitted with their positive leads towards the left, as shown on the overlay diagram.

As the board is double-sided, you must solder the component leads to both sides of the PC board in those locations marked with a red dot on Fig.4. That way, the component leads themselves make the necessary connections between the two sides of the board.

Trimmer capacitor VC1 can go in next, noting that its flat side goes towards the bottom of the board. Follow this with the 68μH RF choke (RFC1) – the PC board can accept either an axial-lead or 'single-ended' choke, so use whichever set of holes is the most convenient for the part supplied.

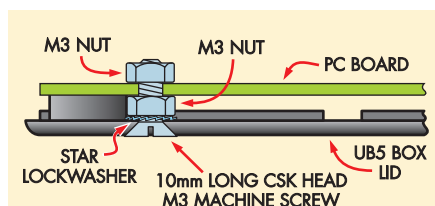


Fig.7: the PC board is mounted on the lid using M3 × 10mm machine screws, nuts and lockwashers.

Fit diodes D1 and D2, followed by regulators REG1 and REG2. The latter are both installed with their leads bent downwards by 90°, about 6mm from their bodies. Slip them into the positions indicated, then fasten their metal tabs to the PC board using M3 × 6mm machine screws and nuts before soldering their leads.

It's important not to solder the leads before the metal tabs are secured. If you do, the solder joints could fracture (or the copper tracks could lift) as the nuts are tightened. Take care to use the correct regulator type in each position (REG1 is a 7805 type, while REG2 is a 7905).

Surface mounting

Now for the dual video op amp (IC1). This comes in a very small SOIC-8 surface-mount package and is mounted on the underside of the board – see Fig.5. Note also that it's mounted with its chamfer and notch side towards the bottom edge of the board.

Because its leads are spaced just 1.25mm apart, you need to **take great care** when soldering them to the copper pads. Be sure to use a soldering iron with a very fine chisel-tip and make sure the tip is very clean.

Place the device and its leads carefully over the pads and hold it in place with a toothpick (or 'crossover' tweezers) while you just touch the tip of the iron to one lead for a second or two, to melt the solder underneath. This should be sufficient to hold the device in place while you solder all the other leads to complete the job.

The board assembly can now be completed by turning it back over and fitting the three connectors (CON1-CON3).

Final assembly

The PC board fits neatly into a UB5-size (83 × 53 × 31mm) plastic box, but first you have to drill the various holes in the box and its lid.

Fig.6 shows the locations and sizes of these holes. There are only seven holes in all: four in the lid for the PC board mounting screws and three larger holes in the box ends for the connectors.

Once these holes have been drilled, mount the PC board on the inside of the lid using four M3 × 10mm machine screws with countersink heads – see Fig.7. Note that each screw has an M3 star lockwasher fitted to it first, after which a nut is fitted and tightened to secure it in position.

In practice, these nuts act as spacers, which raise the PC board about 3mm from the lid (which is used here as the base). Once all the screws are in position, slip the PC board into place and secure it with the four remaining nuts.

Notch adjustment

The luminance notch trap can either be set visually or you can use an RF signal generator and an oscilloscope.

If you have access to the required test instruments, simply set the RF generator to 4.43361875MHz (use a frequency counter to do this if necessary) and feed its output into the Y signal input – ie, pin 3 of CON1 (or the junction of the 75Ω and 680Ω resistors). That done, use your scope to monitor the signal level at the composite video output of the converter (the centre pin of CON2) and adjust trimmer capacitor VC1 carefully until you see the signal level drop down into a sharp null.

The correct setting for VC1 is right at the bottom of that null.

Of course, you won't be able to set the notch frequency this accurately if



Fig.8: this full-size artwork can be cut out and attached to the lid of the case. A single layer of clear, wide adhesive tape will protect it from damage.

you don't have access to test instruments. In that case, you'll have to set it visually, with the converter operating on a suitable S-video signal from your set-top box or a DVD player.

Try to pick a scene where there is some cross-colour patterning visible in the images. It's then just a matter of slowly and carefully adjusting VC1 with an alignment tool or jeweller's screwdriver until the cross-colour 'nasties' disappear.

Note that you may need to repeat this procedure a few times until you're

confident that you've found the correct setting.

Finally, the box can be slipped over the lid assembly and secured using the small self-tapping screws provided. That's it – you're now ready to connect your set-top box or DVD player to your TV's composite video input via your new adaptor.

EPE

Reproduced by arrangement with
SILICON CHIP magazine 2008.
www.siliconchip.com.au

ANDRE LAMOTHE'S
XGAMESTATION
LEARN STEP-BY-STEP HOW TO DESIGN
AND BUILD YOUR OWN VIDEO GAME CONSOLE!
Design Inspired by the Atari 800/2600,
Sinclair ZX Spectrum, Apple II & Commodore 64!

Complete Package eBook Integrated IDE

SX52 CPU
80 MIPS!

OPEN SOURCE!

FEATURES:

- Great for Hobbyists AND Students!
- Complete Software Development Kit!
- eBook on Designing the XGS Console!
- Parallax SX-Key Compatible!
- Fully Assembled XGS Micro Edition Unit!
- The Fun Way to Learn Embedded Systems!

PAL & NTSC
COMPATIBLE!

WWW.XGAMESTATION.COM
SUPPORT@NURVE.NET Ph 512.266.2399 (USA)

e CRICKLEWOOD ELECTRONICS
Established 1981

Frustrated with your supplier?
Visit our component packed
website for a vast range of
parts - old and new,
many unavailable elsewhere!
www.cricklewoodelectronics.com

1000's OF PRICES REDUCED!

Alternatively phone us on
020 8452 0161 with your
requirements.

Visit our Shop, Call or Buy online at:
www.cricklewoodelectronics.com
020 8452 0161

Visit our shop at:
40-42 Cricklewood Broadway
London NW2 3ET



Practically Speaking

Robert Penfold looks at the Techniques of Actually Doing it!

HAVING completed a circuit board successfully it is tempting to sit back and regard the project as almost finished. With some projects this is probably a realistic view of things, but with others it is a bit like getting the lawnmower out of the shed and considering the lawn to be almost fully mown!

With many projects there is still a long way to go once the circuit board has been completed. The hard wiring and mechanical aspects of construction can be quite time consuming, but they should never be rushed.

Did it my way

Project articles invariably provide detailed instructions for building the circuit boards and completing the hard wiring, but are often fairly sketchy about the mechanical aspects of construction. Most constructors prefer to 'do their own thing' with this aspect of project construction, and this is reflected in project articles. There are exceptions, and with some of the more unusual projects it can be important for the original project to be cloned quite accurately, but in most cases there is plenty of freedom to 'do your own thing'.

A problem with going your own way is that the chances of making a mess of things are greatly increased. Careful planning is important when making anything, including relatively simple things. If you simply make it up as you go along, even with a fairly simple project, it will probably look as though the design was not properly thought through in advance.

You might even find that the finished project has a fatal flaw. The classic mistake is to forget about space for the battery. The finished project is perfect in every detail, apart from the fact that is not possible to fit the lid on the case unless the battery is removed!

Case study

The first task when designing the layout of a project is to select a suitable case. There are many different types of case available, but they can be categorised into two main sorts. These are the simple boxes, which are mostly made from plastic or from plastic with an aluminium lid, and instrument cases. The latter used to be made entirely from metal, but these days they are often in the form of a plastic shell with aluminium front and rear panels.

Instrument cases tend to be relatively expensive, but usually give a project a more classy appearance. Instrument cases are usually worth the extra outlay for larger projects or smaller projects where this type of case is appropriate, such as some types of test equipment.

It is usually all right to use any case that is large enough to accommodate everything properly, but it is a good idea to check the construction notes before buying anything. Plastic cases are unsuitable in some applications, while in others a metal case is unsuitable.

Some radio projects for example, have an internal aerial that will be shielded from the radio signals if a metal case is used. With other projects, such as sensitive

audio circuits, it is the other way around. A metal case is needed in order to screen the electronics from radio waves and other sources of electrical interference. Always heed the advice when an article specifies a certain type of case. The project is unlikely to work if you go against this advice.

In these days of miniaturisation it is tempting to cram projects into the smallest possible housing, but it is also a mistake. The 'quart into a pint pot' approach to project construction makes building the projects much more difficult, and it does not necessarily produce a more usable end product. In fact, the opposite can apply, with the finished project being very fiddly and awkward to use. Going in the opposite direction is not a good idea either, as it could produce a cumbersome project in a case that is unnecessarily expensive.

So how do you work out whether a likely case will actually be just about right for your latest project? It is not just a matter of choosing a case that will accommodate all the components; it must be able to take everything using a sensible layout. The front panel layout might look quite good with several controls grouped very close together, but it will be of little practical use if it is virtually impossible to get at each control and operate it properly.

The finished unit needs to look reasonably neat, but it is usability that is of paramount importance. The case must be sufficiently large to permit a layout that has everything well positioned.

Ins and outs

You have to be careful when considering the sizes quoted for boxes and cases in component catalogues. Sometimes internal and external dimensions are quoted, and it is the internal size that governs the useful capacity of an enclosure.

Where only external dimensions are quoted, it is necessary to reduce them by about 5mm to 10mm in order to give an approximation of the internal size. There is a slight complication here, in that most cases have internal obstructions, and these can effectively reduce the internal dimensions of a case.

For instance, many cases have mounting pillars or guide-rails for printed circuit boards (PCBs). These might be useful for their intended purpose, but in practice they are often unnecessary and just get in the way. Many cases have threaded pillars to take the mounting bolts for the lid or outer cover. The mounting pillars for the lid are usually right in the corners, where they are unlikely to become major obstructions, but I have encountered instrument cases where they are positioned well in from the corners, often making their use problematic.



Fig.1. Clockwise from the top left, a large but simple plastic box, a simple folded aluminium box, a steel instrument case with an aluminium chassis, and a plastic instrument case that has an aluminium front panel

Some cases have internal mouldings that seem to serve no purpose whatever, and they are presumably needed as part of the manufacturing process.

Ideally, you need to see a case before buying it, so that a check for any major obstructions can be made. In practice, it will probably not be possible to do this, but illustrations in catalogues can help. Once again though, it is best to err on the side of caution and choose a case that has ample proportions rather than one where you are trusting to luck.

Some obstructions can be carefully removed if they cause major problems. For example, plastic mounting pillars for circuit boards can usually be drilled down to practically nothing. With this type of thing be careful not to overdo it and damage the case, or to remove anything that is actually an important part of the case.

Be careful when designing a layout for a project that uses a case having the outer cover held in place by long self-tapping screws. These penetrate well into the case when the outer cover is fitted in place, possibly with disastrous results if the interior layout has not been designed with due care.

Despite making careful measurements, mounting screws have damaged a battery on one occasion, and even a mains lead on another. Always allow an excess of space for anything like this, and with screws that are unreasonably large it is a good idea to replace them with shorter ones.

Direct approach

It is easy to draw up wonderful plans for a project that looks really good, but real-world design work tends to be about the balancing of conflicting requirements. Ideally, the controls and sockets would be positioned to give a neat and attractive layout, and nothing else would be taken into account. Unfortunately, such a layout might not be very practical. Layouts having long wires running all over the place are best avoided. This is not just a matter of avoiding lots of trailing wires because they look decidedly scrappy. It can be necessary to position controls and sockets where they permit short and neat wiring, rather than simply placing them wherever you like.

Often the wiring has to be kept quite short in order to minimise problems with stray pick up of mains 'hum' and other signals, and to minimise stray feedback. Where appropriate, an article should point out any important restrictions on the layout, such as leads that have to be kept very short, and leads that should be kept well apart. With analogue circuits, it is generally advisable to keep inputs and outputs well separated, and to arrange the layout so that, as far as possible, the wiring can be kept short and direct.

Looks right

When drawing front panel layouts it is best to avoid taking an overly mathematical approach, but a haphazard approach to things is best avoided as well. Front panels usually look neater if there is equal spacing in a row of control knobs of the same size, and if everything is arranged in one or two rows rather than on several levels.

However, a purely mathematical approach to front panel layouts will not always produce the best looking results. The best

looking layout is the one that actually looks best, and not the one that has the best geometry 'on paper'. A good way to try out layouts is to place the control knobs onto the front panel, together with fixing nuts to represent things like toggle switches or sockets. This gives a very good impression of the finished panel's appearance, and it also helps to avoid producing a 'paper' design that cannot be turned into a finished project due to a lack of space for certain components. It is still necessary to do some careful checking and measuring to ensure that there is room for everything. The components on the rear of the panel can be much larger than the control knobs and mounting nuts at the front. Remember to check that nothing fitted on the front panel will be blocked by any obstructions inside the case.

When everything looks just right and the checking process has been completed, make careful measurements and draw a plan of the layout. It does not matter whether the plan is drawn on a scrap of paper using a pencil stub or using the latest computer aided drawing program on a computer. What really matters is that it is clear, that nothing has been omitted, and that you can easily follow it when drilling and cutting the front panel of the case.

Marking out

It is a good idea to double-check the layout to make sure you have not overlooked anything, and then the layout can be transferred to the front panel. Take due care when doing this, as many project cases are made from soft plastics or aluminium. These materials have the advantage of being relatively easy to work, but they are also easily damaged. Mark the drilling points using something that will not scar the case for life, such as a fibre-tip pen.

Avoid using spirit-based inks on plastic panels, because the spirit in the ink might dissolve the plastic and permanently mark the panel. The suitability of a pen can be determined by trying it on an inner surface of the case or panel, where any damage will be of no importance. Very soft pencils (about 6B) mark aluminium panels reasonably well and should not cause any damage. An ordinary eraser can be used to remove the lines when the drilling and cutting have been completed. Inks that are not spirit based can usually be removed with a damp cloth or piece of kitchen towel.

An alternative approach is to fix a piece of paper over the front of the panel using double-sided adhesive tape or a Pritt-Stick glue pen. In other words, something that will hold the paper in place quite well temporarily, but is easily removed once the paper has served its purpose.

This method is very useful with some plastic panels, which seem to resist any form



Fig.2. This plastic box has an uncluttered interior, but the printed circuit mounting rails moulded into the sides make it difficult to mount anything else on these panels

of ink. It works well with practically any case though, making it easy to mark the layout very accurately. Also, the paper gives some protection to the panel. The paper should peel off quite easily once work on the panel has been completed, and any remaining adhesive or paper is then washed off.

Softly, softly

I make no apology for repeating this warning to those who are experienced in general do-it-yourself tasks, car servicing, house extensions, and so on. With electronic project construction you are dealing with minute and often delicate components that require a more gentle approach. Applying the 'hammer and tongs' approach to delicate circuit boards and small plastic cases is likely to result in a great deal of time and materials being wasted. Most projects are housed in plastic or aluminium cases that are easily damaged. The vast majority of cases have finishes that are easily spoiled. Electronic project construction requires a 'softly, softly' approach.

Use a centre punch to mark the positions of holes in metal cases. The punch produces tiny indentations that guide the drill bit and make accurate drilling much easier. An automatic punch works well with aluminium panels. Take due care when using an ordinary punch with aluminium cases, as thin aluminium panels can buckle and distort quite easily.

Using centre punches with plastic cases is a bit risky, since some plastic cases are easily cracked, but an indentation is still needed to stop the drill bit from wandering. Probably the best method is to use a pointed tool such as a bradawl, using the smallest amount of pressure that will do the job properly.

It is then a matter of clamping the panel to the worktop, complete with a scrap piece of MDF or timber beneath the panel. This supports the panel so that there is less risk of it buckling and it also helps to give 'cleaner' holes. It will probably be necessary to use some pieces of cloth to prevent the clamps from marking the panel.


Due to the softness of the materials used for most cases, drill slowly and carefully. Drill holes using an electric drill set at a low speed, or use a hand drill. Proceed slowly and carefully, and you should end up with a first-class finished product.

Resurrect your old LPs and 78s . . .



Build this magnetic cartridge preamplifier

...and dub them onto CDs or MP3 files

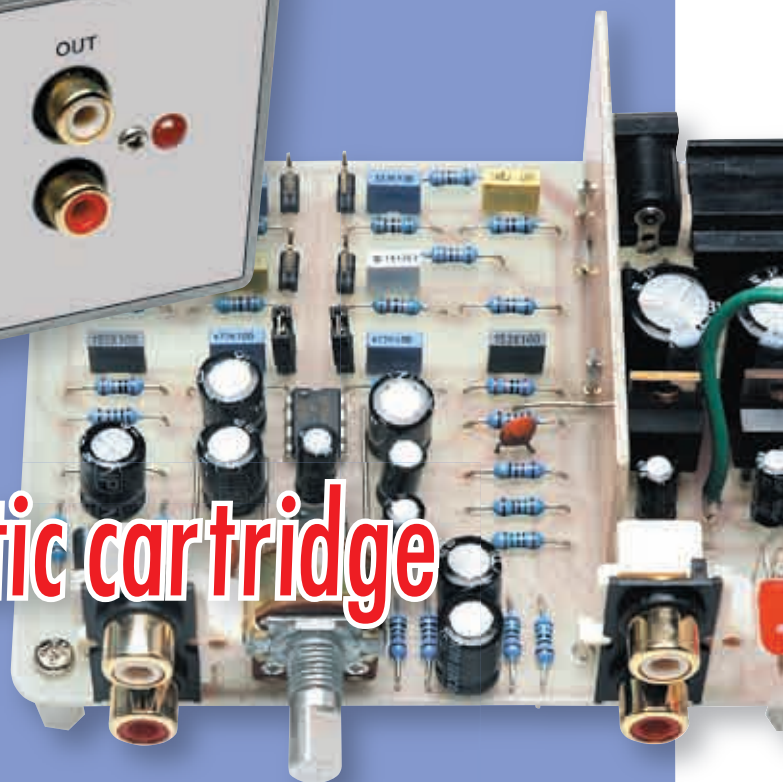

Do you have an old turntable but no RIAA inputs on your preamplifier? If so, you need this preamplifier for playback and for converting the output to CD or MP3 format.

By JOHN CLARKE

DO YOU HAVE a collection of old vinyl or 78 RPM records languishing in a cupboard? Perhaps you should resurrect them before they deteriorate further.

To do this, you need a computer with a CD or DVD burner, suitable software and a preamplifier. The preamplifier described here can be built to suit vinyl or 78 records, and


is self-contained. You can build it into a diecast metal case or mount it underneath your turntable.

Of course, some people will just want to listen to their records without the bother of feeding signals into a computer and so on. This preamplifier will suit those people too, but ultimately, we think that anyone who has become used to the

high-quality sound of compact discs or MP3 players will be disappointed with the clicks and pops and surface noise on LPs and 78s.

So, by all means build the preamplifier to play your old records, but you will probably end up going the whole way and dubbing your records to CD. In the process, you can filter out most of the clicks and noise and once again enjoy those old favourites.

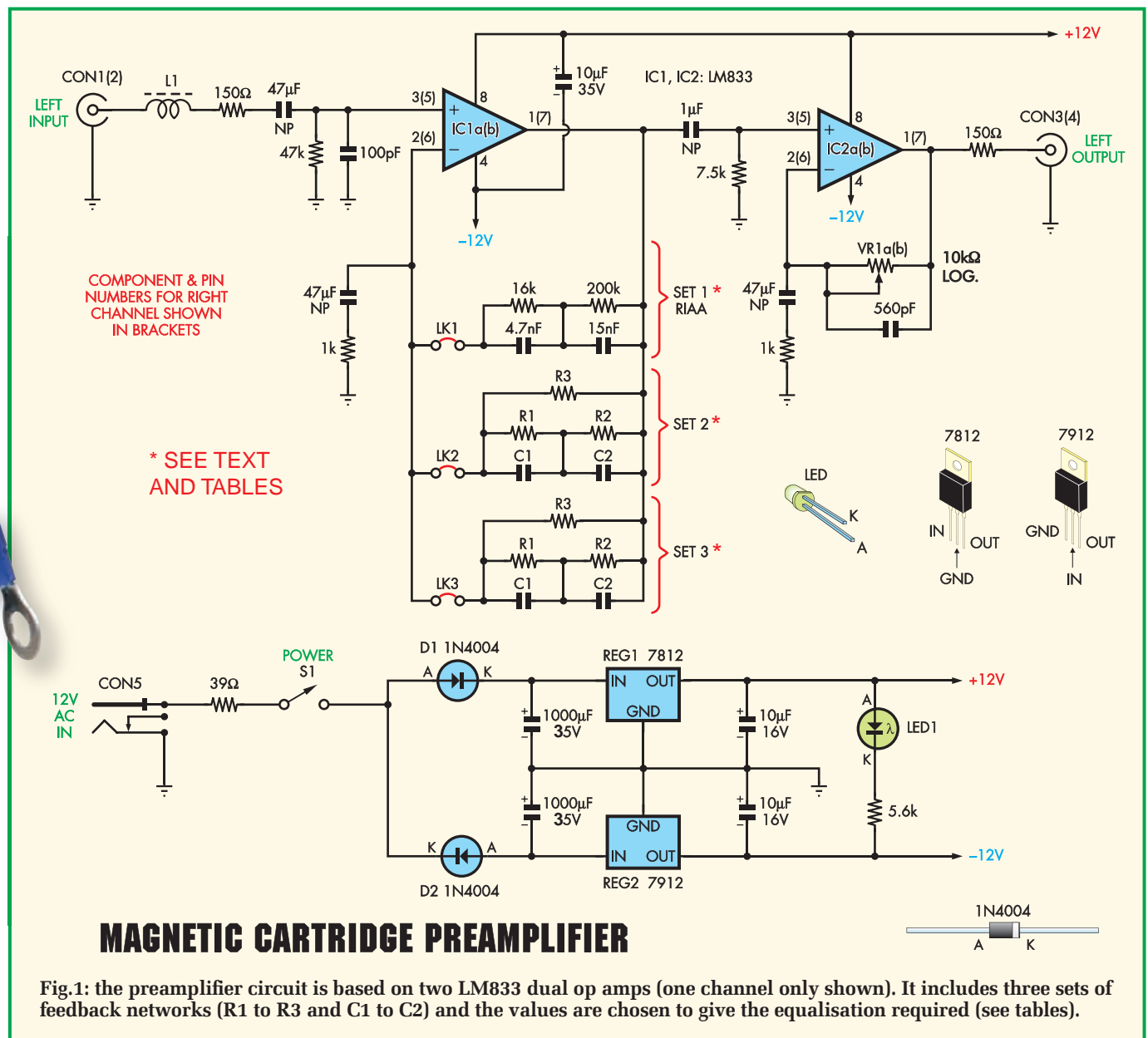If you only have vinyl records (LPs) you can build this project as a standard preamplifier with RIAA equalisation, but if you want to play 78s, you will need to choose one of three equalisation curves that can also be built in. You will also need a turntable that can play at 78 RPM and a cartridge that



accepts the correct stylus. Ideally, the turntable should have speed adjustment so that the pitch can be changed, but this is a rare feature. Alternatively, commonly available recording software can adjust the pitch when you dub the records to CD.

The RIAA preamplifier is housed in a diecast metal box and has RCA phono sockets for the input and output connections. It has a control to set the output level and is powered using an AC plugpack.

Circuit description

The preamp circuitry is based on two LM833 dual op amp ICs, as shown in Fig.1. This shows the left channel only; the right channel is identical.

Some readers may wonder why we have used LM833 dual op amps instead of the newer high-performance OPA2134 devices featured in our recent *Studio Series Preamplifier* (Feb '08 to May '08). In fact, they could be used, but since the signal source is a

magnetic cartridge playing vinyl or 78 RPM shellac records, any slight performance improvement will be negligible and is unlikely to be discerned by listening.

The input signal is fed through inductor L1, a 150Ω resistor and a 47μF

Specification

Signal-to-noise ratio: -84dB unweighted with respect to 10mV in and 560mV out (-89dB A-weighted)

Total harmonic distortion at 1kHz, 10mV in and 560mV out: 0.014%

Crosstalk: -79dB at 100Hz, -80dB at 1kHz and -70dB at 10kHz

Signal handling: 140mV before clipping

RIAA accuracy: typically within 1dB from 20Hz to 20kHz (see graph - Fig.2)

Parts List

- 1 PC board, *EPE* code 681, available from the *EPE PCB Service*, size 102 × 81mm
- 1 blank PC board, size 70 × 30mm (screening shield)
- 1 diecast box, 119 × 94 × 57mm
- 1 12V AC 250mA plugpack
- 1 SPST slimline toggle switch (S1)
- 2 dual RCA phono PC-mounting sockets (CON1 to CON4)
- 1 5-pin DIN PC-mount socket (optional)
- 1 2.5mm PC-mount DC socket
- 1 16mm dual-ganged 10kΩ log PC-mount potentiometer (VR1)
- 2 crimp eyelets
- 1 green banana socket
- 6 2-way 2.5mm pin headers (from a 12-way header strip)
- 2 2.5mm jumper plugs
- 2 ferrite beads 4mm OD × 1.5mm ID × 5mm (L1,L2)
- 4 10mm M3 tapped spacers
- 4 adhesive rubber feet
- 4 M3 × 6mm screws
- 2 M3 × 10mm screws
- 2 M3 nuts and star washers
- 2 No.8 self-tapping screws
- 7 PC stakes
- 1 150mm length of green hook-up wire
- 1 150mm length of red hook-up wire
- 1 150mm length of 0.7mm tinned copper wire

Semiconductors

- 2 LM833 dual op amps (IC1,IC2)
- 1 7812 +12V regulator (REG1)
- 1 7912 -12V regulator (REG2)
- 2 1N4004 1A diodes (D1,D2)
- 1 5mm red LED (LED1)

Capacitors

- 2 1000μF 35V PC electrolytic
- 6 47μF NP or BP non-polarised electrolytic
- 1 10μF 35V PC electrolytic
- 2 10μF 16V PC electrolytic
- 2 1μF NP or BP non-polarised electrolytic
- 2 560pF ceramic
- 2 100pF ceramic

Resistors (0.25W 1%)

- 2 47kΩ 4 150Ω
- 2 7.5kΩ 1 39Ω
- 4 1kΩ

RIAA components

- 2 200kΩ resistors
- 2 16kΩ resistors SEE
- 2 15nF capacitors TABLES
- 2 4.7nF capacitors

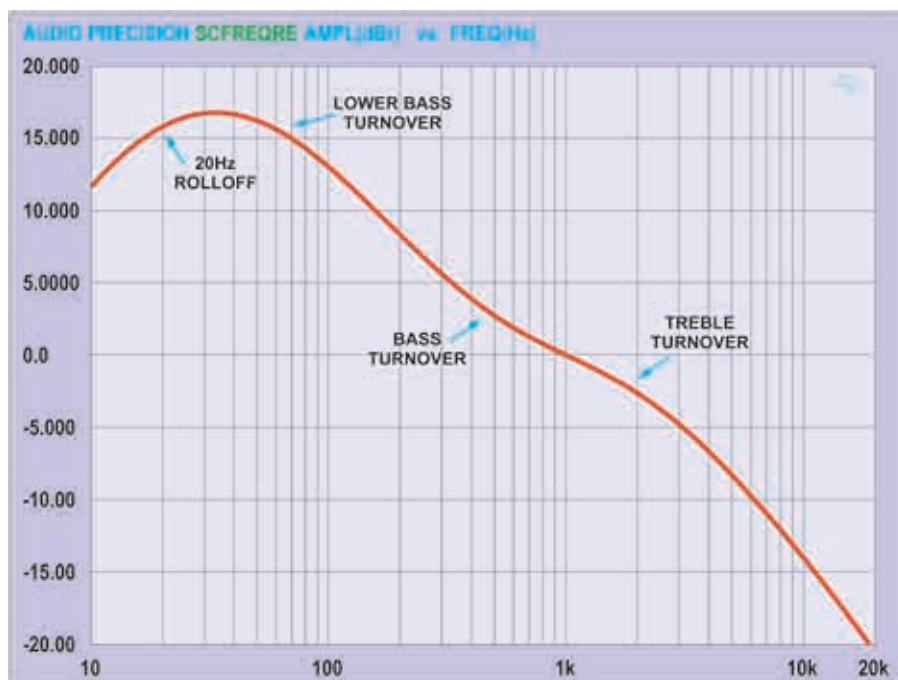


Fig.2: the RIAA response curve. The bass and treble turnover frequencies are set by the RC components in the feedback network connected to IC1a in the preamplifier.

capacitor to pin 3 of IC1a. The 47kΩ resistor and 100pF capacitor provide the loading for a typical magnetic cartridge. The 100pF capacitor also functions as an RF input filter, in conjunction with inductor L1 and the 150Ω resistor.

IC1a's gain is set by the feedback components between pin 1, pin 2 and ground. The 1kΩ resistor and 47μF non-polarised (NP) capacitor set the low-frequency roll-off for this stage at around 3Hz.

We have shown three sets of feedback components (C1, C2, R1, R2 and R3) and these can be selected to provide the RIAA or other equalisation

responses for older recordings. The three sets of feedback components are labelled SET1, SET2 and SET3 and the particular equalisation SET is selected using jumper plug LK1, LK2 or LK3. The feedback components for the various equalisation curves are shown in Tables 2 and 4.

High-pass filter

IC1a's output appears at pin 1 and is fed to pin 3 of IC2a via a high-pass filter comprising a 1μF capacitor and a 7.5kΩ resistor. This filter rolls off signals below 20Hz to reduce rumble from the turntable. Signals above 20Hz

Why so many choices for equalisation?

Readers may be surprised to see the different equalisation curves for vinyl and 78 RPM records. It is not well-known these days, but before the recording industry standardised on the RIAA curves, the bigger recording companies had their own equalisation curves, hence there were curves such as Decca's 'ffrr' (full frequency range recording), as well as those for EMI, NARTB and Columbia.

The situation was even more chaotic before vinyl LPs came on the scene, and there was more choice (and confusion) with 78 records. Hence, some of the equalisation curves used included Decca (EMI) 78, Westrex and so on.

The reason for including these different sets of components in Tables 2 and 4 is so that if you can identify the company that made a particular recording, you can then select the appropriate equalisation characteristic.

Note that we have also shown values for flat frequency response (ie, no equalisation) and tape head equalisation.

Table 1: Microgroove 45 and LP frequencies

Curve	Treble turnover	Bass turnover	Lower bass turnover	Cut at 10kHz	Boost at 50Hz
RIAA	2.1215kHz	500Hz	50.5Hz	-13.6dB	17dB
ffrr LP	3kHz	500Hz	100Hz	-10.5dB	12.5dB
EMI LP	2.5kHz	500Hz	70Hz	-12dB	14.5dB
NARTB	1.6kHz	500Hz	–	-16dB	16dB
Columbia	1.59kHz	500Hz	100Hz	-16dB	12.5dB

Table 2: Components for microgroove 45s and LPs

Curve	R1	R2	C1	C2	R3
RIAA	16k Ω	200k Ω	4.7nF	15nF	–
ffrr LP	220k Ω	18k Ω	15nF	3.3nF	270k Ω
EMI LP	330k Ω	18k Ω	15nF	3.9nF	270k Ω
NARTB	2.2nF	18k Ω	18nF	5.6nF//390pF	270k Ω
Columbia	100k Ω	18k Ω	18nF//2.2nF	5.6nF//390pF	270k Ω

Table 3: Coarse groove 78 frequencies

Curve	Treble turnover	Bass turnover	Lower bass turnover	Cut at 10kHz	Boost at 50Hz
Decca 78	3.4kHz	150Hz	–	-9dB	11dB
ffrr 78	6.36kHz	250Hz	40Hz	-5dB	12dB
Westrex	Flat	200Hz	–	–	15dB
Blumlein	Flat	250Hz	50Hz	–	12dB
BSI 78	3.18kHz	353Hz	50Hz	-10.5dB	14dB

Table 4: Components for coarse groove 78s

Curve	R1	R2	C1	C2	R3
Decca 78	open	18k Ω	68nF	3.3nF	270k Ω
ffrr 78	220k Ω	18k Ω	33nF	1.5nF	270k Ω
Westrex	18nF	18k Ω	33nF	–	270k Ω
Blumlein	220k Ω	18k Ω	33nF	–	270k Ω
BSI 78	220k Ω	18k Ω	22nF	3.3nF	270k Ω

Table 5: Components for a flat response

Gain	R1	R2	C1	C2	R3
x 1	open	1k Ω	–	4.7nF	–
x 10	link	10k Ω	–	470pF	–
x 100	link	100k Ω	–	47pF	–

Table 6: Components for tape head equalisation

	R1	R2	C1	C2	R3
NAB	–	3.6k Ω	–	15nF	200k Ω

These tables show the components necessary to achieve the various response curves required to play back from vinyl records and other recording surfaces, including Shellac 78s and tape heads. The parts necessary to achieve a flat response (with various gains) for general purpose use are also shown.

are free to pass to the next stage of amplification within IC2a.

The gain of op amp IC2a is adjustable using potentiometer VR1. When VR1 is set fully anticlockwise, its resistance is zero and IC2a has a gain of one. Conversely, when the wiper is fully clockwise, VR1's resistance is 10k Ω and so the gain is 11. The 560pF capacitor across VR1 rolls off the gain at higher frequencies to prevent oscillation.

The outputs from IC2 are fed to the RCA phono sockets via 150 Ω resistors, another measure to prevent oscillation because of the capacitance of the screened signal leads.

Power for the circuit comes from a 12V AC plugpack, which is fed to two diodes and two 1000 μ F capacitors to produce positive and negative supply rails. These are fed to 3-terminal voltage regulators (REG1, REG2) to derive \pm 12V DC rails.

Note that the plugpack feeds the two rectifier diodes (D1, D2) via a 39 Ω resistor to limit the peak current into the 1000 μ F capacitors. This minimises any tendency for 100Hz rectifier buzz to become audible in the preamp's output signal.

The metal case of the preamp may be earthed if necessary, to avoid mains hum in the signal. In most cases, this will not be required.

Building the preamplifier

The preamplifier is built on a single-sided PC board, measuring 102 \times 81mm. This board is available from the *EPE PCB Service*, code 681. It fits into a diecast box, size 119 \times 94 \times 57mm. Fig.3 shows the component layout and wiring details.

It's a good idea to first check the PC board for any defects, such as shorts between copper tracks, or for any breaks in the copper areas. Repair these if necessary and also check that the board has the correct hole sizes for components such as the dual RCA phono sockets, DC power socket and the dual-ganged potentiometer.


Begin the assembly by installing all the links, PC solder stakes and 2-pin headers. Before you insert the resistors, decide on the value of components you are going to use for each of the equalisation sets. **In most cases you will only use one set for the RIAA equalisation (the others can be left out).** Note that you need to place the same components in both the left and right channels for each set.

Constructional Project

Table 7: Capacitor Codes

Value	μ F Code	EIA Code	IEC Code
68nF	0.068 μ F	683	68n
33nF	0.033 μ F	333	33n
22nF	0.022 μ F	223	22n
18nF	0.018 μ F	183	18n
15nF	0.015 μ F	153	15n
4.7nF	0.0047 μ F	472	4n7
5.6nF	0.0056 μ F	562	5n6
3.9nF	0.0039 μ F	392	3n9
2.2nF	0.0022 μ F	222	2n2
1.5nF	0.0015 μ F	152	1n5
560pF	NA	561	560p
470pF	NA	471	470p
100pF	NA	101	100p
47pF	NA	47	47p

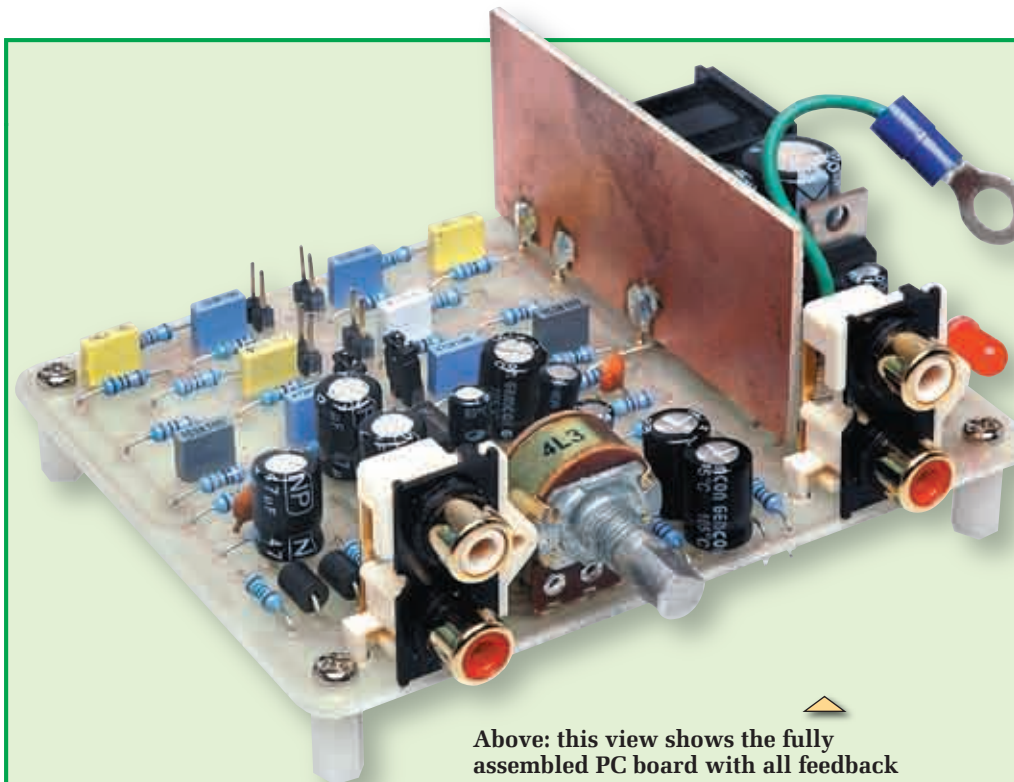Reproduced by arrangement with
SILICON CHIP magazine 2008.
www.siliconchip.com.au



Above: this view shows the fully assembled PC board with all feedback component sets installed. In practice, you would normally only install one feedback set (typically for RIAA equalisation) and omit the parts for the other two sets.



The PC board is installed in the case by angling it (as shown here) so that the RCA phono sockets and the pot shaft go through their respective holes. It then sits on nylon spacers that are pre-fastened to the bottom of the case and it is secured using machine M3 \times 6mm screws.

Install the resistors using the colour code table (Table 8) as a guide to finding the correct values. It's also a good idea to use a digital multimeter to make sure they are the correct values, as some of the colours can be difficult to decipher.

The two ferrite beads are mounted with short lengths of tinned copper wire passed through them.

The ICs can go in next, taking care to orient them correctly. Install the two diodes and the two voltage regulators, make sure the 7812 and the 7912 types are placed in their correct positions.

Next up are the capacitors. The polarised electrolytic types must be mounted with the correct polarity, as shown on the overlay diagram (Fig.3). Also, make sure you use the 35V 10 μ F capacitor adjacent to IC2. The NP (non-polarised) or BP (bipolar) electrolytic capacitors can be inserted either way around. Use Table 7 as a guide to selecting the non-electrolytic capacitors.

Next, mount the two dual RCA phono sockets, the potentiometer and












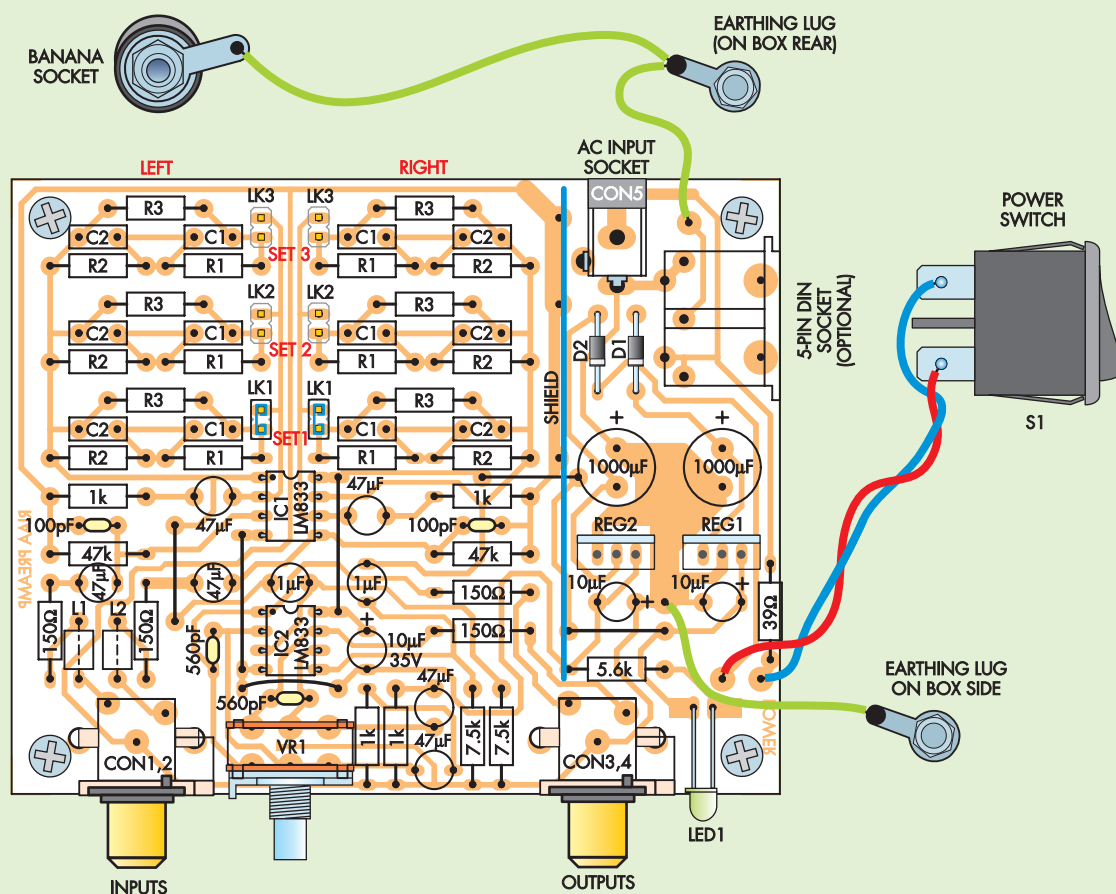  
 


Fig.3: follow this parts layout and wiring diagram to build the preamplifier. Note that you can select only one set of feedback components at a time using either links LK1 or LK2 or LK3.

Table 8: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
	1	330kΩ	orange orange yellow brown	orange orange black orange brown
	1	270kΩ	red violet yellow brown	red violet black orange brown
	1	220kΩ	red red yellow brown	red red black orange brown
	2	200kΩ	red black yellow brown	red black black orange brown
	1	100kΩ	brown black yellow brown	brown black black orange brown
	2	47kΩ	yellow violet orange brown	yellow violet black red brown
	1	18kΩ	brown grey orange brown	brown grey black red brown
	2	16kΩ	brown blue orange brown	brown blue black red brown
	1	10kΩ	brown black orange brown	brown black black red brown
	2	7.5kΩ	violet green red brown	violet green black brown brown
	4	1kΩ	brown black red brown	brown black black brown brown
	4	150Ω	brown green brown brown	brown green black black brown
	1	39Ω	orange white black brown	orange white black gold brown


the DC socket. The optional 5-pin DIN socket can be installed later if you find that you need an earthed supply and there's no mains earth available (eg, an earthed metal case) to connect to the green banana socket.

The 'screening' shield consists of a piece of PC board, size 70 × 30mm, and is soldered to the PC stakes in the position shown. LED1 mounts high on its leads so it can be bent over and inserted into a hole in the side of the case.

Case work

The metal case will require drilling to accommodate the two stereo RCA phono sockets, the potentiometer and the LED on the front face of the case. On one side, holes are required for the

Constructional Project

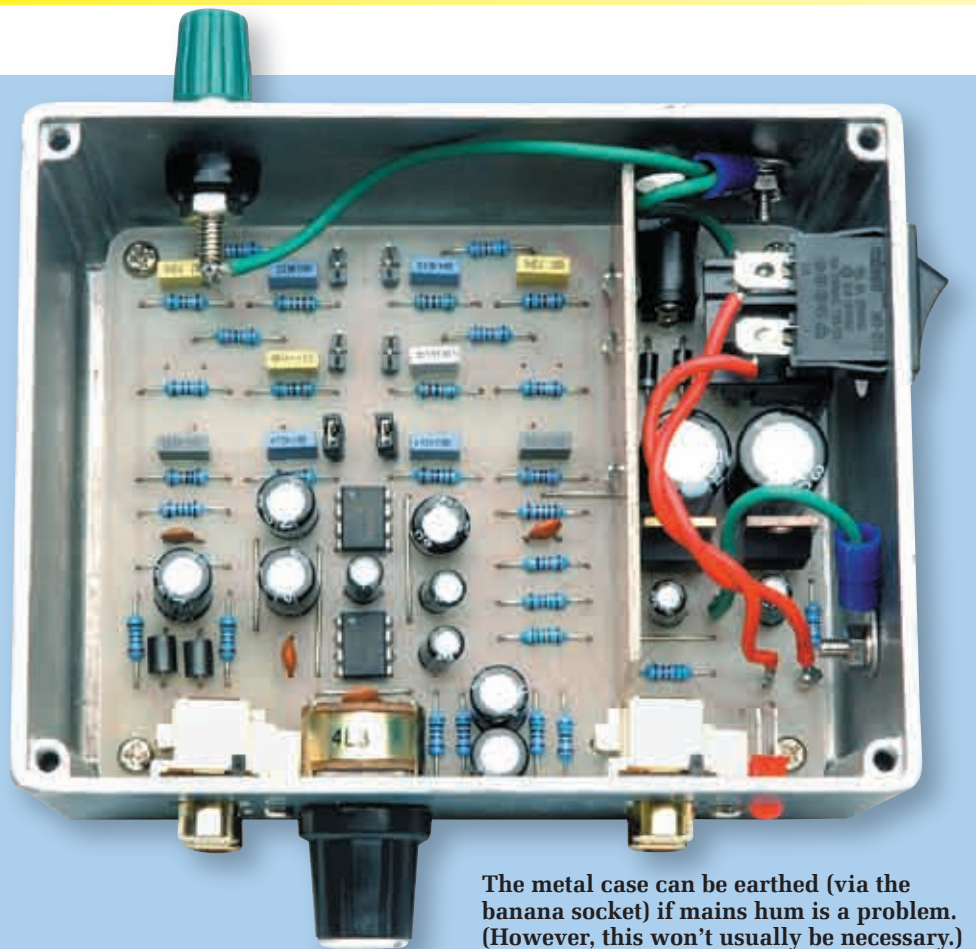

The metal case can be earthed (via the banana socket) if mains hum is a problem. (However, this won't usually be necessary.)


earth screw, the power switch and the DIN socket if used. At the rear, holes are required for the DC supply socket and the banana screw terminal/socket.

Mark and drill these holes. The slot required for the switch is best made by drilling about three holes within the cutout area and then filing it to shape. Four holes are also need to be drilled in the base for the plastic spacers for the PC board.

That done, attach the four rubber feet to the base of the case and then wire up the switches and earth connections as shown in Fig.3.

Testing

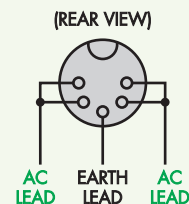Connect power to the preamplifier and check that the LED lights when power is switched on. If it does not light, then perhaps the LED is installed the wrong way around.



WIRING THE 5-PIN DIN PLUG

Fig.4: use the 5-pin DIN plug only if you need an earthed supply. The Jaycar MP-3022 earthed 17V AC plugpack can supply the required AC power and earth.

Next, measure the voltage between pins 4 and 8 of IC1 and IC2. It should be close to 24V DC in both cases. If this is correct, you are ready to connect a turntable and test the preamplifier.

Select RIAA equalisation for both the left and right channels using the jumper links, then connect the RCA phono leads from the turntable to the input sockets on the preamplifier. The RCA phono outputs on the preamplifier go to either a power amplifier or the line input of a computer using a 'Y' lead. The Y lead consists of a shielded stereo lead with RCA phono plugs at one end and a stereo 2.5mm jack plug at the other end.

If you are connecting the preamp to an amplifier, then plug in headphones or use loudspeakers.

If you are playing to a computer, then make sure the line input level is turned up. You can set this in Windows XP via Start/Settings/Control Panel/Sounds and Audio Devices/Audio, then select Volume in the Sound Recording section. EPE



EPE Online
www.epemag.com

Get your magazine 'instantly' anywhere in the world – buy and download from the web.

TAKE A LOOK, A FREE ISSUE IS AVAILABLE

A one year subscription (12 issues) costs just \$18.99(US)

Back issues are also available

MAGENTA

ELECTRONICS LTD

135 Hunter Street Burton on Trent Staffs DE14 2ST
Tel: 44 (0)1283 565435 Fax: 44 (0)1283 546932

**Chips, Parts
& Kits for
EPE Projects**

Programmed PICs and
chips for most EPE
projects.
Check our website or
'phone for prices.
We have supplied kits
for EPE* projects for
almost 30 years!!
(& Everyday Electronics)

20W Stereo Amp.

Wide band Low distortion
11W /channel
Stereo 20W Mono. True
(rms) Real Power

Short Circuit & Overheat
Protected. Needs 8 to
18V supply.
(Kit: inc. all parts & heatsink
for stereo or mono)



Latest Technology
- Stable, Reliable,
high performance

KIT 914- £11.90

Top Kits.

ICEbreaker PIC16F877 in - circuit
emulator - Kit 900.... £34.99

1kV/500V Insulation Tester
Inc. drilled case -Kit 848.. £32.95

Pipe Descaler - High Power
with led monitor - Kit 868..£22.95

Ultrasonic PEsT Scarer random
32k pulses Kit867..£19.99

P-I Metal Detector Micro based
design - sensitive Kit847..£63.95

MAGENTA Bat Detectors

Our original famous KIT detector
KIT 861...£37.99 & See the new
built MkIIb and MKIII on the web.

All Prices Include VAT, Add £3.00 P&P per order, or £7.99 for next
day. Chqs. P.O. & most major cards accepted. Mail Order Only.

MAGENTA

www.magenta2000.co.uk
sales@magenta2000.co.uk

SHERWOOD ELECTRONICS

Buy 10 x £1 Special Packs and choose another one FREE

SP1 15 x 5mm Red LEDs	SP135 5 x Miniature slide switches
SP2 12 x 5mm Green LEDs	SP136 3 x BFY50 transistors
SP3 12 x 5mm Yellow LEDs	SP137 4 x W005 1-5A bridge rectifiers
SP5 25 x 5mm 1 part LED clips	SP138 20 x 2-2/63V radial elect. caps.
SP6 15 x 3mm Red LEDs	SP142 2 x CMOS 4017
SP7 12 x 3mm Green LEDs	SP143 5 Pairs min. crocodile clips (Red & Black)
SP8 10 x 3mm Yellow LEDs	SP144 5 Pairs min. crocodile clips (assorted colours)
SP9 25 x 3mm 1 part LED clips	SP146 10 x 2N3704 transistors
SP10 100 x 1N4148 diodes	SP147 5 x Stripboard 9 strips x 25 holes
SP11 30 x 1N4001 diodes	SP151 4 x 8mm Red LEDs
SP12 30 x 1N4002 diodes	SP152 4 x 8mm Green LEDs
SP18 20 x BC182B transistors	SP153 4 x 8mm Yellow LEDs
SP20 20 x BC184B transistors	SP154 15 x BC548B transistors
SP23 20 x BC549B transistors	SP156 3 x Stripboard, 14 strips x 27 holes
SP24 4 x CMOS 4001	SP160 10 x 2N3904 transistors
SP25 4 x 555 timers	SP161 10 x 2N3906 transistors
SP26 4 x 741 Op Amps	SP164 2 x C106D thyristors
SP28 4 x CMOS 4011	SP165 20 x LF351 Op Amps
SP29 4 x CMOS 4013	SP166 20 x 1N4003 diodes
SP33 4 x CMOS 4081	SP167 5 x BC107 transistors
SP34 20 x 1N914 diodes	SP168 5 x BC108 transistors
SP36 25 x 10/25V radial elect. caps.	SP172 4 x Standard slide switches
SP37 12 x 100/35V radial elect. caps.	SP173 10 x 220/25V radial elect. caps.
SP38 15 x 47/25V radial elect. caps.	SP174 20 x 22/25V radial elect. caps.
SP39 10 x 470/16V radial elect. caps.	SP175 20 x 1/63V radial elect. caps.
SP40 15 x BC237 transistors	SP177 10 x 1A 20mm quick blow fuses
SP41 20 x Mixed transistors	SP178 10 x 2A 20mm quick blow fuses
SP42 200 x Mixed 0-25W C.F. resistors	SP181 5 x Phono plugs - asstd colours
SP47 5 x Min. PB switches	SP182 20 x 4-7/63V radial elect. caps.
SP49 4 x 5 metres stranded-core wire	SP183 20 x BC547B transistors
SP102 20 x 8-pin DIL sockets	SP186 8 x 1M horizontal trim pots
SP103 15 x 14-pin DIL sockets	SP189 4 x 5 metres solid-core wire
SP104 15 x 16-pin DIL sockets	SP192 3 x CMOS 4066
SP109 15 x BC557B transistors	SP195 3 x 10mm Yellow LEDs
SP112 4 x CMOS 4093	SP197 6 x 20-pin DIL sockets
SP115 3 x 10mm Red LEDs	SP198 5 x 24-pin DIL sockets
SP116 3 x 10mm Green LEDs	SP199 5 x 2-5mm mono jack plugs
SP118 2 x CMOS 4047	SP200 5 x 2-5mm mono jack sockets
SP124 20 x Assorted ceramic disc caps	
SP126 6 x Battery clips - 3 ea. PP3 + PP9	
SP130 100 x Mixed 0-5W C.F. resistors	
SP131 2 x TL071 Op Amps	
SP133 20 x 1N4004 diodes	
SP134 15 x 1N4007 diodes	


RESISTOR PACKS - C.Film

RP3 5 each value - total 365 0-25W	£3.40
RP7 10 each value - total 730 0-25W	£4.65
RP10 1000 popular values 0-25W	£6.60
RP4 5 each value - total 305 0-5W	£4.20
RP8 10 each value - total 610 0-5W	£6.85
RP11 1000 popular values 0-5W	£8.95

2008 Catalogue available £1 inc. P&P or FREE with first order. P&P £1.75 per order. NO VAT Cheques and Postal orders to: SHERWOOD ELECTRONICS, 10 NEWSTEAD STREET, MANSFIELD, NOTTS. NG19 6JJ

Measure, Test & Control

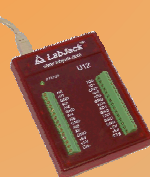PC based
measure
& control
units.
Analogue/
Digital IO,
data
loggers
from £49



Budget
Test
Equipment
Scopes
Multimeters
Function
Generators
from £99



Robot and
Controller
Kits -
Micros,
LCD,
Relay
boards
Free
Software
From £29



PC Weather
Stations
Wind speed,
direction,
temp,
humidity,
rainfall
Free
software
From £59



Learn more at www.audon.co.uk

audon Electronics

www.audon.co.uk | +44 (0)115 925 8412 | Fax +44 (0)115 925 9757

PCB-POOL®

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

1 EUROCARD

(160 x 100 mm)

+ Tooling

+ Photoplots

+ VAT

€49

Price example
Any size and contour possible!

Optional:

- Soldermask
- Fast-turnaround
- Silkscreen
- 4-Layer Multilayer
- 6-Layer Multilayer

FREE LAYOUT SOFTWARE!



Freephone 0800-3898560

Tel.: +353 (0)61 701170
Fax: +353 (0)61 701165
pcb-pool@beta-layout.com

Simply send your files and order ONLINE: **PCB-POOL.COM**

Teach-In 2008

Part Eleven – Randomising values with PICs, plus a Fruit Machine!

JOHN BECKER



IN this final part of *Teach-In 2008*, we examine a concept that is of great benefit to many who write PIC programs for various games applications such as – randomisation.

There are many occasions when games need to periodically acquire values of a random nature, using those values to determine what happens at the next stage of the game. Such values need to be arrived at in a totally unpredictable manner, and minimise the risk of occurring in a repeatable fashion.

We showed in Part 3 a simple form of randomising for the Dice display, and in Part 8 for the Reaction Timing demo, yet another example was used in the Domino game last month. At the end of this part we give an example of a simple ‘One-armed Bandit’ or ‘Fruit Machine’ game that uses the more sophisticated technique described now.

Using discrete electronic components there are various ways of causing circuit responses to random events. Monitoring temperature, light or noise levels and deriving usable values from those is one way in which nature can produce a random trigger event. The problem there is that the derived value will normally only fall within a very small range. There is also the consideration that the detection circuits can become complex, which is not compatible with the basic simplicity of a circuit that is microcontroller and software based.

Demo circuit

Throughout Part 11 we shall use, in whole or in part, the circuit shown in Fig.11.1. Its breadboard layout is shown in Fig.11.2.

The circuit in Fig.11.1 consists of the PIC16F628 connected to an LCD display. Switch S1 is the activating switch. Ignore the switch labelling for this demo. The PIC’s internal 4MHz oscillator is used.

There are two demonstration programs, **TeachInY01.asm** and **TeachInY02.asm**. The former illustrates several methods by which random values can be generated. You select the relevant sections as instructed. The latter is the ‘Fruit Machine’, usable as a standalone program, but which you can also modify if you wish. It is discussed later.

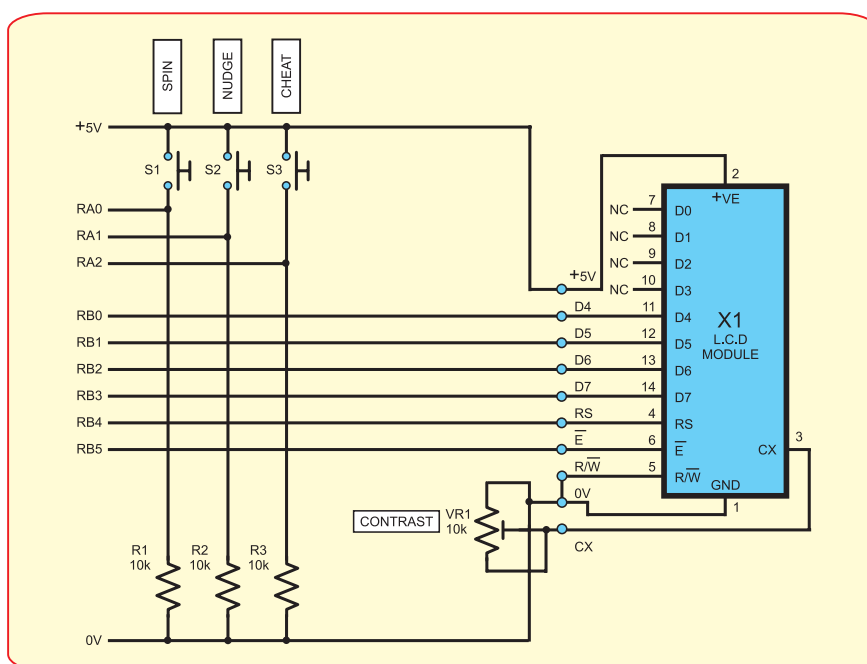


Fig.11.1 Circuit diagram for part 11 demos

The main control section for **TeachInY01.asm** is shown in Listing 11.1. The ‘housekeeping’ initialisation routines have been omitted, but are similar to those used in the previous *Teach-In 2008* demos.

Simple randomising

At the simplest level in a microcontroller design, random numbers can be obtained by the mere act of pressing a switch for a length of time determined by the user, incrementing a counter during the switch press, and then taking the value that exists at the end of the switch press.

Referring to Listing 11.1, switch S1 is monitored via PORTA,0. It is normally biased low and is repeatedly polled to see if it has been pressed:

```
MAIN    btfss PORTA,0
        goto MAIN
```

When it is pressed, there are several sub-routines which can be activated to illustrate how the switch press is handled. In Listing

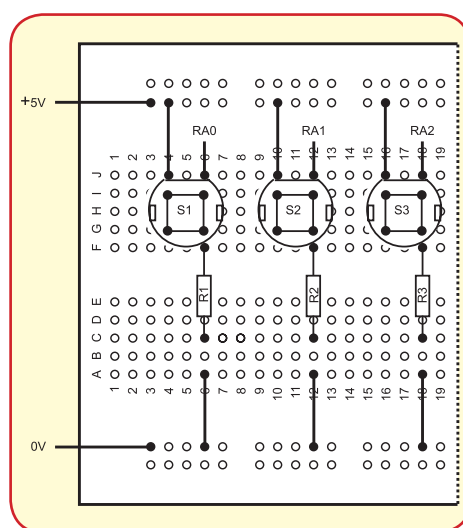


Fig.11.2. Breadboard layout for Fig.11.1

11.1, it is the routine at BYTECOUNT255 which is accessed. You can select the other options by deleting the semicolon in front of the required ‘call’ statement, and inserting a

semicolon in front of the statement you no longer want. You then reassemble the code to a HEX file and program the PIC with it.

The routine for BYTECOUNT255 is shown in Listing 11.2.

When the switch is pressed, counter COUNTLSB increments at the rate at which the PIC is running (1MHz for a 4MHz oscillator) for as long as the switch is pressed.

When the switch is released, the binary count value in COUNTLSB is converted to a decimal format and output to the LCD. What you then do with this value is entirely up to you. Just jotting it down on a pad is probably all you may want to do at present, just so that you can compare the results of several switch presses in a sequence.

As things stand, it is the full value of the 1-byte counter, with a range of 0 to 255, which is shown, using the BIN2DEC and LCD control routines previously described.

Should you wish to slow down the incrementing rate, a delay routine may be called by removing the semicolon in front of **call PAUSIT**.

Value limitation

In a games situation, you may not want the random value to be displayed, in which case simply omit the display commands and make use of the derived value in any way you want.

If you require the random value to be limited to a maximum value below 255, this can be done in several ways. An example of limiting it to a maximum of 15 is shown in Listing 11.3.

Here, the limitation is done by the insertion of the command **andlw 15** (binary 00001111). Other AND values could be used instead, limiting the value to the maximum that can be held in the resulting active bits of COUNTLSB. A command of **andlw 7** (binary 00000111) would result in a maximum value of 7.

Of course, for a maximum value of 7, it is not necessary to use the BIN2DEC routine to convert the value for LCD display, as it is only necessary to OR the value with 48 to convert it for the LCD, as in Listing 11.4.

In this instance, it is also possible to keep the value below 8 by the inclusion of the command **bcf COUNTLSB,3** after **incf COUNTLSB,F**, as in Listing 11.5.

There are situations where you may want to limit the range to a value which cannot be obtained by ANDing or clearing bits. Such would be the case if you wished to create a value predictor for Lotto, where the maximum value is 49. An example of such limitation is shown in Listing 11.6.

Here the count value is constantly checked to see if it has gone beyond 49, ie to 50. If it has, the count value is reset to 0 at this point. Other values could be used instead, as appropriate to the situation.

There may be occasions when you want to arrive at values within a range greater than 255. Here the counter could use two or more bytes in the counting routine, as shown in Listing 11.7, which uses two bytes, COUNTLSB and COUNTMSB. Using two bytes produces a potential maximum of

Listing 11.1

```

MAIN      btfss PORTA,0
           goto MAIN
           call CLRLINE1
           call LCDMSG2

;          call BYTECOUNT7
;          call BYTECOUNT15
;          call BYTECOUNT255
;          call BYTE2COUNT
;          call BYTECOUNT50
;          call BYTECOUNT7A
;          call RANDOMISE

           goto MAIN

```

Listing 11.2

```

BYTECOUNT255  incf COUNTLSB,F

;

           btfsc PORTA,0
           goto BYTECOUNT255
           call CLRLINE1
           call LCD1
           bsf RSLINE,4
           movf COUNTLSB,W
           movwf REGA0
           clrf REGA1
           clrf REGA2
           clrf REGA3
           call BIN2DEC
           call SHOWDIGIT7
           return

```

Listing 11.3

```

BYTECOUNT15   incf COUNTLSB,F
                 btfsc PORTA,0
                 goto BYTECOUNT15
                 call CLRLINE1
                 call LCD1
                 bsf RSLINE,4
                 movf COUNTLSB,W
                 andlw 15
                 movwf REGA0
                 clrf REGA1
                 lrf REGA2
                 clrf REGA3
                 call BIN2DEC
                 call SHOWDIGIT9
                 return

```

65535. The routine could even be similarly extended to four bytes, an enormous value!

All the above routines make use of the length of time that the user keeps the switch pressed. You will also have noticed that the counter is never reset at the start of the switch being pressed. This helps to randomise the value produced. Randomisation is also helped by a phenomenon discussed in a previous part – byte values themselves can take on random values at the moment that a PIC is powered up.

Automatic randomisation

There are situations, though, in which random numbers may need to be generated automatically throughout a program, without the intervention of user-pressed switches.

There are several techniques which could be used, one of which is frequently encountered in purely hardware controlled designs – using shift registers and an XOR gate. The principle is shown in Fig.11.3.

Software can be used to simulate this technique. One way of doing it is shown in Listing 11.8.

In Listing 11.8, the equivalent of four 8-bit shift registers are used (RANDOM1 to RANDOM4), and two XOR gates (XORGATE1 and XORGATE2). The value within the RANDOM(x) bytes is repeatedly rotated left each time the routine at SETRANDOM is called. Selected bits of two of the RANDOM(x) bytes are monitored, and if set, then bits within the XOR gates are also set.

The routine is too complicated to fully describe here, but the Carry flag of STATUS is rotated into the shift register on each rotate left. The Carry flag is also affected by the status of the XOR gates. As you have been told, any left rotation of a byte also rotates the value of the Carry flag in at the 'right' of the rotated byte, and the status of the final bit of that byte is rotated back into Carry.

The result is that the values within the RANDOM(x) bytes change in a pseudo-random fashion each time the SETRANDOM routine is called. The value within any of the RANDOM(x) bytes can be used as the source of the required random value. That value can also be limited to a given maximum prior to it being used by the rest of the program, whatever that might be. Any of the techniques described above can be used to provide that limitation.

In the **TeachInY01.asm** demo program, select **call RANDOMISE** to see the random value generated each time the switch is pressed. The routine's details are shown in Listing 11.9.

Seeding

What may not be obvious is the fact that the value within the RANDOM(x) bytes at power-on could in fact be zero. This is a situation which can never generate a value other than zero. It is essential to ensure that this can never happen.

It is possible, of course, to check the RANDOM(x) bytes for all zeros following switch-on and setting at least one of them to a non-zero value. In a simple program, however, just setting a specified value into the bytes would itself be a non-random event. What is needed is a value which itself changes each time the power is switched on. Such a value is known as a 'seed'.

One way to do this is to have a value held within the PIC's non-volatile memory (EEPROM) which is retrieved at switch on, and then is immediately updated and stored back to the EEPROM as well as being set into RANDOM(x) bytes.

In the long term, there will indeed be repetition of seed values, but this technique does help to enhance the apparent randomisation of overall value generation. Remember that in software, we can only ever use pseudo-random value generation, but extending the repetition range is highly beneficial, reducing the chances of obvious predictability.

In Part 9 we illustrated how the PIC's EEPROM could be read and written to. That technique can be used in connection with acquiring and updating the seed value.

Any 8-bit value of the user's choosing could be set into the basic ASM program, with it automatically being set into the PIC via the HEX file. Each time the program is run, that value would be retrieved, used and updated, say incrementing it. It would be necessary, of course, to ensure that the updated value itself was never zero. But that's easy enough – if it is zero then increment it to 1.

That concludes this section looking at obtaining random values. Let's now look at a practical way in which randomisation is used.

Listing 11.4

```

BYTECOUNT7      incf COUNTLSB,F
                  btfsc PORTA,0
                  goto BYTECOUNT7
                  call CLRLINE1
                  call LCD1
                  bsf RSLINE,4
                  movf COUNTLSB,W
                  andlw 7
                  iorlw 48
                  call LCDOUT
                  return

```

Listing 11.5

```

BYTECOUNT7A      incf COUNTLSB,F
                  bcf COUNTLSB,3
                  btfsc PORTA,0
                  goto BYTECOUNT7
                  call CLRLINE1
                  call LCD1
                  bsf RSLINE,4
                  movf COUNTLSB,W
                  iorlw 48
                  call LCDOUT
                  return

```

Listing 11.6

```

BYTECOUNT50      incf COUNTLSB,F
                  movf COUNTLSB,W
                  xorlw 50
                  btfsc STATUS,Z
                  clrf COUNTLSB
                  btfsc PORTA,0
                  goto BYTECOUNT50
                  call CLRLINE1
                  call LCD1
                  bsf RSLINE,4
                  movf COUNTLSB,W
                  movwf REGA0
                  clrf REGA1
                  clrf REGA2
                  clrf REGA3
                  call BIN2DEC
                  call SHOWDIGIT9
                  return

```

Fruity bandits ho!

Just for the sheer fun of it, we now present a program which is complete in its own right – the One-armed Bandit or Fruit Machine. You can enjoy using this on your own, or even to entertain your friends.

The program uses the same circuit and breadboard layout as before, but now switches S2 and S3 are brought into use, named as S1 Spin, S2 Nudge and S3 Cheat! The program is in **TEACHINY02.asm**.

The program only roughly follows the typical structure of a real gaming machine of a similar nature. It effectively has three spinning wheels, represented by LCD display numbers that change at the top left of line 1. For simplicity, there is a cycle of four numbers for each wheel, 0 to 3,

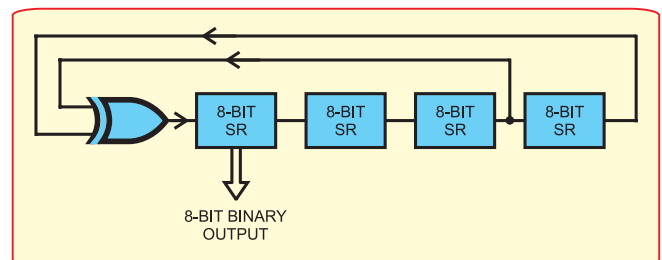


Fig. 11.3. Shift register randomisation principle

although this can be increased by the user if preferred, using one of the techniques described earlier.

At each press of the Spin switch, a jackpot value is incremented, representing the value that could be won when all three wheel values are identical. The 'wheel' numbers cycle through the three counters used, and are displayed on the LCD. They change so fast that the eye never sees the actual detail. When Spin is released, the counter values stop changing and their detail is shown.

The software immediately checks if all three displayed numbers are the same. If they are, the value of the jackpot is added to a total and the message WINNINGS xxx appears, where xxx represents the total won since the program was switched on. If it has been won, the next press of Spin clears the jackpot display, to restart from a value of 1.

If the jackpot has not been won, the numbers are checked to see if any two are the same. If they are, you can then push the Nudge switch to spin the wheel which has a value different to the other two. The spin continues for as long as the switch is pressed, again the value is displayed on the screen at a rapidly changing rate. On release of the switch, the cycling of the active counter ceases and the value now available can be seen. If the three values are now the same, you win the jackpot.

Nudge, nudge

If the jackpot has not been won the simple message NO LUCK THIS TIME! is shown and the jackpot and totals values remain unchanged.

Jackpot total scoring is affected not only by the value within the jackpot, but also by the value of the winning number, 1 for 1, 2 for 2, 3 for 3, and 10 for 0.

The Cheat switch allows you to always win the jackpot when the program provides the Nudge option. Pressing the switch always ensures that the 'wrong' number becomes the same as the other two, so ensuring a win. If you were to build this circuit on stripboard and house it in a box, you could have the Cheat switch on a lead external to the box and hidden somewhere. You could then press this switch unseen while pretending to press the Nudge switch, disguising from your friends that you are in fact cheating!

Possible changes

There are changes to the program that you might like to make. You could increase the number of values that are cycled through the counters, as described above. This will make it harder for a winning combination to occur (if you are not cheating!). The scoring values at any win could also be increased quite readily. The incremental value of the jackpot can also be changed to a higher value with a spot of minor program modification.

You could also allocate symbols other than the counter values themselves to be shown. For example, via a look-up table, you could allocate alphabet letters to be shown instead of the numerals. In Part 10 last month we also showed how you can create your own LCD symbols for display in place of the actual numerals.

Be adventurous, have a go at changing this program to suit your own needs. What you do and how you achieve it is entirely over to you – good luck!

PIC name again

That really ends this *Teach-In 2008* series, but one final point is worth making.

Since the series started, it has come to light that Wikipedia (http://en.wikipedia.org/wiki/PIC_microcontroller) states that:

The original PIC was built to be used with GI's (General Instrument) new 16-

Listing 11.7

BYTE2COUNT	incfsz COUNTLSB,F goto BYTE2 incf COUNTMSB,F
BYTE2	btfsc PORTA,0 goto BYTE2COUNT call CLRLINE1 call LCD1 bsf RSLINE,4 movf COUNTLSB,W movwf REGA0 movf COUNTMSB,W movwf REGA1 clrf REGA2 clrf REGA3 call BIN2DEC call SHOWDIGIT6 return

Listing 11.8

SETRANDOM	clrf XORGATE1 clrf XORGATE2 btfsc RANDOM1,2 bsf XORGATE1,0 btfsc RANDOM4,6 bsf XORGATE2,0 bcf STATUS,C movf XORGATE1,W xorwf XORGATE2,W btfsc STATUS,Z bsf STATUS,C rrf RANDOM1,F rrf RANDOM2,F rrf RANDOM3,F rrf RANDOM4,F return
-----------	---

Listing 11.9

RANDOMISE	call SETRANDOM call LCD1 bsf RSLINE,4 movf RANDOM1,W movwf REGA0 movf RANDOM2,W movwf REGA1 movf RANDOM3,W movwf REGA2 movf RANDOM4,W movwf REGA3 call BIN2DEC call SHOWDIGIT1 return
-----------	--

bit CPU, the CP1600. While generally a good CPU, the CP1600 had poor I/O performance, and the 8-bit PIC was developed in 1975 to improve performance of the overall system by off-loading I/O tasks from the CPU. The PIC used simple microcode stored in ROM to perform its tasks, and although the term wasn't used at the time, it shares some common features with RISC designs.

In 1985, GI spun off their microelectronics division, and the new ownership cancelled almost everything – which by this time was mostly out-of-date. The PIC, however, was upgraded with EPROM to produce a programmable channel controller.

Microchip Technology does not use PIC as an acronym; in fact the brand name is PICmicro. It is generally regarded that PIC stands for Peripheral Interface Controller, although GI's original acronym for the initial PIC1640 and PIC1650 devices was Programmable Interface Controller. The acronym was quickly replaced with Programmable Intelligent Computer.

Further reference

So, now over to you – enjoy using your PICs and the programs you write for them. And don't forget to read *PIC 'n Mix*, the regular column in *EPE*, which covers many aspects relating to PICs.

PIC32 Starter Kit Review

by Mike Hibbett



Microchip's newest processor – not one for beginners

Despite their line up of hundreds of PIC device variants, it's not often that Microchip introduces a completely new range of processors. In November 2007, however, that's exactly what happened. Microchip introduced the PIC32 family of 32-bit processors. There are currently ten variants available, with another seven on the horizon (which, most importantly, will add USB support to the family.)

THE PIC32 is significantly different from any previous processor available from Microchip. In fact, it's not even a Microchip processor – it's a MIPS32 M4K processor, licensed from a company called MIPS. MIPS created the M4K processor as a design specification, and licensed it out to companies who then add it into their own chips – as Microchip have done in this case.

If you would like to understand the background of this processor, take a look at www.mips.com

PIC32 features

The most interesting aspect of the PIC32 is its CPU databus size – 32 bits. This means that the processor can deal with very large numbers in a single instruction, making it very fast. Not only this, but it runs at 80MHz – twice the speed of the PIC18 family, enabling it to perform functions that no other PIC processor has been able to do before – such as MP3 decoding for example.

The new PIC32 parts introduce, for the first time, *USB OTG ports*. OTG means 'On The Go', referring to a mode which enables the processor to act as a USB host device. This means that

a PIC project could connect to and control another USB device, such as a web camera, with suitable software. This is a feature engineers have been crying out for, so we should see some interesting applications created with these new processors!

And, of course, being Microchip products, these devices are available through the usual hobbyist-friendly suppliers such as Farnell, RS Components and Digikey.

On the downside – and this is what will make the parts difficult for hobbyists to use – the devices are only supplied in small pitched, flat surface-mount packages with a lead spacing of 0.5mm. Unless you are highly experienced with SMD soldering techniques, these parts are virtually unsolderable and, therefore, are going to be difficult to build into your own design. We see a blossoming market for third party suppliers to produce small PCBs with the processor fitted to it and tracks out to standard 0.1 inch header holes.

Another issue that is going to put off many hobbyists will be the fact that the PIC32 is an extremely complex processor – far more complex than

any of the previous processors from Microchip. This is a serious processor, for serious work. It is designed to be programmed in C, and coupled with a high level operating system or RTOS.

On the other hand, this will be a wonderful device to push your assembly programming skills to the next level, if you like a challenge! A link to the datasheet for the processor can be found at the end of this article.

Starter kit

To help users become familiar with the device, Microchip has produced a small, low-cost product called the PIC32 Starter Kit, which we will be looking at in this article.

The starter kit contains a small PCB holding a PIC32 processor, a USB debug interface, some LEDs, switches and a connector for attaching the board to expansion modules (that you will no doubt be able to buy from Microchip or third parties). The USB interface is only for programming the PIC32 – it connects to a PIC18F4550, which acts like a PicKit2 programmer unit located on the PCB itself. The PIC32 device on

the starter kit has no USB functionality unfortunately, so you will not be able to make use of the interface in your applications.

Supplied with the board is a USB cable and a CD with tutorials and development tools. The board is powered directly by the USB cable, so you have everything you need to write, debug and test software on 'real' hardware. The photo below shows the full kit contents.

Software installation

As with all USB devices, it is important to install the software first before plugging the hardware into a USB port on your PC. If you don't, then the PC will not recognise the USB interface on the PIC32 board, and will disable access to it. So we left the PCB to one side, popped in the CD and followed the on-screen instructions.

Immediately we hit a problem. A pretty installation screen appeared, prompting 'Click to install from CD'. When this was clicked the Firefox web browser popped up, displayed a blank screen and nothing further happened.

Closing the web browser revealed the problem – displayed at the bottom of the installation menu is the text 'Firefox users: Navigate to the

CD root directory and launch /fscommand/pic32_sk_installer.exe'.

They have gone to the (excessive) trouble of using flashy graphics and a web browser to install the software, but not provided support for the second most popular web browser in use. Where is the logic in that? Fortunately, installation from the fall-back installer worked perfectly.

Supplied software

The installation process loads the MPLAB IDE v8.0 onto your hard drive, and adds the MPLAB C32 compiler and MPLAB ASM32 assembler, both developed specifically for the PIC32 processor. The installed files can be found under *C:\program files\Microchip*. It's also worth taking a look through the newly installed directories, making a note of documentation found in .pdf and .txt files.

Several example projects are included to help you get started, and one in particular, located in *C:\Program Files\Microchip\pic32_solutions\pic32mx_starter_kit\sample_code\StarterKitTutorial*, has an accompanying multimedia tutorial, which can be found in: *C:\Program Files\Microchip\pic32_solutions\pic32mx_starter_kit\getting_started_flash_tutorial*.

This is an excellent tutorial for those who are completely new to using MPLAB, and gives a starting point for editing and building new software within a few minutes. For those who are new to MPLAB, refer to the series of articles on MPLAB that we presented in the magazine in the June to September 2007 issues. They will help flesh out the details.


Having installed the software from the CD, you should immediately go and check for any new updates to the software on the Microchip website. At the time of writing MPLAB has progressed to v8.10, and as this is a new processor from Microchip, it is well worth making sure you are current with their development tools. Ensure you check for updates to the C32 compiler and ASM32 assembler program too.

For some strange reason no processor datasheet is included on the CD, so you will certainly want to download that from the Microchip website. See the references at the end of the article for its location.

Alternative software

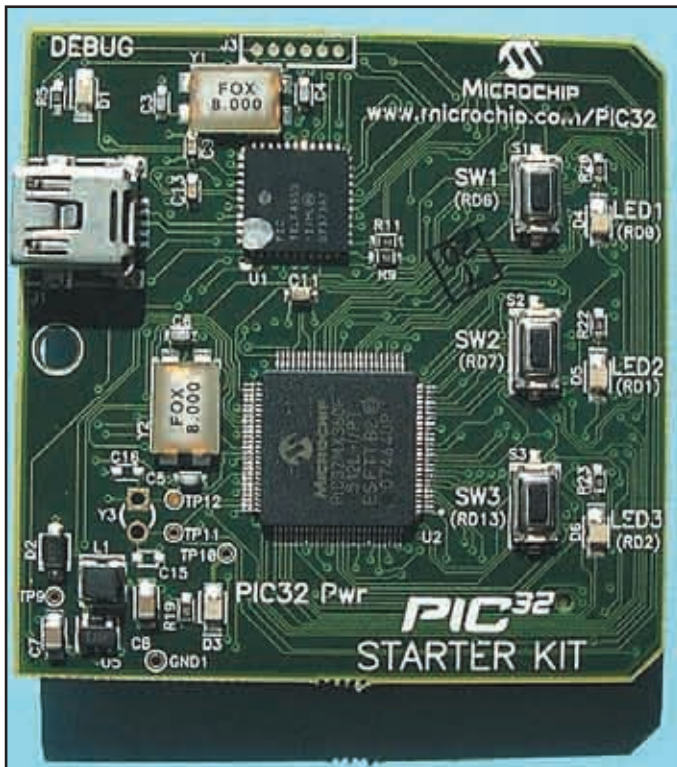While the MPLAB development environment supplied on the CD is a full and free product, the C compiler MPLAB C32 is not. It is limited to programs no greater than 64KB in





Topside view of PCB



Underside view of PCB

size, which may become a serious limitation when you consider that the PIC32 device has a massive 512KB of flash memory!

The full C32 compiler can be purchased, of course, but it costs several hundred pounds which may be an issue for hobbyists. Fortunately, several groups of engineers have announced on the Internet that they are working on producing an unrestricted compiler suite for the PIC32 – we will announce progress as it happens. (MPLAB C32 is itself based on GCC, a free open source compiler. The C libraries for PICC32 however are not part of GCC, and the ‘free’ compiler is useless without a library. It’s the library that people are working on creating.)

Hardware

The two sides of the starter kit board are shown above. It’s a compact little board, and is very portable with its DVD style case. Handy for shuffling between work and home.

Unlike the PicKit2 Demo board, which comes with a small prototyping area and 0.1 inch pitch holes for all I/O signals, the PIC32 starter kit board is equipped with three pushbutton switches and three LEDs. No UART access, no I/O pins, no solder pads or

holes. Only a specialised 120-pin connector on the rear for expansion.

So to get any form of circuitry connected up to the processor you will need to find the matching connector and build an expansion board. Once again, however, we hit a problem – the connector pins are on a very fine pitch (0.5mm, again) and present the same soldering challenges as the processor itself. Once again, expect third party companies to start selling expansion PCBs to solve this problem.

Microchip produce their own range of expansion boards that mate with the starter kit PCB. The PIC32 I/O Expansion Board DM320002 brings the processor signals out to a variety of connectors and headers, but it isn’t cheap – it adds another £36 to the cost of getting a development system together.

Alternatively, the MA320002 board is a small PCB fitted with just the processor that brings the processor pins out to standard 0.1 inch pitch header strips – a lot easier to work with, but you will need to provide your own programming interface connections. These are relatively cheap – £12 from RS Components, compared to £25 for the starter kit.

Unless you are in a hurry to get a system up and running, we would

suggest the MA320002 board is the way to go – unless you are happy to solder 0.5mm lead pitch packages, in which case you can hand solder the PIC32 to your own PCB. Good luck with that though, it takes considerable skill!

The final option for getting to the I/O is to obtain a mating connector, and build your own expansion board. The part required is manufactured by Hirose, part number CL570-0203 or FX10A-120S/12-SV(71). It’s available from Digikey.

Overall, we were initially disappointed with the PIC32 starter kit, since by itself, with its limited I/O capabilities, it doesn’t provide much more than a software simulator – not very exciting. But it’s still a good starting point for the adventure of learning to program the device, an adventure which is a considerable challenge. But for some projects, however, the challenge may well be worth the effort!

References

Hirose connector datasheet: www.hirose.co.jp/catalogue_hp/e57000028.pdf

PIC32 Datasheet: www.microchip.com/stellent/idcplg?IdcService=SS_GET_PAGE&nodeId=260

Ingenuity Unlimited


Our regular round-up of readers' own circuits

WIN A PICO PC-BASED OSCILLOSCOPE WORTH £799

- 200MHz Analogue Bandwidth Dual Channel Storage Oscilloscope
- Spectrum Analyser
- Frequency Meter
- Multimeter
- USB Interface.

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC-based oscilloscope could be yours.

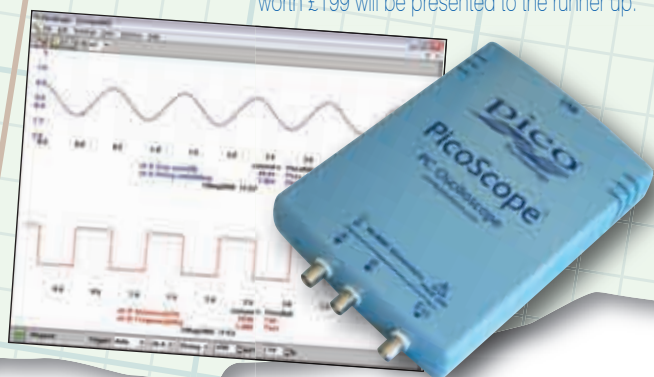Every 12 months, Pico Technology will be awarding a PicoScope 3206 digital storage oscilloscope for the best IU submission. In addition a PicoScope 2105 Handheld 'Scope worth £199 will be presented to the runner up.



We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas must be the reader's own work and must not have been published or submitted for publication elsewhere.

The circuits shown have NOT been proven by us. Ingenuity Unlimited is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. Please draw all circuit schematics as clearly as possible. Send your circuit ideas to: Ingenuity Unlimited, Wimborne Publishing Ltd., Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Email: editorial@epemag.wimborne.co.uk. Your ideas could earn you some cash and a prize!

Noise Generator – The other side of golden?

USUALLY, the aim of component manufacturers is to eliminate noise from their components. Thus, as electronics technology has advanced, so has noise in components become scarce. In the 1960s and 70s there still were quite a few noisy components around – which are now hard to find. Here, though, is a 'genuine noise' circuit built of components which should hopefully be readily available.

But first, why make noise? Here are a few examples of its uses. It may be useful for simulating 'chaotic' sounds such as 'ocean surf', or 'rushing wind'. Or it may be useful for injecting a genuinely random signal into a circuit. The author has found it useful for 'busting through' frequency lock in metal detector designs by injecting it into the 'zero beat frequency' zone of such a circuit, thus improving sensitivity.

Noise circuit

In this circuit (Fig.1), noise is generated by IC1, a 5V micropower regulator. Capacitor C1 stabilises the noise source, IC1. C2 is a DC-blocking capacitor, while R1 and C3 form a 15kHz low-pass filter, with a frequency calculated by the formula $f = 1 / (2\pi R1 C3)$.

The low-pass filter is essential to prevent the high frequency component of the noise from overheating amplifier IC2. With the filter in place, about 80mV noise is generated. Without it, an excessive 500mV

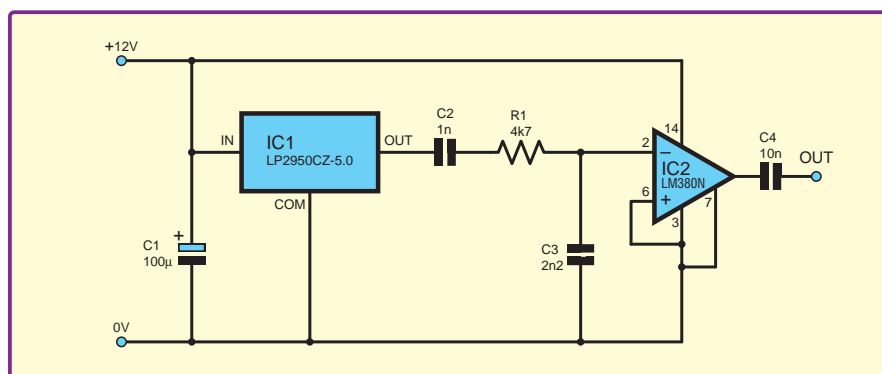


Fig.1. Circuit diagram for the simple Noise Generator

is generated. Capacitor C4 is both a DC-blocking capacitor, and provides further protection for IC2 from overheating.

Not every preamplifier or amplifier will serve the purpose in combination with IC1. That is, IC2 cannot simply be substituted for any preamplifier or amplifier. An example of a suitable substitute is the CMOS 4069 hex inverter, which fits the bill when wired as a high gain preamplifier. The circuit draws about 13mA at 12V.

Thomas Scarborough,
Cape Town, South Africa

INGENUITY UNLIMITED

BE INTERACTIVE

IU is your forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly a prize.



LED brightness and switching inductive loads

Recently, *Jimkirk* posted details of one of his circuits on the *EPE Chat Zone* (via www.epemag.wimborne.co.uk). The circuit uses a phototransistor to switch a relay via another bipolar transistor. His circuit was not working, but at the time of writing it is not entirely clear why; it could be, for example, due to faulty components, the wrong type of components (eg relay specification), or insufficient gain in the switching transistor. However, one definite problem was noted by user Ant – the relay did not have a ‘protection’ diode connected across it. Also, on this topic is an earlier post from *Echase*:

If you switch a relay, motor or other inductive load with a bipolar transistor, it is usual to connect a diode in reverse across the load to absorb the switch off spike, to stop it damaging the transistor... If you use a MOSFET it usually (always?) has an internal reversed diode across the drain and source junctions. Does this diode provide the same function as the above diode, even though it's not in the same position in the circuit, meaning that the above is not now needed?

We will look at the topic of switching inductive loads later in this article. First, we will consider a question posted by *Techno* on the Chat Zone. He asks:

I am connecting 10 white LEDs in parallel – I want to use a 24V DC supply. What value resistor must I use so that I can get the LEDs as bright as possible without damaging them?

The first point we have to make is that connecting the LEDs in parallel is not a good idea. This is because it will lead to possible variation in brightness between LEDs and may also lead to excessive power consumption in the resistors used to set the LED current. We will look in detail at why this is, and suggest a better approach, before returning to look at inductive load switching.

LED brightness

It is the *current* through an LED, not the voltage across it, which determines its brightness. Two individual LEDs of exactly the same type will produce the same illumination with the same forward current (I_F), but may have different forward voltage drops (V_F) at this current.

The variation in voltage drop between individual devices may be in the range 0.1 to 0.3V for typical ‘ordinary’ coloured LEDs. For high power and white LEDs the range

may be much larger. This is a key fact that needs to be considered when designing LED drive circuits. This is illustrated in Fig.1, which shows possible forward characteristics for two LEDs of the same type.

Two LEDs driven in parallel, using a single current limiting resistor, is shown in Fig.2. This circuit forces the LEDs to have the same forward voltage drop, which means that their forward currents and hence brightness may be very different (see Fig.1).

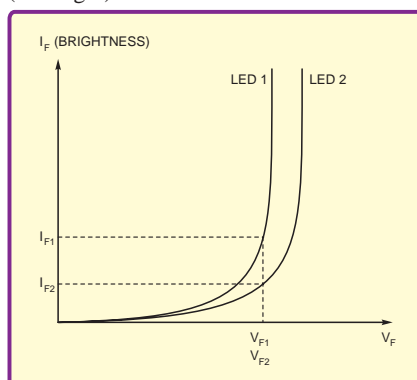


Fig.1. With the same forward voltage the LEDs may have different forward currents and hence different brightnesses.

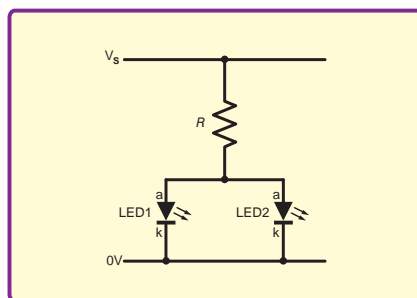


Fig.2. Driving two LEDs in parallel

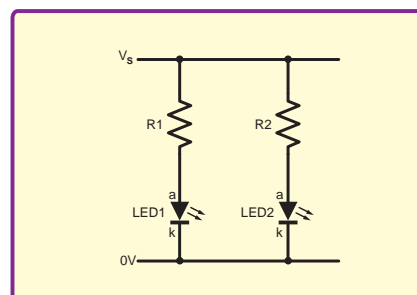


Fig.3. Two LEDs with separate current-limiting resistors

Fig.3 shows two LEDs with separate current-limiting resistors. However, we can still get problems with variation between individual devices resulting in varying brightness. An example will help explain this.

Assume we have white LEDs with LED1 having a forward voltage drop of 3.6V at a forward current of 20mA. If the supply (V_S) is 5V, we have $R1 = 70\Omega$ so that $R1$ drops 1.7V and we have 3.6V across LED1. If LED2 is also connected with $R2 = 70\Omega$, but has, say, a forward voltage drop of 4.0V (due to variations in individual device characteristics), then the current in LED2 will be 14.3mA. The difference in current may show up as a noticeable difference in brightness.

If we use a higher supply voltage, the brightness variation problem is reduced. For example, consider a 24V supply. Let's say we have $R1 = 1k\Omega$ to get about 20mA (20.4mA) with a 3.6V drop across LED1 so that the LED is driven as before. Now consider LED2 with a 4.0V drop again and $R2 = 1k\Omega$. The current in LED2 is 20.0mA, almost the same as LED1, so they should appear equally bright.

This comes at a high price though – the total power dissipation in the two current limiting resistors is about 0.8W in the second example, which is almost twenty times higher than in the first example. The second circuit is very inefficient and would not be very suitable for battery powered operation.

In series

The circuit in Fig.4 shows three LEDs driven in series. The current through the LEDs must be equal so their brightness will be equal.

A potential difficulty with this circuit is that a relatively high voltage is required to drive the series chain. For 10 white LEDs we would typically need about 30V to 45V depending on the forward voltage drop. In any case, more than the 24V supply that Techno wants to use. White LEDs have typical forward voltage drops ranging from about 3V to about 4.5V, depending on the type of LED used, although lower drops may occur for individual devices or if relatively low currents (and hence brightness levels) are used.

For a large number of LEDs, a compromise between parallel and series connection can reduce the need for a large supply voltage. This is illustrated by Fig.5, where 10 LEDs are connected in two groups of five in series. This would be suitable for driving the 10 LEDs from a 24V supply, as we would expect the groups

of five LEDs to have a total voltage drop in the range 15V to 23V. The choice of R depends on the expected forward voltage drop V_F at the current used I_F , which could be obtained from the manufacturer's datasheet or by measurement if you already have the devices.

The value of R is calculated using Ohm's law, using the LED current and the difference between the total LED drop and the supply. Thus, for Fig.5, $R = (V_S - 5V_F) / I_F$. For $V_S = 24V$, $V_F = 3.6$ and $I_F = 20mA$ we get $R = 300\Omega$, with a power dissipation of 180mW in the resistors (Power = I^2R).

Maximum brightness

To respond to the final part of Techno's question, that of achieving maximum brightness, the answer has to be 'read the datasheet'. This will provide information on the maximum forward current and hence maximum brightness levels.

The maximum current will depend on ambient temperature and will decrease at high temperatures (eg above 50°C). Again, the exact details depend on the type of LED used. For high power LEDs, operation at maximum brightness may require the use of a heatsink.

The preceding discussion indicates that we can drive a large number of LEDs with even brightness if we have a high supply voltage. Techno is fortunate that the 24V he has available should be sufficient for what he requires.

Often this is not case, with, for example, 3V battery supplies being common. In such cases, therefore, it is necessary to generate a high voltage to drive the LEDs in series, usually with constant current control to set the brightness. There are a number of ICs which perform this function, and one of these, the MAX8596X, was discussed in detail in *Circuit Surgery* in the July '08 issue (pages 60-62).

Switching inductive loads

We now return to the issue of switching inductive loads. When current in an inductive load, such as a relay or solenoid, is switched off, the magnetic field, which had been established by the supplied current, collapses rapidly inducing a reverse voltage known as the *back-EMF* or *inductive kick*. This may result in voltages large enough to damage or destroy the semiconductor devices used to switch the load. The more rapid the change in current as the inductor is switched off, and the larger the inductor value, the greater the back-EMF generated.

The usual method of preventing back-EMF from causing problems is to place a diode (sometimes called the *freewheeling diode*, *flyback diode* or *snubber diode*) across the inductor, as shown in Fig.6. The term *clamped inductive load* is also used in this situation. This diode is reverse biased when the power switching device is on, but is forward biased by the back-EMF; so the diode dissipates the power or feeds it back to the power supply. Obviously, the freewheeling diode must have sufficient switching speed, and power handling capacity, to cope with the energy from the back-EMF.

So, as Echase asks, why do some power MOSFET circuits not depict freewheeling diodes? In power MOSFETs, as in other

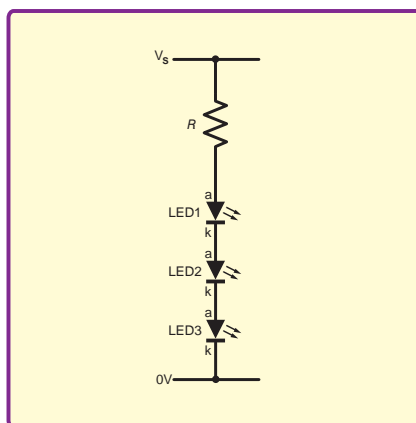


Fig.4. Driving LEDs in series ensures the same forward current, but requires a higher drive voltage.

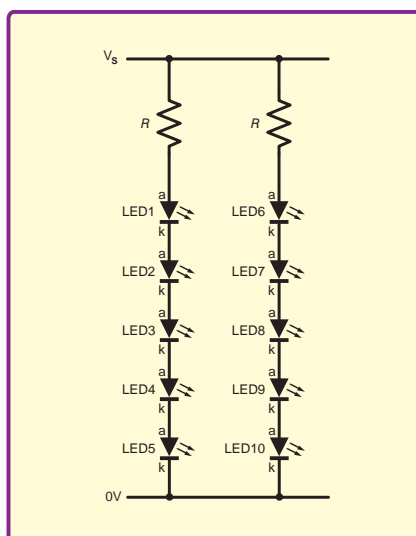


Fig.5. Driving LEDs in series/parallel groups

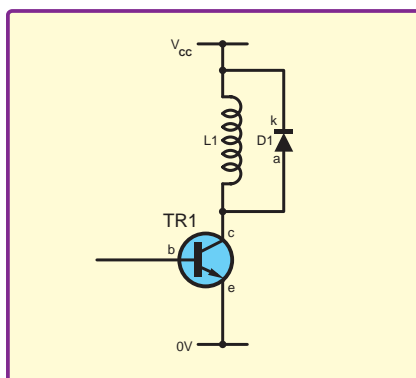


Fig.6. Using a diode to protect a transistor switching an inductive load

semiconductors, the reverse voltage spike from the inductor switching induces avalanche breakdown causing high current flow through the device and therefore high power dissipation, with associated temperature rise, and potential destruction of the device.

Some power MOSFETs are designed to withstand a reasonable amount of avalanche energy and can therefore be used to switch inductive loads, without a protection diode across the load (ie unclamped inductive loads). These devices are often described as *avalanche rugged*,

and their capabilities are characterised in terms of their single-shot and repetitive avalanche ruggedness, usually in terms of maximum avalanche energy, or by safe operating area (SOA) curves of maximum avalanche current against time duration.

As usual, datasheets should be consulted to determine the suitability of a device to the required application. Manufacturers also publish application notes giving detailed background information on MOSFET avalanche ruggedness. For example AN-1005 from International Rectifier (www.irf.com) and AN10273_1 from Philips Semiconductors/NXP (www.nxp.com).

Body drain diode

Echase also mentioned the diode which is often depicted between the drain and source on power MOSFET schematic symbols. This is the 'body-drain' or 'parasitic' diode, which is an intrinsic part of the MOSFET's structure. Fig.7 shows power MOSFET symbols that includes these diodes.

The integral body-drain diode in a power MOSFET can sometimes be used as a freewheeling diode when switching inductive loads. The diode conducts when the reverse polarity back-EMF voltage is applied to the device, preventing over-voltage conditions from damaging the MOSFET.

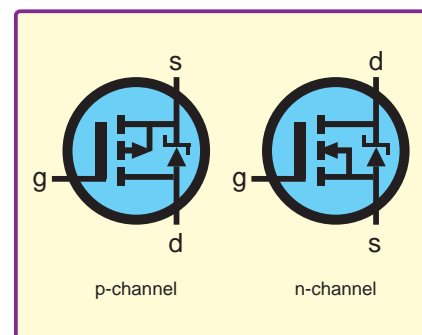


Fig.7. Power MOSFET symbols showing an internal parasitic diode

Power dissipation, for a given current, is higher in 'reverse' conduction via the body-drain diode because the forward voltage drop across the diode is larger than the usual drain to source voltage drop when the device is conducting in the normal way. The device may, therefore, not be able to sustain this condition for long without being destroyed by the heat generated. Hopefully, short-lived inductive kicks will not produce sufficient heat to damage the device.

The current handling capability of the integral body-drain diode is typically as high as that of the transistor itself. However, in applications requiring high frequency switching the intrinsic diode does not have high enough performance and an external diode must be used.

A key problem is that the internal diode does not have a fast enough recovery time; which means it does not switch off fast enough. In some circuits this can lead to short circuit conditions when one MOSFET switches on as another switches off.

Take care when reading power MOSFET schematics to check whether an external high speed diode or the internal body diode is depicted.

Interfacing PICs to the Internet

This month we start on a series of articles that are close to this author's heart – hooking up a microcontroller to the Internet, via an ethernet interface.

The subject is vast and covers a wide range of complex topics. Fortunately, Microchip have made it easy – very easy in fact – to wire up a PIC processor to an ethernet interface, get hooked up to the Internet and explore the possibilities.

Connecting a microprocessor to the Internet opens enormous opportunities, some of which do not become apparent until you start building projects that connect to it. Examples of what you can do with a simple PIC microcontroller connected to the Internet include:

- Checking for email
- Polling a remote sensor
- Remote control of equipment
- Publishing sensor information
- Send messages to your mobile phone
- Decoding Internet radio stations

The list could go on, and new, innovative services are being made available on the Internet at a rapid rate.

Information published on the Internet can be made private, accessible only by password, or publicly available – the choice is yours. By default, access is open and information can be viewed by anyone, so bear that in mind when experimenting.

Internet viruses

It is normal these days to be rather paranoid about connecting a computer to the Internet – computer viruses abound, with new ones reported almost weekly. A PIC processor connected to the Internet is not, fortunately, going to suffer from such problems, as computer viruses are designed to run on PCs only and have no way of 'infecting' a home-grown microcontroller project.

At worst, someone can connect to your device and use it, but they won't be able to corrupt the device and leave a malicious program. Not so with a PC! It's really pot-luck that a PC connected to the Internet does not get infected these days.

So what exactly is ethernet, and how does it relate to the Internet?

ARPANET

Before discussing ethernet, let's take a look at the Internet. The Internet was first conceived at the end of the 1960s as a research project set up by DARPA,

a division of the American Department of Defense, to find a way to hook up the various mainframe computers at academic and defence contractor sites across the country. It's an incredible story, too big to give full justice to here. In those days the network was called ARPANET, but it later became the Internet, in recognition of the fact that the system became a 'network of interconnected networks'.

What the designers realised while they were developing the network infrastructure was that a common means of exchanging information between computers was required. Until that point, mainframe computers had their own, manufacturer-specific means of communication. So a computer from ICL could not communicate with one from Honeywell.

To solve this problem the designers developed a protocol for exchanging information, called TCP/IP. In those days the term 'protocol' had never before been used in a computing context, so while it is a common term today in computing it was a novel use of the word then.

In a nutshell, TCP/IP is a set of standards that define how computers connected to each other in a large network can exchange information between themselves reliably. It does not explain or even refer to how the data will be transferred – the electrical connections between the computers – just how connections can be established, maintained, and information exchanged without loss or corruption. The electrical connections were considered to be handled by a 'lower layer' of software below TCP/IP.

Layered approach

This 'layered' approach to software extended to the design of TCP/IP itself. TCP/IP is really two acronyms, TCP standing for 'Transport Control Protocol' and IP standing for 'Internet Protocol'. IP is the layer of software designed to transport data from one computer to another, while TCP is the protocol which provides *reliable* exchange of data. TCP sits on top of IP, and any computer application that wants to exchange information reliably with another computer would call functions within the TCP software library to do it.

TCP/IP provided the lower levels of software to allow computers to connect, but at the time of its inception no software existed to actually *use* it. This was the beginning of network computing and these were ground breaking days – as the engineers involved in the work soon realised.

As more and more computers became connected to the ARPANET, so more computer scientists and engineers were exposed to it, and soon hundreds of skilled programmers started finding new ways to use it. Programs such as *Finger*, *Archie*, *Gopher*, *ftp*, *Telnet* and the ubiquitous *email* were developed to exploit the new frontier of interconnected computers, and some of these programs still persist today (email being the obvious one!).

In those days, the ARPANET was a completely open network – the idea of password protecting a computer from rogue access was unheard of, and largely unnecessary. The computers cooperating in the ARPANET were sited at defence contractors or selected universities, and security was mostly self-policing. It's only as recently as the late 1980s that restrictions on access to services started to become password protected. The idea of an open mainframe computer system would be ridiculous today.

During the early 1980s the ARPANET extended beyond the USA into European universities and beyond. By the middle of the 1980s access into ARPANET (the Internet as it was now being called) came into the reach of ordinary citizens through ISPs – internet service providers.

In those days, ISPs were forward thinking companies who recognised the increasing demand for access to the Internet, and started wiring up large numbers of modems between their corporate Internet access and the public telephone system. Users could dial into the company's telephone system, be connected to a modem and connected onto the Internet. Users' computers were connected to the Internet only while they were dialed into the ISP's modem, which was something one only did for a few hours a day (and usually, annoying the rest of the household!).

Broadband

By the end of the 1990s an alternative to dial-up Internet access became available – broadband. Broadband offered three significant improvements over dial-up access. First, it didn't interfere with your normal voice telephone. Improvements in digital telephone exchange systems meant that the high frequency broadband signals could be carried over the telephone wires at the same time as voice signals, meaning that you no longer annoyed the rest of the household.

Second, data rates jumped significantly from the 56K bits/s available from dial-up to rates over 2M bits/s. Finally, the feature

that is most useful to us, is that broadband services were provided full time – the charge was a flat monthly connection fee, not by the minute that you are connected.

That final point significantly changed the way people used the Internet. The Internet was no longer something that you had to dial into, and wait a few minutes to access while the computers connected to each other. The Internet was there, all the time.

It became a pervasive presence in the house, with information and communication with others available instantly. Broadband access was fast, and did not use a serial link between the modem and the PC – it required something faster, and the main interface technology that came to dominate was Ethernet.

Ethernet

Ethernet is a standard for physical interfaces between computers. It was developed back in the mid 1970s, almost in parallel with the development of the ARPANET. In those days, serial links such as RS232 were the norm, designed to connect devices such as teletype terminals and printers to a computer. These were slow links, running at a few hundreds or thousands of bytes per second.

As the complexity of peripheral devices increased (such as the introduction of colour, graphical terminals) it became apparent that a faster means of connecting multiple devices together was needed. Ethernet became the dominant standard. A fitting coverage of the development of Ethernet is also, sadly, beyond the scope of this article (if you know of a good book on the subject, do let us know!)

Ethernet started as an expensive solution compared to lower speed serial interfaces, but as its usefulness became apparent and adoption increased, prices plummeted. The standard has improved over the years, with interfaces remaining backward compatible with the earlier, slower ones while still using the same physical interface.

These days, computers are shipped by standard with a 100M bits/s or 1G bits/s ethernet interface, which still supports older 10M bits/s devices. As we will see in later articles, this last point is quite important – the ethernet interface devices available from Microchip only support connection to other devices at 10M bits/s.

On the uptake

The exponential increase in the availability and uptake of broadband Internet connections by home users is what makes the subject of this series of articles relevant. It's been possible to create small, relatively low cost microcontroller projects that connect to the Internet for over 15 years – but without easy, full-time access to the Internet there has simply been no point. In the past, you would have needed a computer to dial into the Internet, and you would have needed to connect your microprocessor system to the computer to connect onto the Internet. In practice, the microcontroller would have simply been a peripheral device on the PC.

These days, however, a broadband connection to the Internet is provided by a high speed modem that has several ethernet

interfaces free, to allow multiple PCs to be connected. If your microcontroller project has an Ethernet interface you no longer need the PC to be switched on – you simply connect it to the modem, and the world is suddenly at your finger tips!

With today's 'all pervasive' Internet, you also have easy access to your device remotely. You can connect to the Internet from work, in libraries or Internet cafes anywhere in the world. And once connected to the Internet, you can access your device, which may be at home or some other distant location.

Using a small home-built 'Internet enabled' device has additional benefits too. Power consumption is going to be significantly lower than a PC (300 milliwatts rather than the 150 watts of a typical PC), which is a significant consideration in these days of increasing energy costs.

The security issues are much better too – a PC left connected to the Internet is vulnerable to attack from computer viruses and hackers, while a PIC based device will not be. You could implement an Internet enabled sensor monitoring system without having to worry about someone placing rogue software onto your computer that might reveal sensitive personal data.

The Web

Throughout this whistle-stop tour of the history of the Internet we have missed out the most significant development of Internet software. The World Wide Web, invented by British academic Tim Berners-Lee while he was working at CERN in Switzerland, helped transfer the Internet from the domain of the geek to the domain of the general public.

The invention was actually a software protocol – HTTP, or hypertext transfer protocol, which defined a system for exchanging information written in a simple text-based standard, called HTML. HTML defines how you store text, images and crucially links to other sources of information.

Previously, information would have been stored as simple text files, or were binary files that had to be opened by the program associated with that file. Although HTML documents are written as simple text files containing text, links to images and links to other documents, a special program – the web browser – was developed that could present this information in a nicely formatted way.

A web browser is now the defacto means of accessing the Internet, and is installed on every computer that can access the Internet. HTML and HTTP are also well defined standards now, and despite a few minor incompatibilities, any web browser on any operating system on any computer should display the HTML data in the same way.

Gaining access

To access information on the Internet with a web browser requires the computer serving up the information at the other end to run a program called a *web server*. A web server is a program which simply 'serves up' HTML files to a web browser when requested. Web servers can be implemented as very simple programs (HTTP and HTML are after all very

simple protocols), which means that implementing one on a small embedded system can be quite straightforward.

What this means is that it can be easy to produce a very elegant looking user interface to your project (perhaps a nicely formatted web page showing the temperature in your workshop) by writing a simple HTML web page and providing a small web server on your embedded system. This can be much easier than producing a crude terminal interface over RS232, especially as web server programs are freely available for use with the PIC processor.

You can probably guess from the way this discussion is going that to connect your PIC project to the Internet requires some new, complex software: TCP/IP, an ethernet driver, a web server and 'web pages' written in HTML. Fortunately for us, Microchip provide all the software required, for free – all we have to worry about is configuring the software, (selecting the parts we require) and writing some simple web pages to present the information. You can completely ignore the complexities of the Internet connection software, build your own system, and then dip into the lower level code at a later date when you feel like it.

Microchip's offering

So what exactly have Microchip created that enables us, the humble hobbyist, to take advantage of the Internet? It's two things really. The first is a simple, low cost, and easy-to-use ethernet interface IC, and the second is the TCP/IP software to drive it.

The significance of the phrase 'easy to use' in that first point cannot be overstated. Ethernet interface ICs have been available for years, but until now they have been too complex for use by the average hobbyist. Initially, an Ethernet interface required several ICs, including special storage memory, and were complicated to access with a simple microcontroller. In more recent years, ICs have been created (such as the Realtek RTL8019) that reduce the component count to a single IC and a few passives.

These devices, however, are only produced in fine pitched packages that are difficult to solder, and have complex processor interfaces. Microchip have solved this problem by introducing a single chip solution that is available in a dual-in-line package with an SPI interface to the processor – which means that an Internet capable project could be constructed easily, cheaply and on stripboard. These parts are also available from many 'hobbyist friendly' suppliers, which means that this really is a practical option, and not just some theoretical solution available only to the few. The cost of the components required to implement an Internet interface can be as low as £10.

Interfacing to the Internet does require some complex software, but with Microchip's help developing an Internet project can now be approached by the interested hobbyist.

In next month's article we will take a deeper look at the TCP/IP protocols, and take a look at the Microchip ethernet interface IC – the ENC28J60.

PICmicro TUTORIALS AND PROGRAMMING

HARDWARE

VERSION 3 PICmicro MCU development board

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual I.e.d.s, quad 7-segment display and alphanumeric I.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



£158 including VAT and postage, supplied with USB cable and programming software

£40 OFF Buy the Development Board together with any Hobbyist/Student or Institutional versions of the software CD-ROMs listed below and take £40 off the total (including VAT) price.

SOFTWARE

ASSEMBLY FOR PICmicro V3

(Formerly PICtutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes.

The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro micro-controller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.




'C' FOR 16 Series PICmicro Version 4

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

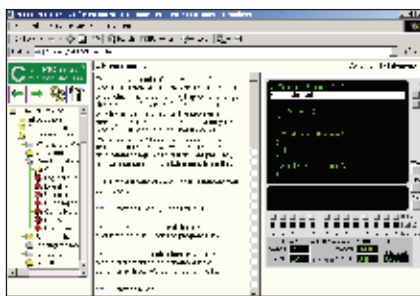- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.




Minimum system requirements for these items: Pentium PC running Windows 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.

FLOWCODE FOR PICmicro V3

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex systems in a matter of minutes. A Powerful language that uses macros to facilitate the control of devices like 7-segment displays, motor controllers and I.c.d.'s. The use of macros allows you to control these devices without getting bogged down in understanding the programming.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 3 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols
- Full on-screen simulation allows debugging and speeds up the development process.
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- New features in Version 3 include 16-bit arithmetic, strings and string manipulation, improved graphical user interface and printing, support for 18 series devices, pulse width modulation, I2C, new ADC component etc. The Hobbyist/Student version is limited to 4K of code (8K on 18F devices)

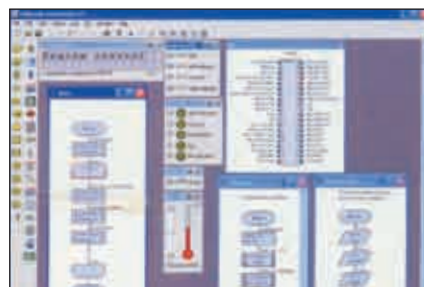

PRICES

Prices for each of the CD-ROMs above are:
(Order form on next page)

Hobbyist/Student	£45	inc VAT
Institutional (Schools/HE/FE/Industry)	£99	plus VAT
Institutional/Professional 10 user (Network Licence)	£300	plus VAT
Site licence	£599	plus VAT
Flowcode 10 user (Network Licence)	£350	plus VAT
Flowcode 50 user (Network Licence)	£699	plus VAT

(UK and EU customers add VAT at 17.5% to 'plus VAT' prices)

SPECIAL PACKAGE OFFER

TINA Pro V7 (Basic) + Flowcode V3 (Hobbyist/Student)

TINA Analogue, Digital, Symbolic, RF, MCU and Mixed-Mode Circuit Simulation, Testing and PCB Design

TINA Design Suite is a powerful yet affordable software package for analysing, designing and real time testing analogue, digital, MCU, and mixed electronic circuits and their PCB layouts. You can also analyse RF, communication, optoelectronic circuits, test and debug microcontroller applications.

Enter any circuit (up to 100 nodes) within minutes with TINA's easy-to-use schematic editor. Enhance your schematics by adding text and graphics. Choose components from the large library containing more than 10,000 manufacturer models. Analyse your circuit through more than 20 different analysis modes or with 10 high tech virtual instruments. Present your results in TINA's sophisticated diagram windows, on virtual instruments, or in the live interactive mode where you can even edit your circuit during operation.

Customise presentations using TINA's advanced drawing tools to control text, fonts, axes, line width, colour and layout. You can create, and print documents directly inside TINA or cut and paste your results into your favourite word- processing or DTP package.

TINA includes the following Virtual Instruments: Oscilloscope, Function Generator, Multimeter, Signal Analyser/Bode Plotter, Network Analyser, Spectrum Analyser, Logic Analyser, Digital Signal Generator, XY Recorder.

Flowcode V3 (Hobbyist/Student) – For details on Flowcode, see the previous page.

This offer gives you two separate CD-ROMs in DVD style cases – the software will need registering (FREE) with Designsoft (TINA) and Matrix Multimedia (Flowcode), details are given within the packages.

Get TINA + Flowcode for a total of just £50, including VAT and postage.

**£50.00
inc. VAT
and p&p**

DIGITAL WORKS 3.0



Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability ● Software for simulating digital logic circuits ● Create your own macros – highly scalable ● Create your own circuits, components, and i.c.s ● Easy-to-use digital interface ● Animation brings circuits to life ● Vast library of logic macros and 74 series i.c.s with data sheets ● Powerful tool for designing and learning.

Hobbyist/Student £45 inc. VAT.

Institutional £99 plus VAT.

Institutional 10 user £249 plus VAT.

Site Licence £599 plus VAT.

ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 jpg images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details).

Also contains a **FREE** 30-day evaluation of Paint Shop Pro 6 – Paint Shop Pro image editing tips and on-line help included!

Price £19.95 inc. VAT

PROJECT DESIGN WITH CROCODILE TECHNOLOGY

An Interactive Guide to Circuit Design

An interactive CD-ROM to guide you through the process of circuit design. Choose from an extensive range of input, process and output modules, including CMOS Logic, Op-Amps, PIC/PICAXE, Remote Control Modules (IR and Radio), Transistors, Thyristors, Relays and much more. Click Data for a complete guide to the pin layouts of i.c.s, transistors etc. Click More Information for detailed background information with many animated diagrams.

Nearly all the circuits can be instantly simulated in Crocodile Technology* (not included on the CD-ROM) and you can customise the designs as required.

WHAT'S INCLUDED

Light Modules, Temperature Modules, Sound Modules, Moisture Modules, Switch Modules, Astables including 555, Remote Control (IR & Radio), Transistor Amplifiers, Thyristor, Relay, Op-Amp Modules, Logic Modules, 555 Timer, PIC/PICAXE, Output Devices, Transistor Drivers, Relay Motor Direction & Speed Control, 7 Segment Displays. Data sections with pinouts etc., Example Projects, Full Search Facility, Further Background Information and Animated Diagrams.

Runs in Microsoft Internet Explorer

*All circuits can be viewed, but can only be simulated if your computer has Crocodile Technology version 410 or later. A free trial version of Crocodile Technology can be downloaded from: www.crocodile-clips.com. Animated diagrams run without Crocodile Technology.

**Over 150 pages
Over 600 images**



Single User £39.00 inc. VAT.

Multiple Educational Users (under 500 students) £59.00 plus VAT. Over 500 students £79.00 plus VAT.

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.

Please send me: CD-ROM ORDER FORM

- ☐ Electronic Projects
- ☐ Electronic Circuits & Components V2.0
- ☐ Analogue Electronics
- ☐ Digital Electronics V2.0
- ☐ Analogue Filters
- ☐ Electronics CAD Pack
- ☐ Robotics & Mechatronics
- ☐ Assembly for PICmicro V3
- ☐ 'C' for 16 Series PICmicro V4
- ☐ Flowcode V3 for PICmicro
- ☐ Digital Works 3.0

Version required:

- ☐ Hobbyist/Student
- ☐ Institutional
- ☐ Institutional/Professional 10 user
- ☐ Site licence

- ☐ PICmicro Development Board V3 (hardware)

- ☐ TINA Pro V7 Basic + Flowcode V3 Hobbyist/Student

- ☐ Electronic Components Photos
- ☐ Project Design – Single User
- ☐ Project Design – Multiple User (under 500 students)
- ☐ Project Design – Multiple User (over 500 students)

Note: The software on each version is the same, only the licence for use varies.

Full name:

Address:

..... Post code: Tel. No:

Signature:

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

☐ Please charge my Visa/Mastercard/Maestro: £

Valid From: Card expiry date:

Card No: Maestro Issue No.

Card Security Code (The last 3 digits on or just under the signature strip)



ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world. EU residents outside the UK add £5 for airmail postage per order.

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (**do not add VAT** unless you live in an EU (European Union) country, then add 17.5% VAT or provide your official VAT registration number).

Send your order to:
Direct Book Service
Wimborne Publishing Ltd
Sequoia House, 398a Ringwood Road
Ferndown, Dorset BH22 9AU
 To order by phone ring
01202 873872. Fax: 01202 874562
 Goods are normally sent within seven days
E-mail: orders@wimborne.co.uk
Online shop:
www.epemag.wimborne.co.uk/shopdoor.htm



READOUT

Email: editorial@wimborne.co.uk

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly



WIN AN ATLAS LCR ANALYSER WORTH £79
An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd, will be awarded to the author of the Letter Of The Month. The Atlas LCR automatically measures inductance from 1mH to 10H, capacitance from 1pF to 10,000µF and resistance from 1Ω to 2MΩ with a basic accuracy of 1%. www.peakelec.co.uk

★ LETTER OF THE MONTH ★

More on Linux and web security

Dear EPE,

Following up on Graham Harby's June *Letter of the Month*, 'Linux and web security' and Alan's June/July response, I really found this discussion useful with my laptop shackled with half a dozen anti-virus type applications from HiJackThis and Spy Doc to Avast. All consume resources, if not scanning they are busy updating or complaining about the licence expiring, bringing to mind the phrase 'spider to catch the fly'!

Having read Graham's letter explaining about the Linux operating system and how there are no known 'live' Linux viruses, I found the perfect solution for me; use the Linux operating system for surfing the net and Windows for everything else. In his letter, Graham recommended the 'Ubuntu' distribution of Linux because of its ease of use and the fact that it is all absolutely free!

I then followed his advice and installed it in a new partition of my Windows disk drive, so I was able to dual boot

(to Windows and Ubuntu). It was easy to install, as long as you follow the installation instructions on the Ubuntu website, and was ready to use in about twenty minutes.

My first impression of Ubuntu is that it is very user friendly and it came with everything from wordprocessing software to vector drawing packages. My parents, who find Windows awkward to use, thought Ubuntu was a breeze in comparison.

The only problem that I encountered was the lack of peripheral compatibility. Basic devices worked with the Ubuntu drivers, eg memory sticks and printers, but any hardware that needs specialised drivers for use with Windows obviously would not work straight away.

The ISP that I am currently with provides a USB modem for connection to the internet. This posed an immediate problem as the drivers were designed only for use with Windows. This is where you do need to be a Linux expert, which unfortunately I wasn't.

However, I found a website that explained how to install my Thomson

Speedtouch 330 modem using simple step-by-step instructions (www.linux-usb.org) and I managed to get it working after several attempts (main problem was downloaded extractor files being saved as text files, just needed the '.txt' extension removed). Having said this, many people now get their internet through their ethernet port (eg Virgin Media customers), and I understand this connection is fully supported by Linux.

After installing and using Ubuntu myself, I would fully recommend it to anyone (mainstream users and enthusiasts) who want to make sure their computer is safe from hackers, viruses and other spyware without slowing down Windows with memory-consuming security software.

Thanks EPE,

James Bickerton, via email

Thanks James, it's good to know of your success and of your recommendation to readers.

PIC N' MIX

Dear EPE,

I would like to comment on the circuit used when multiplexing the 7-segment display, as discussed in *PIC n' Mix*, June '08. For the transistor (will be referred to as upper) which drives the common anode of the display, I would normally prefer a PNP type. This helps to ensure an even more consistent driving current for each segment.

The main reason lies in the base-driving voltage of the transistor. A quick check on the datasheet shows that a BC548 has a $V_{ce(sat)}$ of 0.6V at 100mA (I_b at 5mA). Add that to the segment voltage of 2V and the V_{be} of 0.7V, and you will need to drive the upper transistor with at least $(0.6V + 2.0V + 0.7V) = 3.3V$.

According to the PIC's datasheet, a typical I/O output high minimum voltage is $V_{dd} - 0.7V$, which is 4.3V. So, you'll have 1.0V of buffer to drop over the 470Ω resistor, which give you I_b of 2.1mA, less that the I_b specified for that $V_{ce(sat)}$. This means you'll actually have a

higher $V_{ce(sat)}$ and lower I_c . For a different I_c you'll get a different gain factor, which makes the matter worse. Thus, when different numbers of segment are driven, the $V_{ce(sat)}$, I_b and I_c will fluctuate greatly.

If you use a Darlington transistor instead of the BC548, you'll get less fluctuation due to the much higher current gain. But you'll have less margin to work with as you need to have a minimum driving voltage of 4.0V (V_{be} for Darlington is 1.4V). A slight drop in the supply voltage means a blanked display.

If a PNP transistor is used instead, you'll get a very consistent $I_b/V_{ce(sat)}$, since the segment current is not involved. I've been using 2N2222/2N5401 and 2N3904/2N3906 to drive 7-segment displays. They all have a $V_{ce(sat)}$ of around 0.3V, which gives me plenty of room to work with.

Sometime, I even use 7407 (Hex open-collector inverter) to replace the NPN transistor for a common cathode display, as it saves me some room and a few resistors, it can also be easily hooked to a latch in case I run out of I/O.

Lee Faulty, via email

Thanks Lee, you might care to read last month's Circuit Surgery as it covers similar matters.

Schematic software

Dear EPE,

I have read Steve Liggett's letter, January 2008, about circuit diagram software. For several years I have been using a freeware program called TinyCAD. Its schematics are not as nice as those in EPE, but are better than those from most schematic software.

It can be downloaded from tinycad.sourceforge.net and was written by Matt Pyne of Milton Keynes. There is a good set of symbols included. Symbols may not always be consistent, as several were contributed by users, including myself, but you can usually find a useable one. It is also rather easy to draw new symbols and add them to the library.


Bill Stiles, Hillsboro, MO, USA, via email

That could be useful to readers Bill, thanks

Check out our website, 1,000s of items in stock



PM3082 - £195

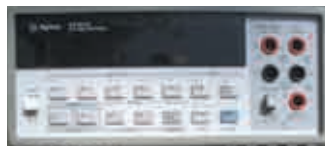

HP 34401A - £500 to £550



HP 33120A - £575 to £700



HP 8563A - £6,000

DIGITISING/STORAGE OSCILLOSCOPES

HP 54616B Digitising 500MHz 2GS/S 2 Channel £1,100
TEKTRONIX TDS520 Digitising 500MHz 500MS/S 2 Channel £800
TEKTRONIX TDS360 Digitising 200MHz 1GS/S 2 Channel £650
TEKTRONIX 2232 Dual Trace 100MHz 100MS/S £325
HP 54600B Dual Trace 100MHz 20MS/S with RS232; 2HP Probes, Ops Manual, Pouch & Front Cover £325
TEKTRONIX TDS224 Digitising 100MHz 4 Channel 1GS/S £750

SCOPEMETERS

FLUKE 97 Dual Trace 50MHz 25 MS/S £295

OSCILLOSCOPES

TEKTRONIX 2465B 4 Channel 400MHz Delay Cursors etc incl. Tek Probes £750
PHILIPS PM3062 2+2 Channels 100MHz Delay TB etc Autoset £195
TEKTRONIX 2445A 4 Channel 150MHz Delay Sweep Cursor etc £375
GOLD OS300 Dual Trace 20MHz £75
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep £125
FARNELL DTV12-14 Dual Trace 12MHz £40
TEKTRONIX P6139A 100MHz Probes - Unused £140

STEWART of READING

17A King Street, Mortimer,
Near Reading RG7 3RS

Telephone: (0118) 933 1111

Fax: (0118) 933 2375

www.stewart-of-reading.co.uk
9am-5pm Monday to Friday

SPECTRUM ANALYSERS

HP 8563A 9KHz-22GHz Synthesised £6,000
HP 8560A 50Hz-2.9GHz Synthesised Various opts £1,900-£3,250
HP 8590A 10KHz-1.5GHz £1,400
HP 3580A 5Hz-50KHz £295
ADVANTEST TR4132 100KHz-1000MHz £750

SIGNAL GENERATORS

HP 83731A Synthesised 1-20GHz £5,000
Marconi 2032 Sig Gen. 10KHz-5.4GHz Opt 01/02/06 - Avionics £3,250
HP 8648A Sig Gen 0.1-1000MHz £750
Gigatronix 7100 Synth 10MHz-20GHz (internal sweep/mod -130 to +15dBm) £3,000
Marconi 2024 9KHz-2.4GHz - HP/IB used/unused £1,250-£1,500
Marconi 2022E Synthesised AM/FM 10KHz-1.01GHz £500
Marconi 2019A Synthesised AM/FM 80KHz-1040MHz £150-£195
HP 33120A Function Gen. 100 microHz-15MHz used/unused £575-£700
T.T.I TG210 Function Gen 0.002Hz-2MHz TTL etc £70
R&S APN62 Synth Function Gen 1Hz-260KHz Bal/Unbal Output LCD £195
Metrix GX5000 Pulse Gen 50MHz Programmable £150
HP 3325A Synthesised Function Gen 21MHz £295

HP 3312A Function Gen 0.1Hz-13MHz AM/FM Sweep/Tri/Burst etc £175
HP 8112A Pulse/ Function Gen 50MHz £350
HP 8116 Pulse/ Function Gen 50MHz £750
Gould J3B Sine/Sq Osc. 10Hz-100KHz Low Distortion £50-£75

FREQUENCY COUNTER/TIMERS

HP 5350B Counter 20 GHz £750
Marconi 2440 Counter 20 GHz £500
Racal 1998 Counter 10Hz-1.3GHz £225
Racal 1991 Counter/Timer 160MHz 9 Digit £150
HP 53131A Universal Counter 3GHz Opt. 001 oven used/unused £995/£750
HP 53131A Universal Counter 225MHz Oven-In original boxes - unused/used £700/£600

DIGITAL MULTIMETERS

HP/Agilent 34401A 6 1/2 Digit £500/£550
Solartron 7150Plus 6 1/2 Digit True RMS IEEE with tem measurement £75
Fluke 77 series 2 3 1/2 Digit Handheld £45
AVO 8 Mk6 In Ever Ready Case with Leads etc £75
AVO 8 Mk5 with Leads etc £50
Goodwill GVT427 Dual Ch AC Millivoltmeter 10mV in 12 ranges 10Hz-1MHz. Unused £60

MISCELLANEOUS

MARCONI 2955A Radio Communications Test Set £1,000
MARCONI 2955 Radio Communications Test Set £625
MARCONI 6960B RF Power Meter with head £500
MARCONI 893C AF Power Meter Sinad Measurement Unused £50
HP 4192A Impedance Analyser with 16047A Text Fixture etc £3,500
HP 8902A Measuring Receiver 150KHz-1300MHz £4,500
HP 85032A Calibration Kits £400
SEAWARD Nova Pat Tester £195
BIRD 43 Wattmeter - Many Elements Available £75
HUNTRON 1000 Tracker £75
RACAL DANA 9343M LCR Databridge Digital Auto Measurements of RCL QD £95
RACAL 9008 Automatic Modulation Meter 1.5MHz-2GHz £60
MEGGER PAT2 Tester £95

POWER SUPPLIES

FARNELL AP60/50 0-60V 0-50A 1KW Switch Mode £400
FARNELL H60/25 0-60V 0-25A £400
THURLBY PL320QMD 0-30V 0-2A Twice Digital £160
H.P. 6626A Precision High Resolution 4 Outputs 0-7V 0-15mA or 0-50V 0-0.5A Twice £500
0-16V 0-0.2A or 0-50V 0-2A Twice £95
FARNELL XA35.2T 0-35V 0-2A Twice Digital £55
FARNELL B30/1030V 10A Variable No Meters £60
FARNELL LT30-10-30 0-1A Twice £50
THURLBY PL3300-32V 0-3A Digital (Kenwood badged) £75
THURLBY PL3200-30V 0-2A Digital £55
TAKASAGO GM035-2 0-35V 0-2A 2 Meters £35

Used Equipment - GUARANTEED.

Most Manuals supplied

Please check availability before ordering or calling.

Prices plus carriage and VAT

EPE BINDERS

KEEP YOUR MAGAZINES SAFE
- RING US NOW!

This ring binder uses a special system to allow the issues to be easily removed and re-inserted without any damage. A nylon strip slips over each issue and this passes over the four rings in the binder, thus holding the magazine in place.

The binders are finished in hard-wearing royal blue PVC with the magazine logo in gold on the spine. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £7.95 plus £3.50 post and packing. If you order more than one binder add £1 postage for each binder after the initial £3.50 postage charge (overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each). Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by card), to:

Everyday Practical Electronics, Wimborne Publishing Ltd, Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU.
Tel: 01202 873872. Fax: 01202 874562.

E-mail: editorial@epemag.wimborne.co.uk.

Web site: http://www.epemag.co.uk

Order on-line from:

www.epemag.wimborne.co.uk/shopdoor.htm

We also accept card payments. Mastercard, Visa, or Maestro (minimum card order £5). Send your card number and card expiry date plus Switch Issue No. with your order.



ELECTRONWORKS

Electronic Kits

Bench Power Supply
1.5V-10V
Power supply.
1A output.

Transformer Included!
£20.00

MP3 booster
Play your MP3 player through your PC speakers

£15.00

In Car Power Supply
Generate 5V or 3.6V from a car battery input.

£20.00

Sinewave Oscillator

An essential piece of test equipment for any budding audio enthusiast

£15.00



Desk Thermometer

How hot is your room? Test it with this handy LED based thermometer

£15.00



Coffee Mat

An electronic coffee mat that flashes LEDs when a cup is placed on it

£15.00

Many more to choose from

Order online at:

www.electronworks.co.uk

Net Work

Alan Winstanley



Spare a thought

This month's *Net Work* includes some practical pointers to help Internet users diagnose basic problems with their connection. A number of general hints will also be described to assist in troubleshooting and analysing various aspects of Internet usage.

In order to understand some Internet fundamentals, it helps to familiarise oneself with some basic aspects of Internet connectivity. At the root of the entire Internet is TCP/IP, or Transmission Control Protocol/Internet Protocol (IP), which was created to enable separate computer networks to communicate with each other.

Every resource or 'node' connected to the Internet has its own unique numerical IP address, such as 38.12.34.567. Due to the pressure for 'spare' numbers under the current standard (IPv4), temporary or dynamic IP addressees are often allocated to users each time they connect to the Internet. Other resources, such as web and mail servers need a fixed IP address if the Internet is to hang together properly. Fixed IP addresses are useful in some Internet applications, including virtual private networks or IP security camera networks, when it is desirable that the IP address does not constantly change. The release of IPv6 is some years away, and will allow for better scalability of IP addresses that cannot be achieved under IPv4.

The job of the 'domain name system' (DNS) is to translate or 'resolve' human-recognisable plain English addresses into numerical IP addresses, rather like a telephone directory yields telephone numbers to its readers. Each ISP maintains its own copy of this 'DNS telephone book' as up to date as possible, so that they instantaneously know the correct place to go when you request a web page, email connection or other service.

One way of seeing this DNS translation in action is with some basic software tools, including the Unix or DOS-based network commands built into eg Windows XP. Some very useful online tools are also available that do the same thing, but raw command line tests are fast and need no foible-filled web browser or other complication to use them.

In Windows XP you can open a DOS box by clicking *Start/Run/cmd* (for command prompt). You could drag a shortcut to the Start menu or Quick Launch bar, so you can open a DOS box with a single mouse click.

The first useful command is *Traceroute*, which lists the route from your local node, through the Internet to a remote system. You can use *tracert* to help locate servers (and their ISPs) or to test whether they are reachable, or see if part of the route is slow or broken. For example, at the DOS command prompt type:

```
>tracert www.epemag.wimbome.co.uk
```

Hop to it

The process of 'hopping' from your own IP address through to that of the remote host then begins, in this case aiming for the web server that hosts our own website. Immediately, the IP address [195.80.2.3] of the website's server is revealed by a DNS

translation (see screenshot). If the IP address is shown when you hit 'return', then you know that your system is reaching out onto the Internet properly and that your ISP's DNS servers are functioning, otherwise the DNS lookup could not happen.

If this DNS/IP address translation does not happen at all, then there is probably a fault at your end of the network, possibly with your Internet connection, or (very rarely) an outage with your own ISP's DNS servers. You should first try unplugging your router for several minutes, before starting again with a *tracert*; check that all network and router cables are inserted properly, and if in doubt eliminate any extension leads or inline suppressor faults from the equation by plugging your router directly into the ADSL splitter. Connectivity faults are regularly due to mechanical reasons that can soon be repaired. Check the router LEDs too. If no connection is available then allow say 20 to 30 minutes before calling your ISP.

If all is well with the *tracert* session then the path through to our own host (TCP is our UK-based ISP) will be listed, one hop at a time. Try a *tracert* on www.ebay.co.uk to see how it hops to the USA. You can pick any other host (your POP3 mail server for instance) to *tracert* as required.

Note how your own IP address is also shown, starting with the 'local' IP address of your PC [192.168.2.1], before reaching out onto the Internet where an IP address of 78.33.38.14 is shown in this example.

Chicken run

A useful aspect to remember about a broadband router is that you may run multiple PCs on a local area network, each of which adopts a unique 'local' IP address that is masked from the outside world. Other machines on my LAN have unique addresses such as 192.168.2.2 or 192.168.2.8 and so on.

The router, however, has a unique IP address that is visible, which is allocated by the internet service provider. It is the job of a router to channel Internet traffic (web, email, FTP etc) from the outside world through to the appropriate machine residing behind the router. A personal favourite website that reveals your IP address is IP Chicken (www.ipchicken.com). A nice graphical *tracert* service is available at <http://visualroute.visualware.com/>

Traceroute is therefore handy for general web and broadband debugging. If the remote host is unreachable along the way, then any server or network-related problem can be difficult to rectify, and by the time they have been highlighted, problems have often cured themselves anyway.

In next month's *Net Work* I'll continue on the same theme, outlining more useful software tools and commands, together with practical examples of their application. You can email Alan at: alan@epemag.demon.co.uk

```
C:\WINDOWS\system32\cmd.exe
(C) Copyright 1985-2001 Microsoft Corp.
C:\Documents and Settings\ARM>tracert www.epemag.wimbome.co.uk

Tracing route to www2.tcp.net.uk [195.80.2.3]
over a maximum of 30 hops:
  0  <1 ms  <1 ms  <1 ms  192.168.2.1
  1  48 ms  39 ms  45 ms  z.dsl.enta.net [78.33.38.14]
  2  39 ms  39 ms  39 ms  g14-4.telehouse-east3.dsl.enta.net [78.33.38.13]
  3  48 ms  38 ms  39 ms  te5-2.telehouse-east.core.enta.net [62.249.192.1]
  4  48 ms  48 ms  45 ms  peer1.ldn1.flagtel.com [195.80.2.3]
  5  39 ms  40 ms  39 ms  so-3-2-0.0.eje01.ldn004.flagtel.com [62.216.129.1]
  6  48 ms  48 ms  48 ms  62.216.144.158
  7  48 ms  48 ms  48 ms  vlan2-core01.lth.tcp.net.uk [195.80.0.77]
  8  43 ms  42 ms  43 ms  fal-0-1-core1.scw.tcp.net.uk [195.80.3.122]
  9  45 ms  43 ms  43 ms  vlan2-core1.ast.tcp.net.uk [195.80.3.33]
 10  43 ms  43 ms  43 ms  www2.tcp.net.uk [195.80.2.3]

Trace complete.
C:\Documents and Settings\ARM>
```

Screenshot of a typical session from the Windows XP command prompt

Electronics Teach-In + FREE CD-ROM

Mike Tooley

A broad-based introduction to electronics – find out how circuits work and what goes on inside them. Plus 15 easy-to-build projects. The 152-page A4 book comes with a free CD-ROM containing the whole Teach-In 2006 series (originally published in *EPE*) in PDF form, interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial), together with simulations of the circuits in the Teach-In series, plus Flowcode (a limited version) a high level programming system for PIC microcontrollers based on flowcharts.

The Teach-In series covers everything from Electric Current through to Microprocessors and Microcontrollers and each part includes demonstration circuits to build on breadboards or to simulate on your PC.

In addition to the Teach-In series, the book includes 15 CMOS-based simple projects from the Back-To-Basics series by Bart Trepak, these are: Fridge/Freezer Alarm, Water Level Detector, Burglar Alarm, Scarecrow, Digital Lock, Doorchime, Electronic Dice, Kitchen Timer, Room Thermometer, Daily Reminder, Whistle Switch, Parking Radar, Telephone Switch, Noughts and Crosses Enigma and a Weather Vane. There is also a MW/LW Radio project in the Teach-In series.

152 pages + CD-ROM Order code ETI £8.50



ROBOTICS

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various 'click-together' components supplied in the basic RIS kit. Then explains in simple terms how the 'brain' of the robot may be programmed on screen using a PC and 'zapped' to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages – large format Order code BP901 £14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS – Robert Penfold

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

198 pages Order code BP902 £14.99

ANDROIDS, ROBOTS AND ANIMATRONS Second Edition – John Iovine

Build your own working robot or android using both off-the-shelf and workshop constructed materials and devices. Computer control gives these robots and androids two types of artificial intelligence (an expert system and a neural network). A lifelike android hand can be built and programmed to function doing repetitive tasks. A fully animated robot or android can also be built and programmed to perform a wide variety of functions.

The contents include an Overview of State-of-the-Art Robots; Robotic Locomotion; Motors and Power Controllers; All Types of Sensors; Tilt; Bump; Road and Wall Detection; Light; Speech and Sound Recognition; Robotic Intelligence (Expert Type) Using a Single-Board Computer Programmed in BASIC; Robotic Intelligence (Neural Type) Using Simple Neural Networks (Insect Intelligence); Making a Lifelike Android Hand; A Computer-Controlled Robotic Insect Programmed in BASIC; Telepresence Robots With Actual Arcade and Virtual Reality Applications; A Computer-Controlled Robotic Arm; Animated Robots and Androids; Real-World Robotic Applications.

224 pages Order code MGH1 £16.99

DIRECT BOOK SERVICE

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS SEE THE NEXT TWO ISSUES OF *EPE*

All prices include UK postage

RADIO

BASIC RADIO PRINCIPLES AND TECHNOLOGY Ian Poole

Radio technology is becoming increasingly important in today's high technology society. There are the traditional uses of radio which include broadcasting and point to point radio as well as the new technologies of satellites and cellular phones. All of these developments mean there is a growing need for radio engineers at all levels.

Assuming a basic knowledge of electronics, this book provides an easy to understand grounding in the topic.

Chapters in the book: Radio Today, Yesterday, and Tomorrow; Radio Waves and Propagation; Capacitors, Inductors, and Filters; Modulation; Receivers; Transmitters; Antenna Systems; Broadcasting; Satellites; Personal Communications; Appendix – Basic Calculations.

263 pages Order code NE30 £20.00

PROJECTS FOR RADIO AMATEURS AND S.W.L.S. R. A. Penfold

This book describes a number of electronic circuits, most of which are quite simple, which can be used to enhance the performance of most short wave radio systems.

The circuits covered include: An aerial tuning unit; A simple active aerial; An add-on b.f.o. for portable sets;

A wavetrap to combat signals on spurious responses; An audio notch filter; A parametric equaliser; C.W. and S.S.B. audio filters; Simple noise limiters; A speech processor; A volume expander.

Other useful circuits include a crystal oscillator, and RTTY/C.W. tone decoder, and a RTTY serial to parallel converter. A full range of interesting and useful circuits for short wave enthusiasts.

92 pages Order code BP304 £4.45

AN INTRODUCTION TO AMATEUR RADIO I. D. Poole

Amateur radio is a unique and fascinating hobby which has attracted thousands of people since it began at the turn of the last century. This book gives the newcomer a comprehensive and easy to understand guide through the subject so that the reader can gain the most from the hobby. It then remains an essential reference volume to be used time and again. Topics covered include the basic aspects of the hobby, such as operating procedures, jargon and setting up a station. Technical topics covered include propagation, receivers, transmitters and aerials etc.

150 pages Order code BP257 £5.49


COMPUTERS AND COMPUTING

THE INTERNET FOR THE OLDER GENERATION Jim Gatenby

Especially written for the over 50s. Uses only clear and easy-to-understand language. Larger type size for easy reading. Provides basic knowledge to give you confidence to join the local computer class.

This book explains how to use your PC on the Internet and covers amongst other things: Choosing and setting up your computer for the Internet. Getting connected to the Internet. Sending and receiving emails, photographs, etc., so that you can keep in touch with family and friends all over the world. Searching for and saving information on any subject. On-line shopping and home banking. Setting up your own simple web site.

228 pages Order code BP600 £8.99

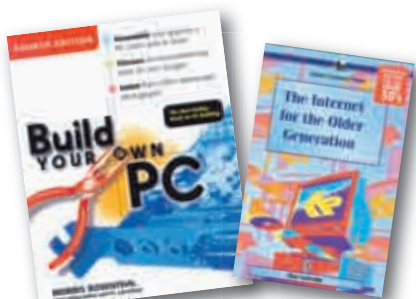

BUILD YOUR OWN PC – Fourth Edition Morris Rosenthal

More and more people are building their own PCs. They get more value for their money, they create exactly the machine they want, and the work is highly satisfying and actually fun. That is, if they have a unique beginner's guide like this one, which visually demonstrates how to construct a computer from start to finish.

Through 150 crisp photographs and clear but minimal text, readers will confidently absorb the concepts of computer building. The extra-big format makes it easy to see what's going on in the pictures. The author goes 'under the hood' and shows step-by-step how to create a Pentium 4 computer or an Athlon 64 or Athlon 64FX, covering: What first-time builders need to know; How to select and purchase parts; How to assemble the PC; How to install Windows XP. The few existing books on this subject, although outdated, are in steady demand. This one delivers the expertise and new technology that fledgling computer builders are looking for.

224 pages – large format Order code MGH2 £16.99

THE PIC MICROCONTROLLER YOUR PERSONAL INTRODUCTORY COURSE – THIRD EDITION John Morton

Discover the potential of the PIC microcontroller through graded projects – this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PICs capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too: this is not a reference book – you start work with the PIC straight away.

The revised third edition covers the popular reprogrammable Flash PICs: 16F54/16F84 as well as the 12F508 and 12F675.

270 pages Order code NE36 £18.50

PROGRAMMING 16-BIT PIC MICROCONTROLLERS IN C – LEARNING TO FLY THE PIC24 Lucio Di Jasio (Application Segments Manager, Microchip, USA)

A Microchip insider tells all. Focuses on examples and exercises that show how to solve common, real-world design problems quickly. Includes handy checklists to help readers perform the most common programming and debugging tasks. FREE CD-ROM includes source code in C, the Microchip C30 compiler, and MPLAB SIM software, so that readers gain practical, hands-on programming experience.

Until recently, PICs didn't have the speed and memory necessary for use in designs such as video- and audio-enabled devices. All that changed with the introduction of the 16-bit PIC family, the PIC24. This new guide teaches readers everything they need to know about the architecture of these chips, how to program them, how to test them and how to debug them. Lucio's common-sense, practical, hands-on approach starts out with basic functions and guides the reader step-by-step through even the most sophisticated programming scenarios.

Experienced PIC users and newcomers alike will benefit from the text's many thorough examples, which demonstrate how to nimbly side-step common obstacles and take full advantage of all the 16-bit features.

496 pages +CD-ROM Order code NE45 £32.50

FREE
CD-ROM

THEORY AND REFERENCE

ELECTRONIC CIRCUITS – FUNDAMENTALS & APPLICATIONS

Third Edition

Mike Tooley

A comprehensive reference text and practical electronics handbook in one volume – at an affordable price!

New chapter on PIC microcontrollers – the most popular chip family for use in project work by hobbyists and in colleges and universities.

New companion website: spreadsheet design tools to simplify circuit calculations; circuit models and templates to enable virtual simulation; a bank of on-line questions for lecturers to set as assignments, and on-line self-test multiple choice questions for each chapter with automatic marking, to enable students to continually monitor their progress and understanding.

The book's content is matched to the latest pre-degree level courses, making this an invaluable reference for all study levels, and its broad coverage is combined with practical case studies, based in real-world engineering contexts throughout the text.

The unique combination of a comprehensive reference text, incorporating a primary focus on practical applications, ensures this text will prove a vital guide for students and also for industry-based engineers, who are either new to the field of electronics, or who wish to refresh their knowledge.

400 pages

Order code NE43 £24.95

BEBOP TO THE BOOLEAN BOOGIE

Second Edition

Clive (Max) Maxfield

This book gives the 'big picture' of digital electronics. This in-depth, highly readable, guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more. The author's tongue-in-cheek humour makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate. Comes with a free CD-ROM which contains an eBook version with full text search plus bonus chapter – An Illustrated History of Electronics and Computing.

Contents: Fundamental concepts; Analog versus digital; Conductors and insulators; Voltage, current, resistance, capacitance and inductance; Semiconductors; Primitive logic functions; Binary arithmetic; Boolean algebra; Karnaugh maps; State diagrams, tables and machines; Analog-to-digital and digital-to-analog; Integrated circuits (ICs); Memory ICs; Programmable ICs; Application-specific integrated circuits (ASICs); Circuit boards (PWBs and DWBs); Hybrids; Multichip modules (MCMs); Alternative and future technologies.

500 pages

Order code BEB1 £29.95

BEBOP BYTES BACK (and the Bebopter Computer Simulator)

CD-ROM

Clive (Max) Maxfield and

Alvin Brown

This follow-on to Bebopter to the Boolean Boogie is a multimedia extravaganza of information about how computers work. It picks up where 'Bebopter I' left off, guiding you through the fascinating world of computer design... and you'll have a few chuckles, if not belly



CD-ROM

laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format

CD-ROM

Order code BEB2 CD-ROM £21.95



GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages

Order code BP239 £5.49

STARTING ELECTRONICS, THIRD EDITION

Keith Brindley

A punchy practical introduction to self-build electronics. The ideal starting point for home experimenters, technicians and students who want to develop the real hands-on skills of electronics construction.

A highly practical introduction for hobbyists, students, and technicians. Keith Brindley introduces readers to the functions of the main component types, their uses, and the basic principles of building and designing electronic circuits.

Breadboard layouts make this very much a ready-to-run book for the experimenter, and the use of multimeter,

but not oscilloscopes, and readily available, inexpensive components makes the practical work achievable in a home or school setting as well as a fully equipped lab.

288 pages

Order code NE42 £11.50

THE AMATEUR SCIENTIST CD-ROM – VERSION 2

The complete collection of The Amateur Scientist articles from *Scientific American* magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards. Plus over 1,000 pages of helpful science techniques that never appeared in *Scientific American*.

Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather... and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems. Includes extensive Science Software Library with even more science tools. Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher. Over 1,000 projects.

CD-ROM

Order code ASI CD-ROM £19.95



eBAY FOR BEGINNERS

Cherry Nixon

There are two kinds of people, those who are trading on eBay and the rest who are missing out. Though eBay has been embraced by entrepreneurs all over the world, it remains the people's site and offers the largest market for the smallest fee.

eBay presents an opportunity for everyone, the trick is to master it. This book shows you how to start trading on eBay UK. It also offers advice on getting organised and tips to put you ahead.

The book has been developed from Cherry's popular hands-on course 'Buying and Selling on eBay for Technological Simpletons'. In addition to fully explaining eBay and how to trade on it there are sections on Paypal, producing pictures of your sale items, fees and accounts, safety and security, including what to do when things go wrong and what protection is provided.

178 pages

Order code BP551 £8.99



MUSIC, AUDIO AND VIDEO

MAKING MUSIC WITH YOUR COMPUTER

Stephen Bennett


Nearly everyone with musical aspirations also has a computer. This same computer can double as a high quality recording studio capable of producing professional recordings. This book tells you what software and hardware you will need to get the best results.

You'll learn about recording techniques, software and effects, mixing, mastering and CD production.

Suitable for PC and Mac users, the book is full of tips, 'how to do' topics and illustrations. It's the perfect answer to the question "How do I use my computer to produce my own CD?"

92 pages

Order code PC120 £10.95

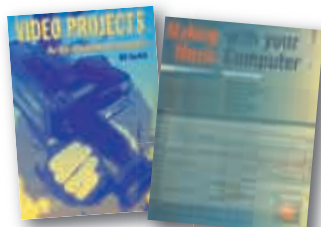

QUICK GUIDE TO MP3 AND DIGITAL MUSIC

Ian Waugh

MP3 files, the latest digital music format, have taken the music industry by storm. What are they? Where do you get them? How do you use them? Why have they thrown record companies into a panic? Will they make music easier to buy? And cheaper? Is this the future of music?

All these questions and more are answered in this concise and practical book which explains everything you need to know about MP3s in a simple and easy-to-understand manner. It explains:

How to play MP3s on your computer; How to use MP3s with handheld MP3 players; Where to find MP3s on the Web; How MP3s work; How to tune into Internet radio stations; How to create your own MP3s; How to record your own CDs from MP3 files; Other digital audio music formats.

Whether you want to stay bang up to date with the latest music or create your own MP3s and join the on-line digital music revolution, this book will show you how.

60 pages

Order code PC119 £7.45

VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply

constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Complete with explanations of how the circuit works, shopping lists of components, advice on construction, and guidance on setting up and using the projects, this invaluable book will save you a small fortune.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages

Order code PC115 ~~£10.95~~ £5.45

**ALL PRICES INCLUDE
UK POST & PACKING**

DATA AND DESIGN

PRACTICAL ELECTRONIC FILTERS Owen Bishop

This book deals with the subject in a non-mathematical way. It reviews the main types of filter, explaining in simple terms how each type works and how it is used.

The book also presents a dozen filter-based projects with applications in and around the home or in the constructor's workshop. These include a number of audio projects such as a rhythm sequencer and a multi-voiced electronic organ.

Concluding the book is a practical step-by-step guide to designing simple filters for a wide range of purposes, with circuit diagrams and worked examples.

88 pages

Order code BP299

£5.49

DIGITAL LOGIC GATES AND FLIP-FLOPS Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.


Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages

Order code PC106

£9.95

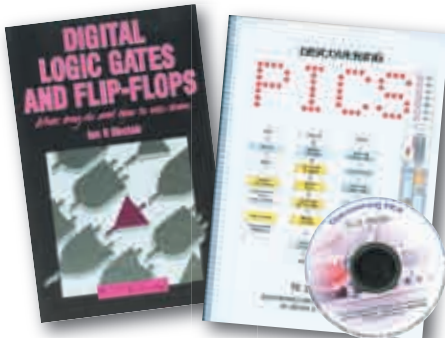

A BEGINNER'S GUIDE TO TTL DIGITAL ICs R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the "real world".

142 pages

Order code BP332

£5.45

MICROCONTROLLER COOKBOOK Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages

Order code NE26

£23.50

RADIO BYGONES

We also carry a selection of books aimed at readers of *EPE's* sister magazine on vintage radio – *Radio Bygones*. These books include Jonathan Hill's excellent *Radio Radio*, a comprehensive book with hundreds of photos depicting the development of the British wireless set up to the late 1960s.

The four volumes of our own *Wireless For the Warrior* by Louis Meulstee are also available. These are a technical history of radio communication equipment in the British Army and clandestine equipment from pre-war through to the 1960s.

For details see the shop on our UK web site at www.epemag.co.uk or contact us for a list of *Radio Bygones* books.

PROJECT BUILDING AND TESTING

ELECTRONIC PROJECT BUILDING FOR BEGINNERS R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages

Order code BP392

£5.49

ELECTRONIC PROJECTS FOR EXPERIMENTERS R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded 'seen it all before' syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different. No doubt many of the projects featured here have practical applications, but they are all worth a try for their interest value alone.

The subjects covered include: Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red 'torch', Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

138 pages

Order code BP371

£5.45

PRACTICAL FIBRE-OPTIC PROJECTS R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes

them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple DC links, P.W.M. DC link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374

£5.45

DISCOVERING PICS W.D. Phillips

A good introduction to PIC programming, covering everything you need to know to get you started. No previous knowledge of microcontrollers is required, but some previous experience with electronic circuits is assumed. Covers the basic concept of a microcontroller, fundamentals of a PIC-based circuit and using the MPLAB program. Further chapters introduce binary, PIC architecture, the instruction set, the PIC memory map and special registers plus real world programming. Four simple projects are also fully described; a Wavy Wand, an Electronic Dice, a Games Timer and a Pulse Monitor.

The associated CDROM contains the book in PDF format, MPLAB (plus instruction manuals in PDF format) and all the programs covered in the book as assembler (ASM) files. Those that wish to programme their own PICs will require a PIC programmer.

In addition a PCB-based hardware kit is also supplied that makes up into the Wavy Wand which will spell out a short message via a line of LEDs when waved through the air.

Book + CDROM + Hardware Order code DOC2 £28.50

BOOK + CD-ROM + HARDWARE

BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £2 per book. For the rest of the world airmail add £3 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, or Maestro to: **DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, SEQUOIA HOUSE, 398a RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AU.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a further selection of books see the next two issues of *EPE*.
Tel 01202 873872 Fax 01202 874562. Email: dbs@wimborne.co.uk
Order from our online shop at: www.epemag.co.uk

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

☐ Please charge my card £ Card expiry date:

Card Number Maestro Issue No.

Valid From Date Card Security Code (the last three digits on or just below the signature strip)

Please send book order codes:

.....

Please continue on separate sheet of paper if necessary

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the *PCB Service*, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. Double-sided boards are **NOT plated through hole** and will require 'vias' and some components soldering to both sides. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU. Tel: 01202 873872; Fax 01202 874562; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm. Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).**

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Back numbers or photocopies of articles are available if required – see the Back Issues page for details. WE DO NOT SUPPLY KITS OR COMPONENTS FOR OUR PROJECTS.

Please check price and availability in the latest issue. A large number of older boards are listed on, and can be ordered from, our website.

Boards can only be supplied on a payment with order basis.

PROJECT TITLE	ORDER CODE	COST
MAY '07		
Bass Extender	618	£5.87
Caravan Lights Check	619	£6.18
JUNE '07		
★ Energy Meter – Main Board	616 } set	£9.83
– Display Board	617	
3V to 9V Converter (PCB plus TL499A IC)	620 + chip	£7.53
Bat Sonar	621	£6.03
JULY '07		
MiniCal 5V Meter Calibration Standard	622	£6.82
Lead-Acid Battery Zapper	623	£6.50
Video Reading Aid	624	£6.50
Digi-Flash Slave	625	£5.55
AUGUST '07		
TwinTen Stereo Amplifier	626	£9.83
Printer Port Hardware Simulator	627	£6.66
★ RFID Security Module	628	£7.14
★ V2 PC Scope – Control Board	629	£7.13
– Analogue Board	630	£6.50
SEPTEMBER '07		
★ Flexitimer – Main Board	631	£7.29
– Display Board 1	632	£7.29
– Display Board 2	633	£7.29
– Display Board 3	634	£7.29
Pocket Tens Unit	635	£6.35
OCTOBER '07		
★ Simple Seismograph	636	£6.66
★ V8 Doorbell – Main Board	637 } set	£11.42
– Display Board	638	
★ Standby Power Saver		
– Transmitter	639	£6.34
– Receiver	640 } set	£6.97
– PSU	641	
NOVEMBER '07		
Vehicle Voltage Monitor	642	£6.34
★ USB Electrocardiograph	643	£7.61
★ Inductance & Q-Factor Meter	644	£7.93
Experimenter's Audio System		
– Main Board	645 } set	£7.61
– PSU	646	
★ Teach-In '08 – Master Control Board	647	£7.93
DECEMBER '07		
iPod or MP3 Player Charger	648	£5.87
AVR ISP Socketboard	649	£7.61
★ PIC Speech Synthesiser – Playback	650	£6.03
– Record	651	£6.66
JANUARY '08		
★ Serial I/O Controller	652	£11.90
★ MIDI Drum Kit – Main Board	653	£11.58
– Display	654	£7.61
Phone/Fax Missed Call Alert	655	£6.66
★ PIC Carillon	656	£7.30
FEBRUARY '08		
MIDI Drum Kit – Optical Sensor	657	£5.39
Studio Series – Stereo Preamplifier – Pre Amp	658 } set	£9.51
– PSU	659	
Electrosmog Sniffer	660	£5.71

PROJECT TITLE	ORDER CODE	COST
MARCH '08		
Fluorescent Tube Driver	661	£7.13
Studio Series – Stereo Headphone Amplifier	662	£8.24
APRIL '08		
★ Studio Series – Remote Control Module	663	£7.13
★ MIDI Activity Detector	664	£6.34
PIC In-Circuit Programming Add-On	665	£5.39
★ PC-Controlled Burglar Alarm – Main Board	666 } set	£11.89
– Display Board	667	
MAY '08		
★ PC-Controlled Burglar Alarm – Keypad	668	£6.18
★ Electric Mobility Buggy Monitor	669	£6.02
Mini Theremin	670	£10.15
JUNE '08		
★ Monopoly Money	671	£7.30
★ Universal High-Energy LED Lighting System	673	£6.82
JULY '08		
★ PIC MIDI Sound Wave Generator	672	£11.20
Galactic Voice	674	£6.82
Coolmaster	675	£6.34
AUGUST '08		
Four-Channel A/V Selector	676	£9.51
DC Relay Switch For High Current Loads	677	£6.02
Versatile Temperature Switch	678	£6.66
★ Mains Monitor – Monitor	679	£7.13
– Interface	680	£5.71
SEPTEMBER '08		
Magnetic Cartridge Preamplifier	681	£7.45
★ Super Speedo Corrector	682	£6.66
Ultrasonic Eavesdropper	683	£6.82
S-Video To Composite Video Converter (double-sided)	684	£9.98

EPE SOFTWARE

★ All software programs for *EPE* Projects marked with a star, and others previously published can be downloaded free from our Downloads site, accessible via our home page at: www.epemag.co.uk

PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our UK website (www.epemag.co.uk); go to the 'Downloads' section.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
.....			
Name			
Address			
.....			
Tel. No.			
I enclose payment of £ (cheque/PO in £ sterling only) to:			
Everyday Practical Electronics			
  			
Card No.			
Valid From		Expiry Date	
Card Security No.		Maestro Issue No.	
Signature			
<p>Note: You can also order PCBs by phone, Fax or Email or via the shop on our website on a secure server:</p> <p>http://www.epemag.co.uk</p>			



EPE EVERYDAY PRACTICAL ELECTRONICS

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it. We have been the leading monthly magazine in this market for the last twenty-three years.

BTEC ELECTRONICS TECHNICIAN TRAINING

NATIONAL ELECTRONICS
VCE ADVANCED ICT
HNC AND HND ELECTRONICS
FOUNDATION DEGREES
NVQ ENGINEERING AND IT
DESIGN AND TECHNOLOGY

LONDON ELECTRONICS COLLEGE
20 PENYVERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721
www.lec.org.uk

Circuit Specialists Europe
WWW.CIRCUITSPECIALISTS.EU
For

Soldering & Desoldering, Bench
Power Supplies, Enclosed
Switching Power Supplies
Take a look at
www.circuitspecialists.co.uk
Mid Season Sale NOW ON!

RSHELECTRONICS

UK & International Suppliers of Electronic Components & Kits
Capacitors Resistors Transistors Optoelectronics PCBs Breadboard
Solder Switches Cable Batteries Tools CMOS ICs Potentiometers
P&P £2.50 (orders over £25 free P&P) No Min Order. No VAT
NEW 2008 MAIL ORDER CATALOGUE AVAILABLE AT
www.rshelectronics.co.uk

5Hz GPS Receiver Modules

- 5Hz update rate
- 32 Channels
- Built in antenna
- High sensitivity
- Low power



See our website for the full range and compatible video overlay units
WWW.PIC-OSD.COM

CPS Solar

Solar panels, solar cells, and many more alternative energy products for battery charging etc, please visit our website for further info or call
Tel: 0870 765 2334.
www.solarpanelsonline.co.uk

BOWOOD ELECTRONICS LTD

Suppliers of Electronic Components

Place a secure order on our website or call our sales line

All major credit cards accepted

Web: www.bowood-electronics.co.uk

Unit 1, McGregor's Way, Turnoaks Business Park, Chesterfield,

S40 2WB. Sales: 01246 200222

Send 60p stamp for catalogue

SAFFRON ELECTRONICS LTD

Suppliers of High Quality Electronic Components since 1991

Resistors, Caps, Batteries, Chargers, Semiconductors, LED's, IC's, PCB's, Switches, Solder, Cable, Wire, Etc.
Online Catalogue and Shop available at

www.SaffronElectronics.co.uk

3/04 St Albans House, St Albans Road, Stafford, ST16 3DR
Telephone: **0845 166 2314** (local rate)

N.R. BARDWELL Ltd – est 1948 Electronic Component Supplies

LED's, Semis, IC's Resistors, Caps, etc send 44p for lists. 1000's bargains at our secure site: www.bardwells.co.uk
288, Abbeydale Rd. Sheffield. S7 1FL
0845 166 2329 (local rate)

Small prototyping company seeking a freelance electronics engineer

to work on upcoming project work. Please get in touch for further details.

Contact Ian 01797 22 99 81 or
cokerian@yahoo.co.uk

Miscellaneous

VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

KITS, TOOLS, COMPONENTS. S.A.E catalogue. SIR-KIT ELECTRONICS, 52 Severn Road, Clacton, CO15 3RB. www.geocities.com/sirkituk



ONLY £8.50

INCLUDING P&P FROM OUR **DIRECT BOOK SERVICE**

ELECTRONICS TEACH-IN

BY MIKE TOOLEY

plus **FREE CD-ROM**

A broad-based introduction to electronics – find out how circuits work and what goes on inside them. Plus 15 easy-to-build projects. The 152 page A4 book comes with a free CD-ROM containing the whole *Teach-In 2006* series (originally published in *EPE*) in PDF form, interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial), together with simulations of the circuits in the Teach-In series, plus Flowcode (a limited version) a high level programming system for PIC microcontrollers based on flowcharts.

See our **Direct Book Service** – pages 67 to 69

Europe's Largest Surplus Store

20,000,000 Items on line NOW !
New items added daily

Established for over 25 years, UK company Display Electronics prides itself on offering a massive range of electronic and associated electro-mechanical equipment and parts to the Hobbyist, Educational and Industrial user. Many current and obsolete hard to get parts are available from our vast stocks, which include:

- ◆ 6,000,000 Semiconductors
- ◆ 5,000 Power Supplies
- ◆ 25,000 Electric Motors
- ◆ 10,000 Connectors
- ◆ 100,000 Relays & Contactors
- ◆ 2000 Rack Cabinets & Accessories
- ◆ 4000 Items of Test Equipment
- ◆ 5000 Hard Disk Drives

We Ship Worldwide

Surplus Wanted

www.distel.co.uk

Display Electronics
29 / 35 Osborne Road
Thornton Heath
Surrey UK CR7 8PD

Telephone
[44] 020 8653 3333
Fax [44] 020 8653 8888

Rechargeable Batteries With Solder Tags

NIMH

AA 2000mAh£2.82
C 4Ah£4.70
D 9Ah£7.60
PP3 150mAh£4.95

NICAD

AA 650mAh..... £1.41
C 2.5Ah£3.60
D 4Ah£4.95

Instrument case with edge connector and screw terminals

Size 112mm x 52mm x 105mm tall

This box consists of a cream base with a PCB slot, a cover plate to protect your circuit, a black lid with a 12 way edge connector and 12 screw terminals built in (8mm pitch) and 2 screws to hold the lid on. The cream bases have minor marks from dust and handling price £2.00 + VAT(=£2.35) for a sample or £44.00+VAT (=£51.70) for a box of 44.



866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42 x 22 dia. the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + VAT = **£8.77**



Please add £1.66 + VAT = £1.95 postage & packing per order

JPG Electronics

Shaws Row, Old Road, Chesterfield, S40 2RB.

Tel 01246 211202 Fax 01246 550959

www.JPGElectronics.com

Mastercard/Visa/Switch

Callers welcome 9.30 a.m. to 5.30 p.m. Monday to Saturday

EPE EVERYDAY PRACTICAL ELECTRONICS

NEXT MONTH

20W CLASS-A AMPLIFIER

This new 20W class-A power amplifier module is a highly refined design. It features ultra-low distortion levels, very low noise levels and a greatly simplified power supply to improve overall efficiency. Since it runs in pure class-A mode, there is no crossover distortion at all – not even a little bit! Banish those class-B crossover blues with this elegant and accessible design.

CORDLESS POWER TOOL CHARGER

Cordless power tools have revolutionised the drill and screwdriver market, but the batteries are expensive and it's all too easy to 'overcook' them. Protect your investment and extend the life of your power tool rechargeable batteries with the Power Tool Charger Controller – and never roast a NiCad again!

INTELLIGENT CAR AIR-CONDITIONING CONTROLLER

Stops the air-conditioner in your car from sapping engine power when going up hills or during overtaking.

RECYCLING ELECTRONICS – £1 BATTERY CHARGER

We recently showed you how to make a super sophisticated battery charger – it was good, very good in fact, but not cheap. In the next issue we reveal how to make a super economy charger from recycled components.

OCT '08 ISSUE ON SALE SEPT 11

ADVERTISERS INDEX

AUDON ELECTRONICS	47
BETA-LAYOUT	47
CRICKLEWOOD	37
DISPLAY ELECTRONICS	72
ELECTRONWORKS	65
ESR ELECTRONIC COMPONENTS	6, Cover (iii)
JAYCAR ELECTRONICS	4/5
JPG ELECTRONICS	72
LABCENTER	Cover (iv)
LASER BUSINESS SYSTEMS	15
LEKTRONIX	29
MAGENTA ELECTRONICS	47
MICROCHIP	Cover (ii)
NURVE NETWORKS LLC	37
PEAK ELECTRONIC DESIGN	29
PICO TECHNOLOGY	17
QUASAR ELECTRONICS	2/3
SHERWOOD ELECTRONICS	47
STEWART OF READING	65

ADVERTISEMENT OFFICES:

Sequoia House, 398a Ringwood Road, Ferndown, Dorset BH22 9AU

PHONE: 01202 873872 Fax: 01202 874562

EMAIL: epeads@wimborne.co.uk


For Editorial address and phone numbers see page 7



velleman®

Free Catalogue

0845 251 4363

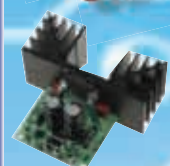

Audio Amplifier

2 x 15Wrms (4 ohm) or 2 x 10Wrms (8 ohm). Overheating & short circuit protected. No need for rectifier & smoothing, only AC supply required.

K4003 Kit £14.25
VM113 Assembled £15.95



Audio Amplifier

100Wrms @ 4ohm DC supply circuit on board with LED indication ideal for active speaker system or sub-woofer, guitar amp, home theatre systems, etc. Over-

load & short-circuit protected.

K8060 Kit £13.25
VM100 Assembled with heatsink £28.75

Audio Amplifier

Stereo 2 x 50Wrms or a Mono 100Wrms amplifier. Three input sensitivity settings. Overload & short-circuit protection, protection against incorrect power supply polarity. Speaker transient suppression.

K4004 Kit £43.95

Digital Storage Oscilloscope



PC based using supplied windows software. All standard oscilloscope functions are available. Its operation is just like a normal oscilloscope. Connection is through the computer's parallel port, the scope is completely optically isolated from the computer port.

K8031 Kit £79.00

PC Function Generator



0.01Hz to 1MHz crystal-based, optically isolated from the PC. Sine, square & triangle. Includes Windows™ '95/'98/NT/2000/XP integrated software for the function generator.

K8016 Kit £84.95

Full range of Velleman Test Equipment also available

PIC Programmer

Suitable for a wide range of Microchip® PIC™ microcontrollers, onboard configurable 40 pin. ZIF socket, Microcontroller selection using patch jumper, easy to use programming PICprog2006™ software included, SUBD connector set included.

K8076 Kit £17.95

1A Power Supply

Low cost universal symmetric power supply just add a suitable transformer and a heatsink, ... trimmers can be replaced by potentiometers to allow continuous adjustment of output, LED output indicators.

K8042 Kit £9.55



PIC Programmer

For Microchip® FLASH PIC™ microcontrollers supports 4 different 300 mil. PICs: 8p, 14p, 18p and 28p test buttons and LED indicators. Supplied with programming examples & easy connection to a PC through the serial port. Supplied with a PIC16F627 and software to compile and program your source code.

K8048 Kit £19.95

VM111 Assembled £26.95

USB Interface

A interface board with 5 digital input & 8 digital output channels. In addition, there are two analogue inputs & two analogue outputs with 8 bit resolution. All communication routines are contained in a Dynamic Link Library (DLL). You may write custom Windows (98SE, 2000, Me, XP) applications in Delphi, Visual Basic, C++ Builder or any other 32-bit Windows application development tool that supports calls to a DLL.

K8055 Kit £18.95

VM110 Assembled £29.95

USB Interface Board

With a total of 33 input/outputs: including analogue / digital and + 1PWM output. Connection to the computer is galvanically optically isolated, so that damage to the computer is not possible thus providing a high level of secure implementation. Supplied with test software & examples.

K8061 Kit £48.95

High Power LED Driver

Power up to four 1W or two 3W high-power LEDs (not incl.) Delivers accurate constant current required by most high-power LEDs, built-in rectifier for easy connection to AC source, compact size, short-circuit protected, no heatsink required.

K8071 Kit £4.95

VM143/1W for 1W LEDs £7.55

VM143/3W for 3W LEDs £7.95

Remote Control by Telephone

Turn up to three devices on or off over the telephone. It is also possible to check the condition of a switch (open or closed). A major advantage of this circuit lies in the fact that audio signals are used to tell whether a specific output has been turned on or off. Operation is protected by a user defined code, which is simply keyed in from the telephone keypad.

K6501 Kit £29.95

USB DMX Interface

Control DMX fixtures using a PC and USB interface, test software and "DMX Light Player" software is included, a DLL is provided to write your own software. Stand-alone test function that outputs all 512 channels at a time, with adjustable levels.

Supplied with case, lead & CDROM

K8062 Kit £46.95




VM116 Assembled £49.95

Remote Control Transmitter

For use with the K8057/VM109 2-channel RF receivers.

Generates unique 32-bit code more than 1,000,000,000 unique codes code can easily be changed for safety purposes choose continuous or 'burst' transmission LED indicator.

K8059 Kit £8.95

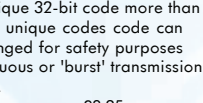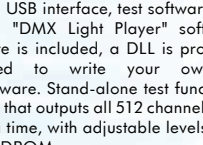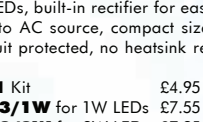

Remote Control Receiver

Two relay contact outputs for use with K8059 and VM108 two channel RF code lock transmitters, toggle or pulse function selectable per output, can learn a unique 32-bit code from the transmitters, store up to 31 transmitters, LED indicators for outputs and functions.

K8057 Kit £12.55

Remote Control Transmitter

Compact 2-button IR keychain remote compatible with most Velleman IR receivers, 2 powerful IR LEDs for a range of up to 15m, 16 channels (allow use of multiple transmitters in one room), easy channel configuration, no jumpers required.

MK162 Mini Kit £6.25

Remote Control Receiver

Two channels with relay output (24VAC/DC 1A max.) ultra compact channel and reception indication through LEDs to toggle / pulse selection for each channel learn mode for channel ID all settings are stored in EEPROM compatible with most Velleman Kit IR remotes.

MK161 Mini Kit £7.95

3-30V 3A Power Supply

Suitable as a power supply for all common Velleman kits using a stabilised DC voltage between 3 and 30V, 3A max. Of course this power supply unit can also be used for other purposes. By replacing the

trimmer by a potentiometer, it may even be used as an adjustable power supply unit. Supplied with heat sink.

K7203 Kit £19.95

Sound to Light Unit

Low, mid and high channels. Sensitivity adjustment per channel. LED indication per channel. Attractive translucent enclosure. Microphone included. Noise suppressed according to EN55015

K8017 Kit £27.55

Clap On/Off Switch

Operate your lighting simply by clapping your hands. Good immunity against surrounding noises, '1-clap' or '2-clap'-mode selection, '2-clap'-mode features built-in safety turn-off timer (approx. 5h), output relay 'pulse' or 'toggle' selection.

MK139 Mini Kit £7.95

Voice Changer

Make your voice sound like a robot, add vibrato effect, use the 'pitch'-buttons and make your voice sound lower or higher, built-in microphone and power amplifier with volume control, just add a speaker.

MK171 Mini Kit £7.95

Ultrasonic Radar Module

Buzzer output: fast / slow / continuous distance indication with 3-LED-bar adjustable alarm. LED alarm indicator, dry contact NO/NC relay

VM125 Assembled £18.25

Mini PIC Application Module

Create your own custom PIC application without the hassle of making the hardware. 9 Free programmable I/Os. Onboard Relay, LEDs & Buzzer. PIC16F630 inc.

VM142 Assembled £20.95



Over 300 Kits, Mini Kits & Modules - Full Catalogue Available



Tel: 0191 2514363
Fax: 0191 2522296
sales@esr.co.uk

Station Road
Cullercoats
Tyne & Wear
NE30 4PQ



Prices Exclude Vat @17%.
UK Carriage £2.50 (less than 1kg)
£5.50 greater than 1kg or >£30
Cheques / Postal orders payable to
ESR Electronic Components Ltd.
PLEASE ADD CARRIAGE & VAT TO ALL ORDERS

The Proteus Design Suite

Celebrating 20 Years of Innovation



- ↓ **1988** Labcenter commences trading with PC-B for DOS
- ↓ **1989.** First integrated autorouter added for PCB Design.
- ↓ **1990** Schematic Capture added to PCB Layout package
- ↓ **1991. World First** Schematic Capture for Windows™.
- ↓ **1992.** Topological route editing for easier PCB layout.
- ↓ **1993. Proteus** offers fully integrated circuit simulation.
- ↓ **1994.** Autorouter enhanced with Rip-Up and Retry algorithm.
- ↓ **1995** Gridless, shape based power plane support
- ↓ **1996.** True, mixed mode SPICE simulation introduced.
- ↓ **1997.** Interactive simulation - ideal for educational users.
- ↓ **1998.** PIC microcontroller simulation technology developed.
- ↓ **1999.** 8051 microcontroller simulation technology developed.
- ↓ **2000** World First Interactive MCU co-simulation (VSM)
- ↓ **2001.** High level language support added for MCU simulation.
- ↓ **2002.** ELECTRA adaptive shape based router interface added.
- ↓ **2003. World First** 32 bit MCU simulation support with ARM7.
- ↓ **2004.** Integration between Proteus VSM and MPLAB™.
- ↓ **2005** Redesigned GUI across the Proteus Design Suite
- ↓ **2006.** 3D visualisation engine integrated with ARES PCB Design.
- ↓ **2007. World First** USB schematic based USB Simulation.
- ↓ **2008** Coming Soon: Introduction of HDL support in simulation, ODB++ manufacturing output, improved core SPICE simulation algorithms, enhanced live DRC error checking and much more.

LABCENTER ELECTRONICS LTD

A technology pioneer in the EDA Industry since 1988
 Technical Support direct from the program authors
 Flexible packages and pricing tailored to customer requirements.

Labcenter  **www.labcenter.com**
Electronics



Labcenter Electronics Ltd. 53-55 Main Street, Grassington,
 North Yorks. BD23 5AA. Registered in England 4692454
 Tel: +44 (0)1756 753440, Email: info@labcenter.com